


TESCO METERING

# Practical Use of Vectors in Electric Metering and Field Testing at Instrument Rated Services

*TESCO's Meter School*  
**TESCOOL**  
*July 20-23, 2025*

July 22, 2025  
8:45 AM -10:15 AM  
Carl Chermak

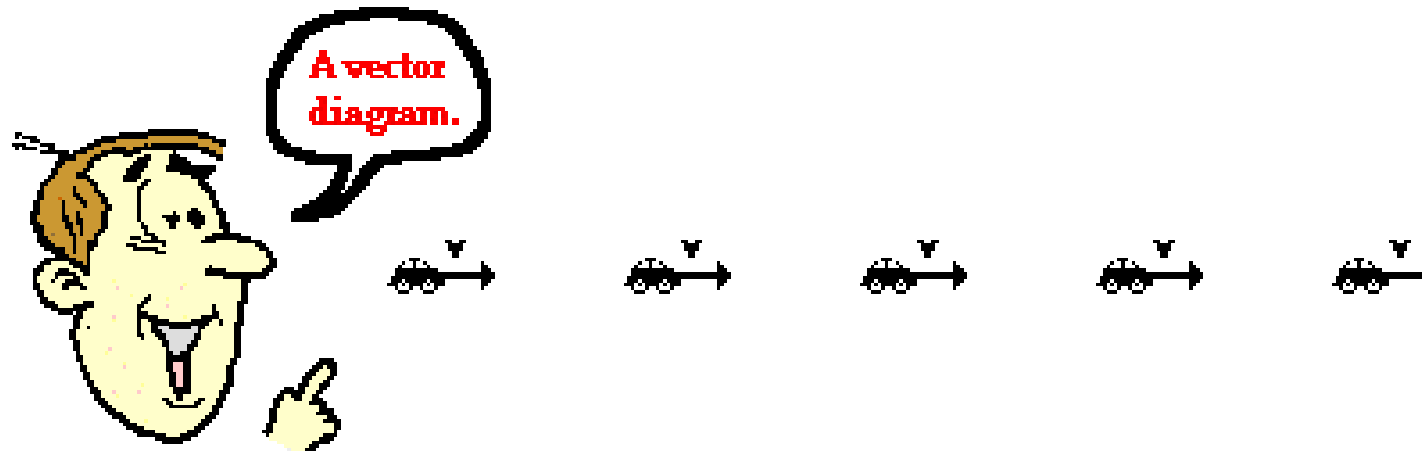- Electrical Quantities are Difficult to Visualize.
- Written or Spoken work is inadequate.
  - Usually hard to explain in a universally understood way.
  - Would take a relatively long time to explain.
- Employ Vector Diagram to Represent Electrical Quantities.
  - Saves time
  - Vastly more effective, once it is understood



## The most basic statement of metering:

$$\text{Watts} = \text{Voltage} \times \text{Current} \times$$


Power Factor Mathematically:

$$\text{Watts} = V \times I \times \cos \theta$$

## What is a Vector?



A measurement that takes two numbers to represent.

BOTH a magnitude (size) and direction

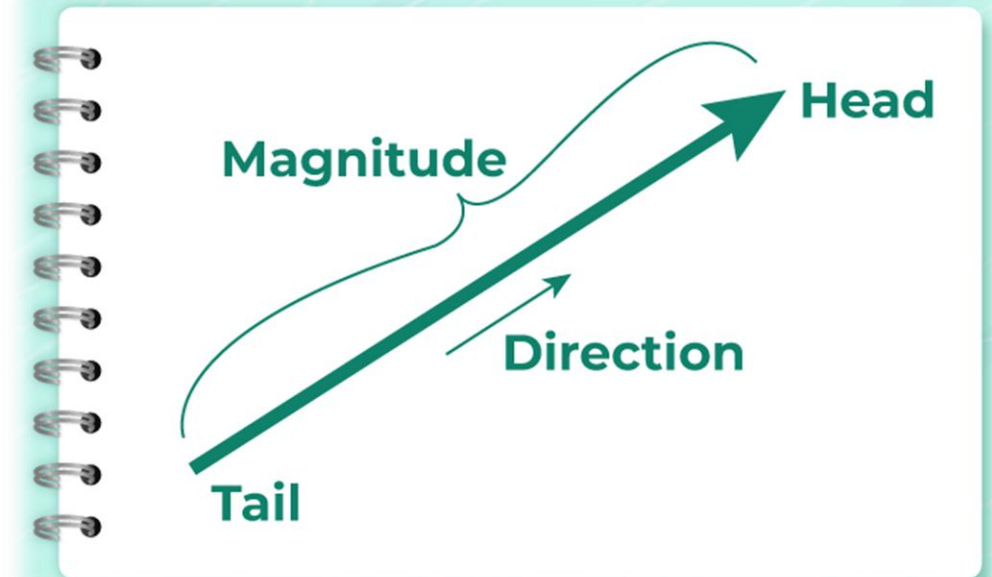
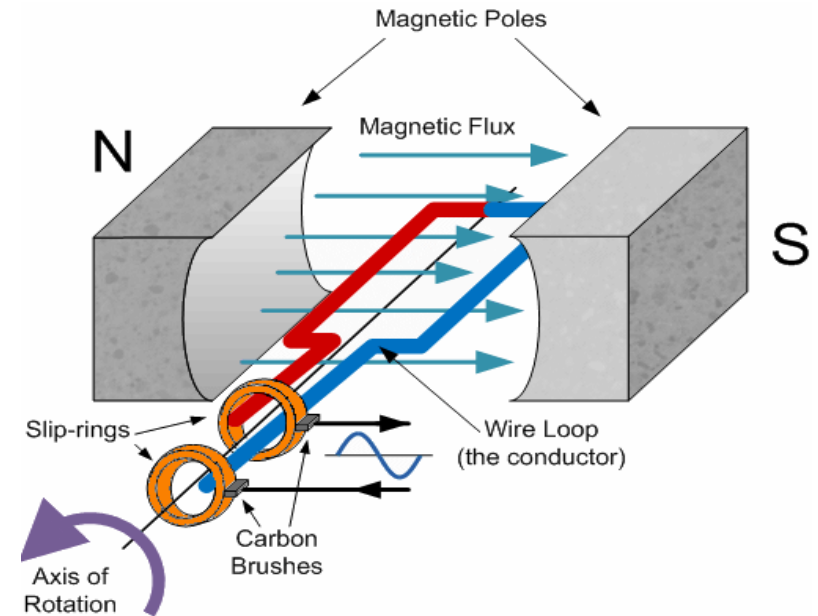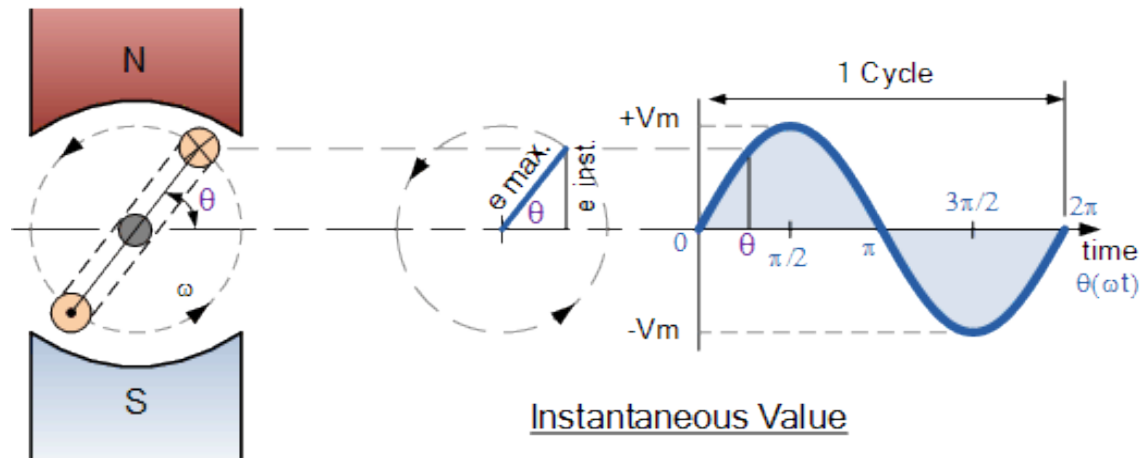
# Origination of a Sinusoid


- By Electromagnetic Induction, a single wire conductor passing through a permanent magnetic field and cutting the lines of magnetic flux, will produce an ElectroMotive Force (EMF).
- Due to the constant rotation, the EMF is different at each moment in time. The instantaneous value at each moment is considered the Instantaneous Voltage. Commonly, the symbol **E** and **V** are interchanged to represent voltage values.



4




Reference: <https://www.electronics-tutorials.ws/accircuits/sinusoidal-waveform.html>

# "Time" in Degrees

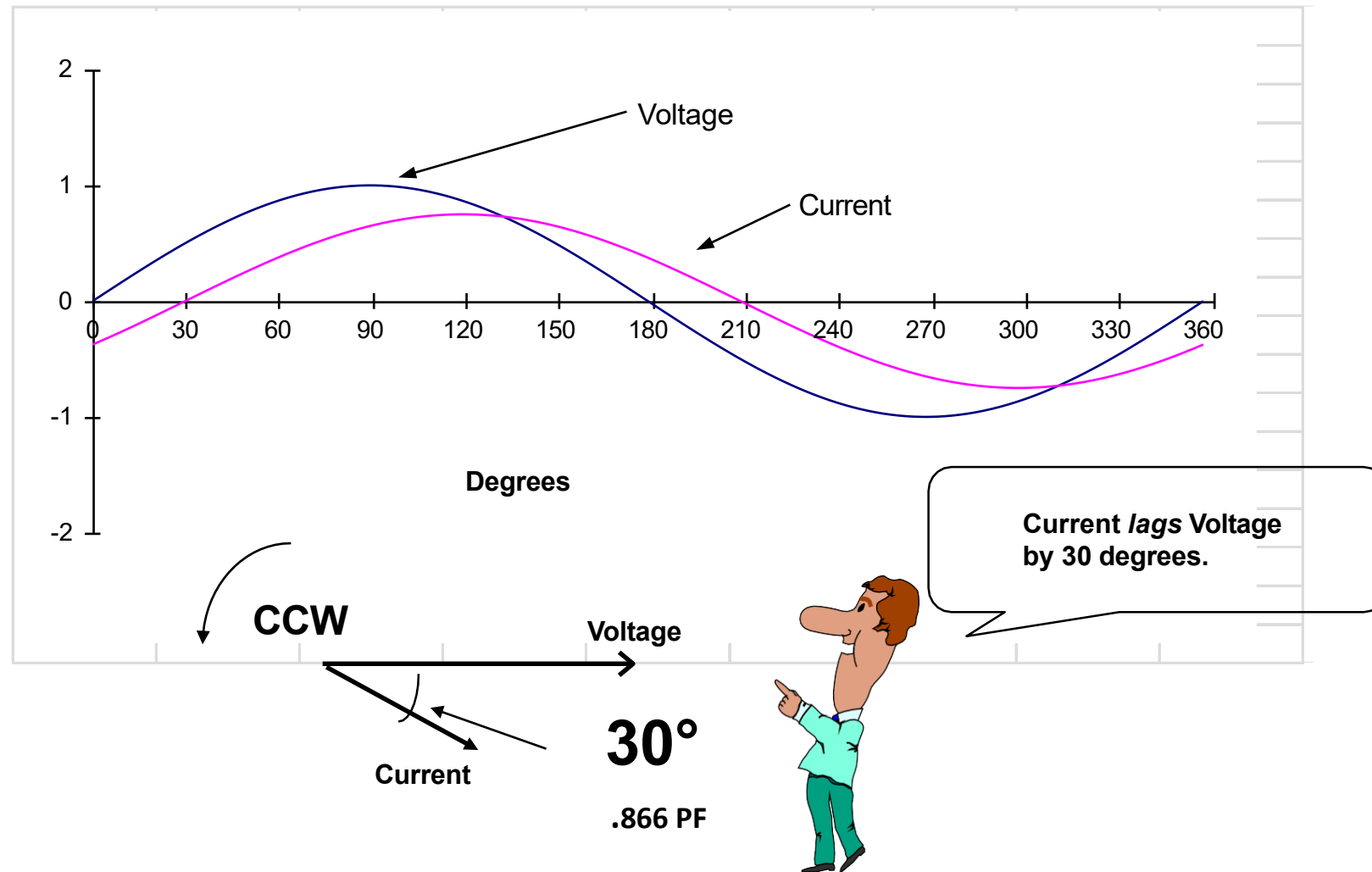


# "Time" in Degrees

1

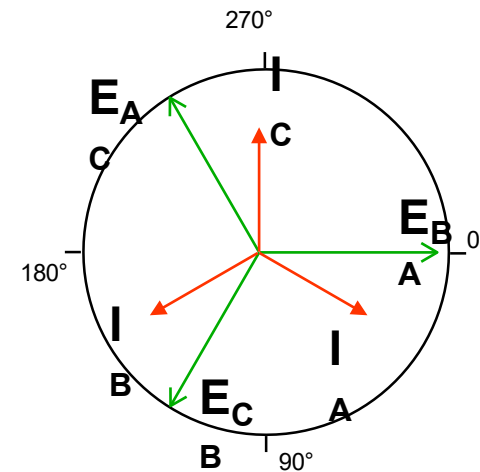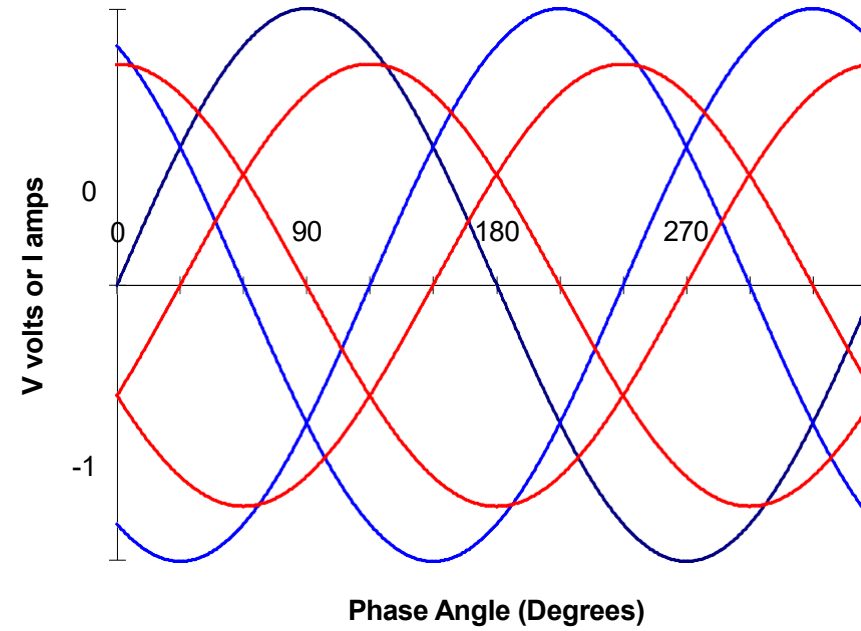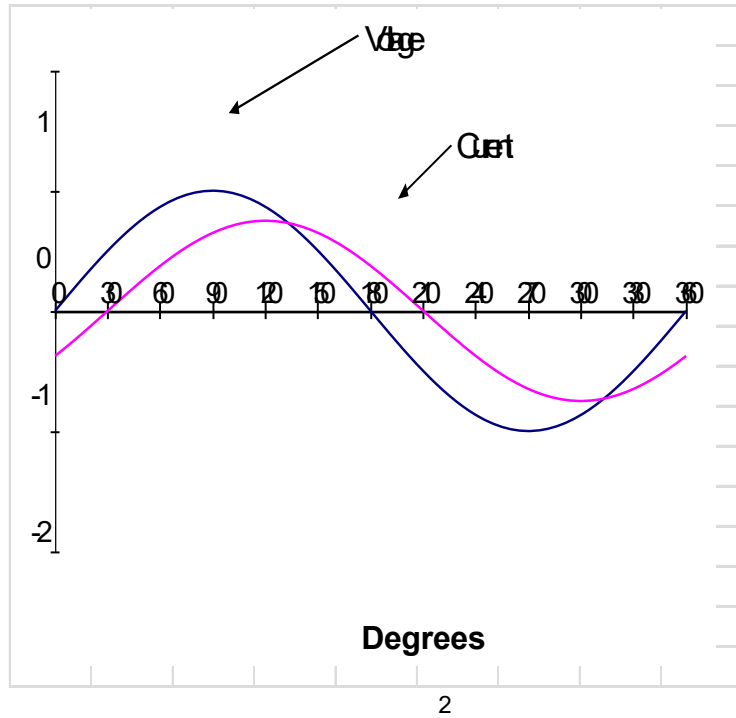


# AC Voltage and Current

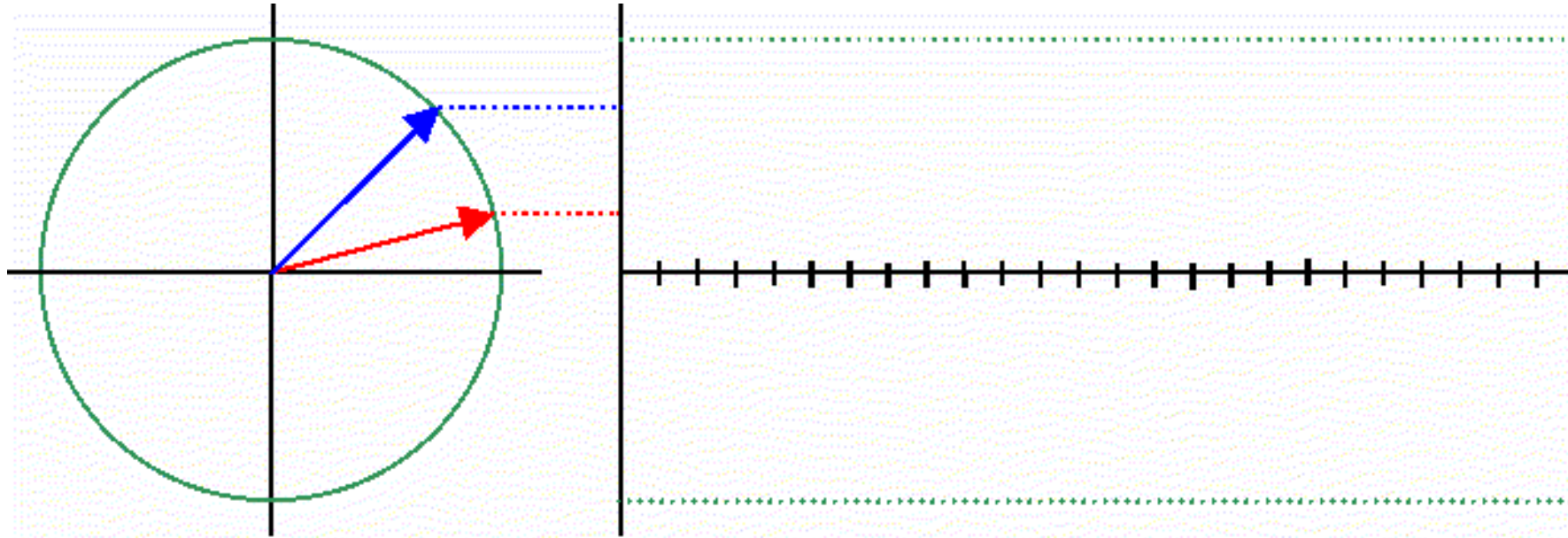
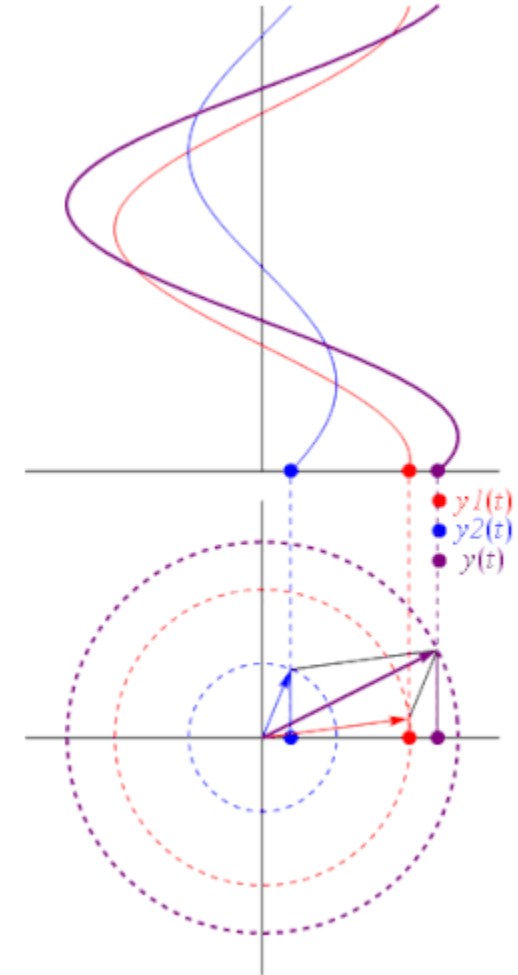
## A Symbolic Representation of the relationship of the voltage and current


- **Vectors & Vector Diagrams**
  - **SIMPLE.** Used to Represent Electrical Quantities.
  - **QUICK.** Saves time.
  - **Vastly more effective**
  - **Also referred to as “Phasors”**





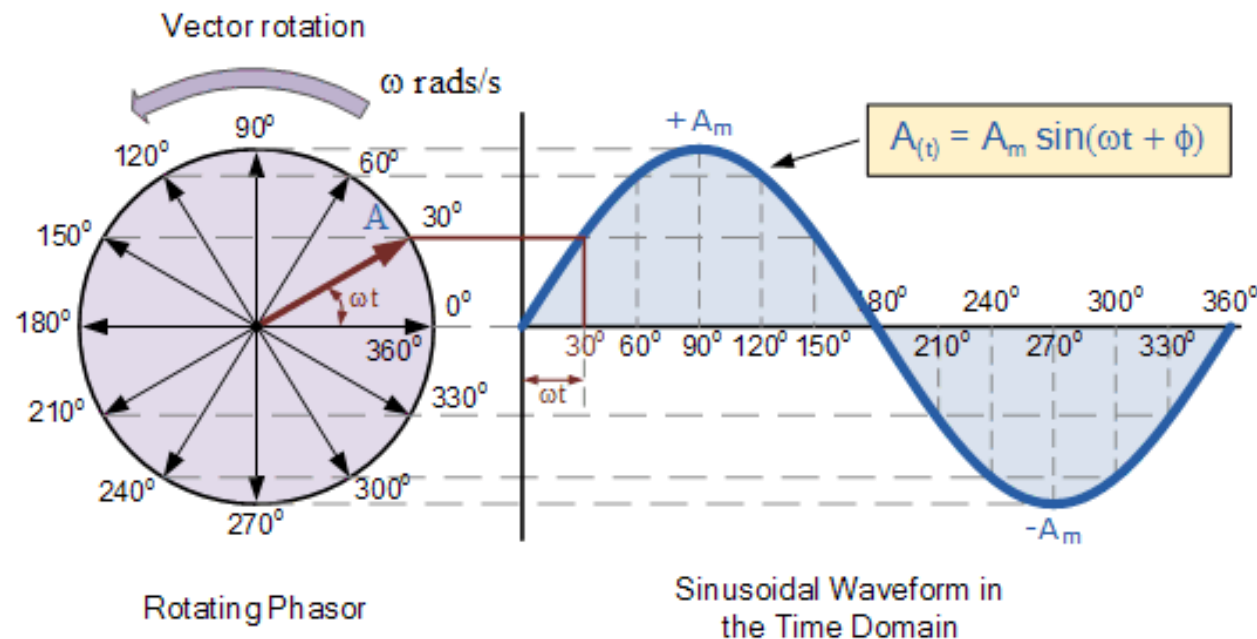
# The Phasor Diagram



- A phasor diagram is a method of expressing the magnitudes and time relationships (or phase angle relationships) between two or more sinusoidal quantities of the same frequency.
- Each alternating quantity having the same frequency can be represented on the same diagram by additional lines. Their time relationship will determine the angle between the lines.
- The phasor diagram is a “snap-shot” of the set of lines at an instant in time. The instant is generally chosen to be the time at which the voltage passes through zero in the positive direction. If there is more than one voltage, the instant at which phase A voltage passes through zero is chosen.



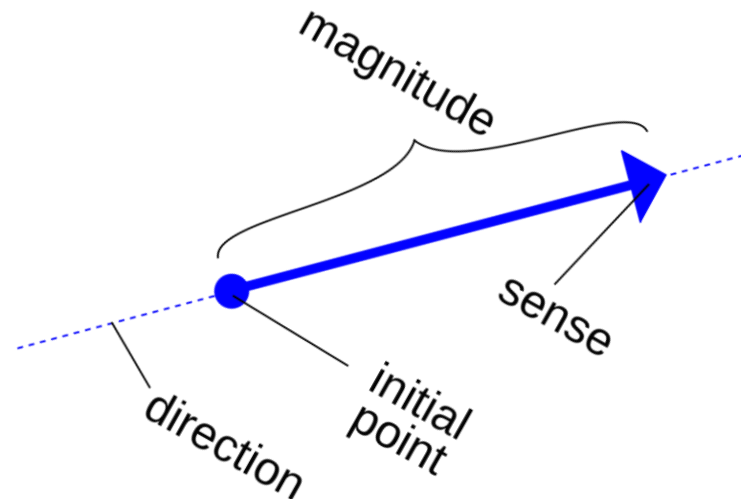- Vectors all have **MAGNITUDE** and **DIRECTION**
- Line length can represent **MAGNITUDE**.
- Line with arrowhead in a given direction indicates that quantity's relationship to any other quantity being represented.
- **DIRECTION:** Angles between lines take on significance. They represent time (shown in degrees instead of seconds).



# Placing Coils in Order

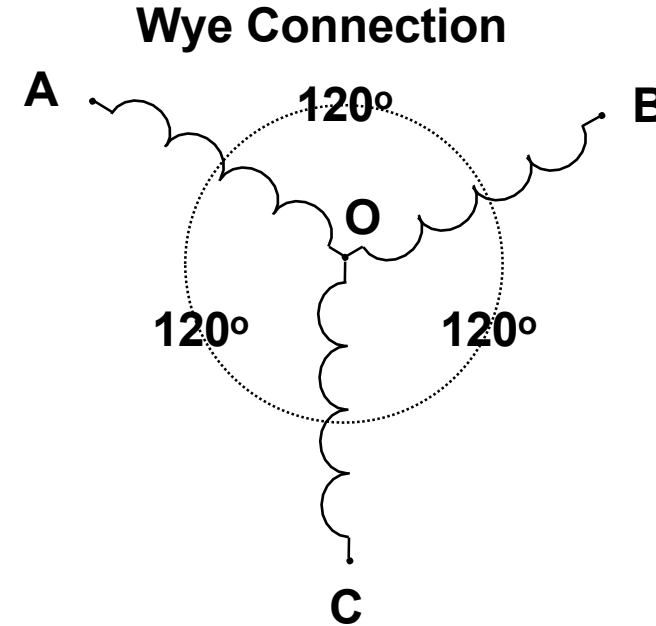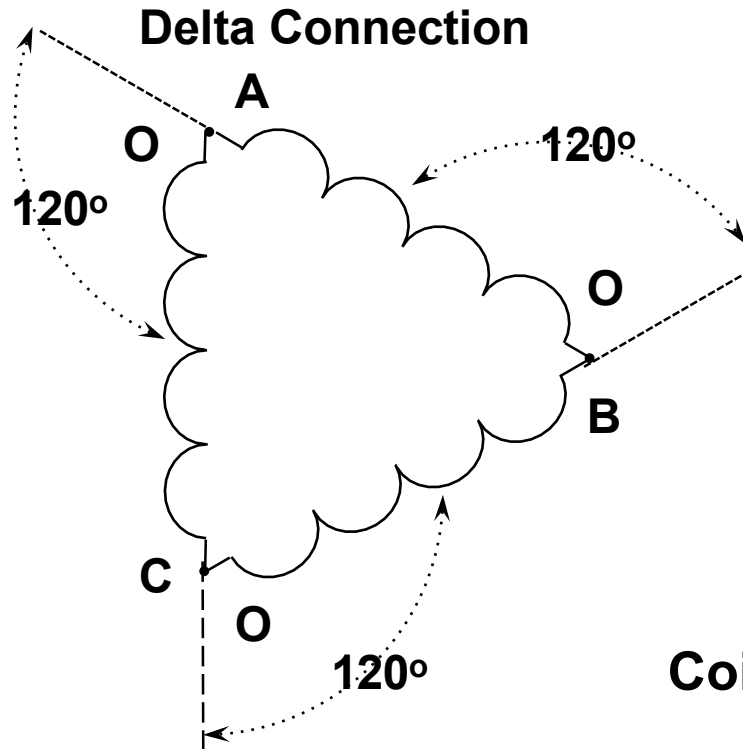

**Coils connected together  
and placed on an alternator in order  
OA, OB, and OC  
(Changing Coil order changes Sequence)**


## General Guidelines

- Complete circle (360 Degrees) equal one cycle of the frequency displayed.
- **One component (Usually Phase A voltage) becomes the reference and is placed at zero degrees.**
- Use “open” arrowhead on voltage line(s).
- Use “closed” (or filled in) arrowhead on current line(s).
- Label all voltages and currents by phase.
- Indicate Phase Rotation (counter-clockwise assumed if not noted).

- **Watthour meter theory review:**
  - If we apply “V” volts and “I” amps to a meter, and the phase angle between the voltage and current is some angle  $\theta$ , the meter speed will be proportional to:


$$\text{Watts} = V \times I \times \cos \theta$$

VECTORIALLY

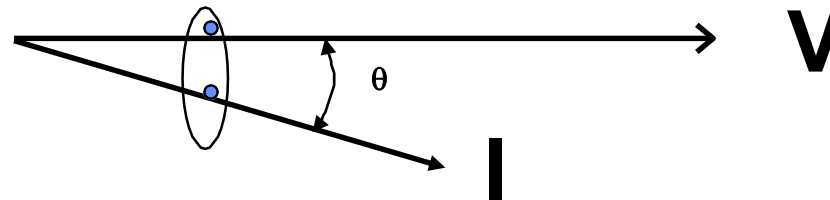

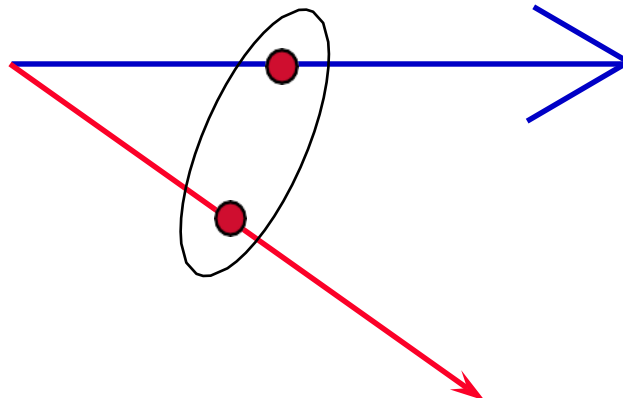
# Analyzing the Phasor Picture


- Both voltage & current are required in each meter element (stator) for that element to have an effect on registration.
- Time relationship (degrees separation) between voltage & current acting together on each element will determine that element's effect.
- Only angles of less than 90 Degrees between the current and voltage on any meter element will cause positive watthour registration.




# The Phasor Diagram

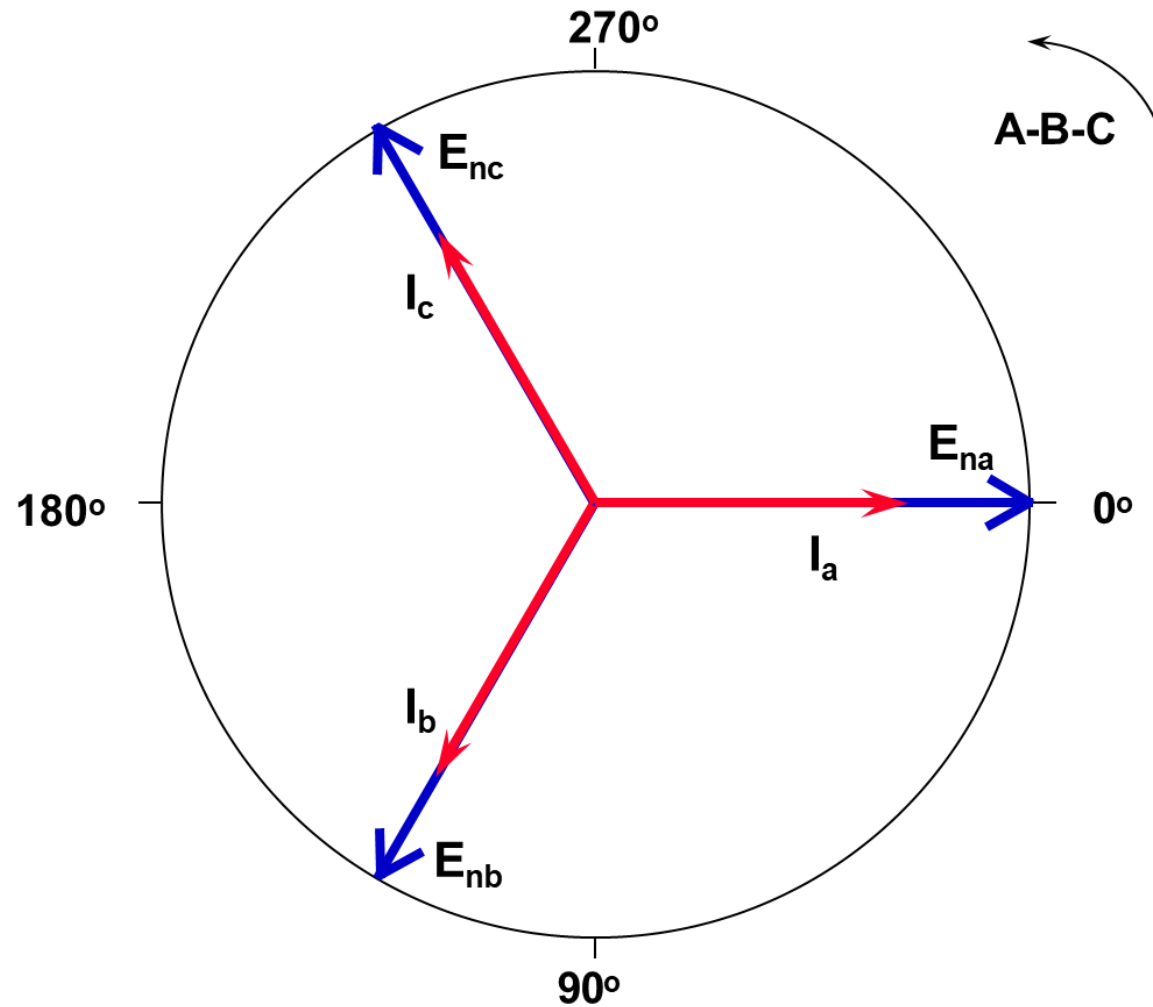

# Service & Meter Phasors

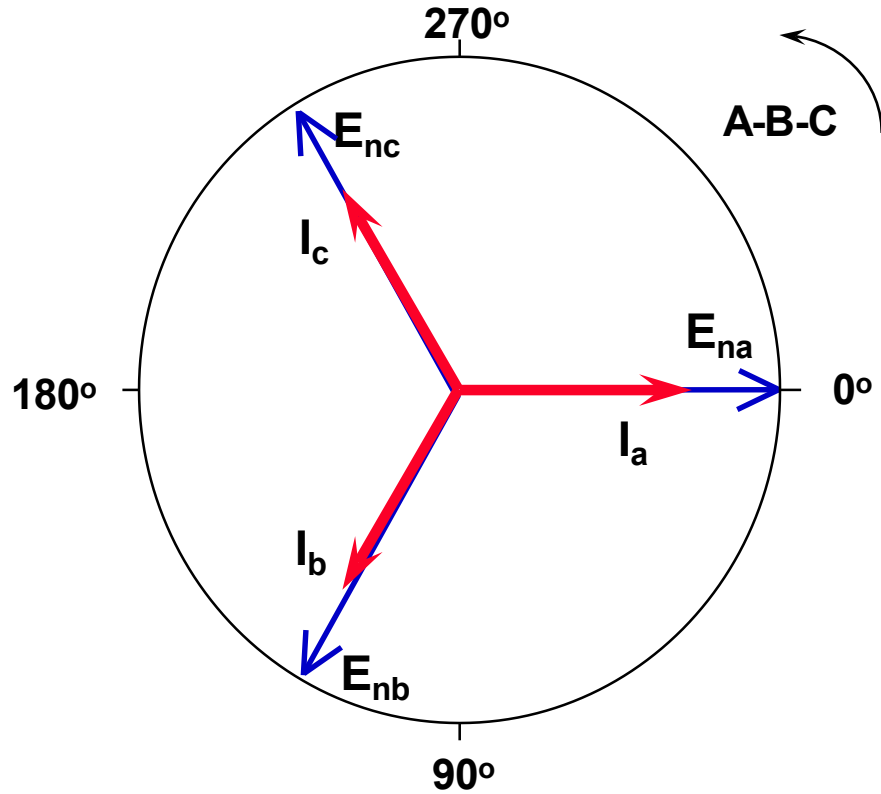

**Service Phasors**








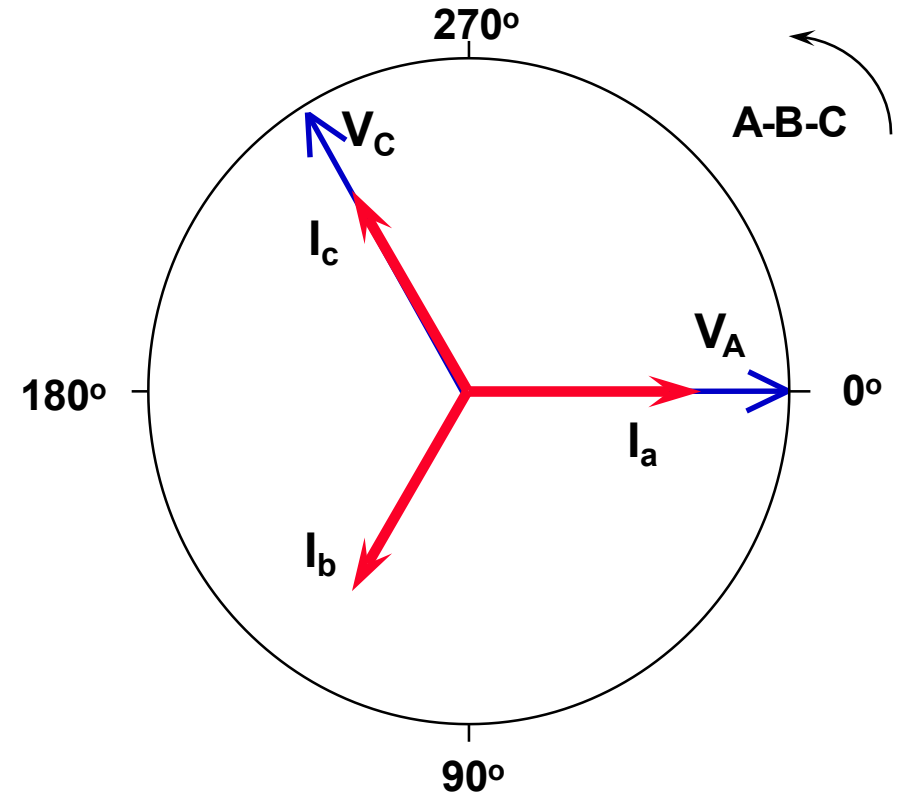


**Meter Phasors**


**2 ½ Element**




# Load Caused Phase Angles

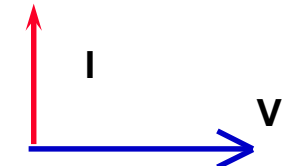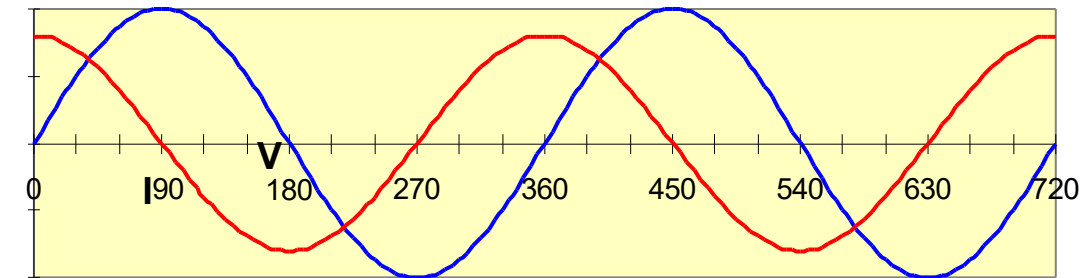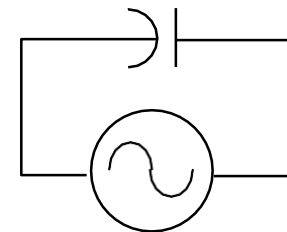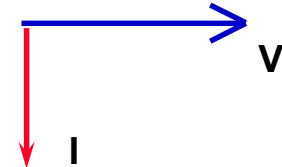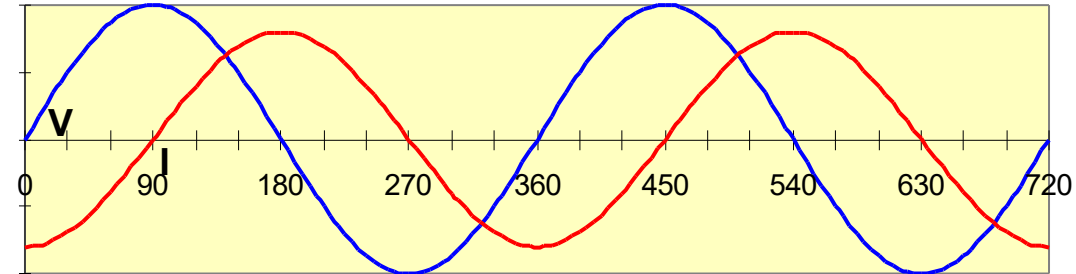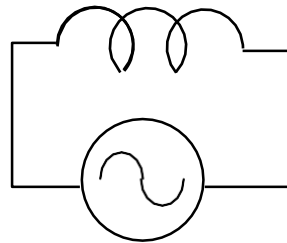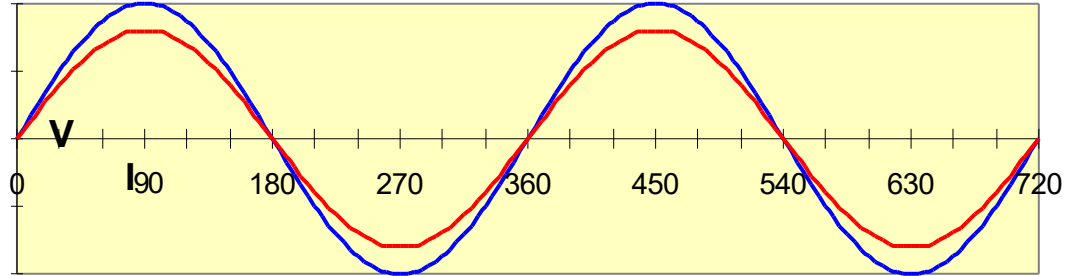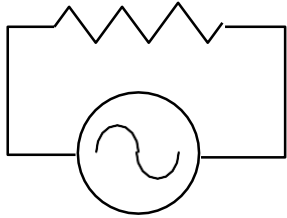

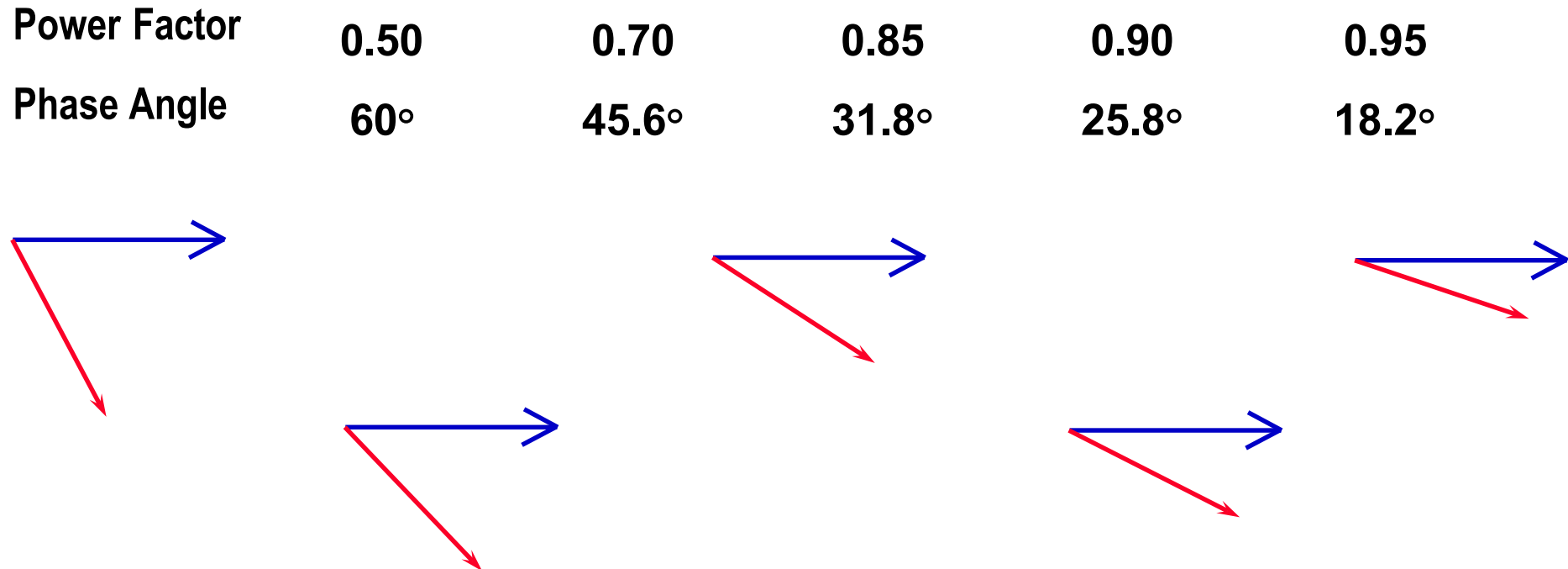- We represent energy as:  $\text{Energy} = E \times I \times \cos \theta \times t$ 
  - $\theta$  is the angle between V and I
  - $\cos \theta$  is also known as Power Factor
- What  $\theta$  values give with these lagging Power Factors?





# Three Wire Delta Source

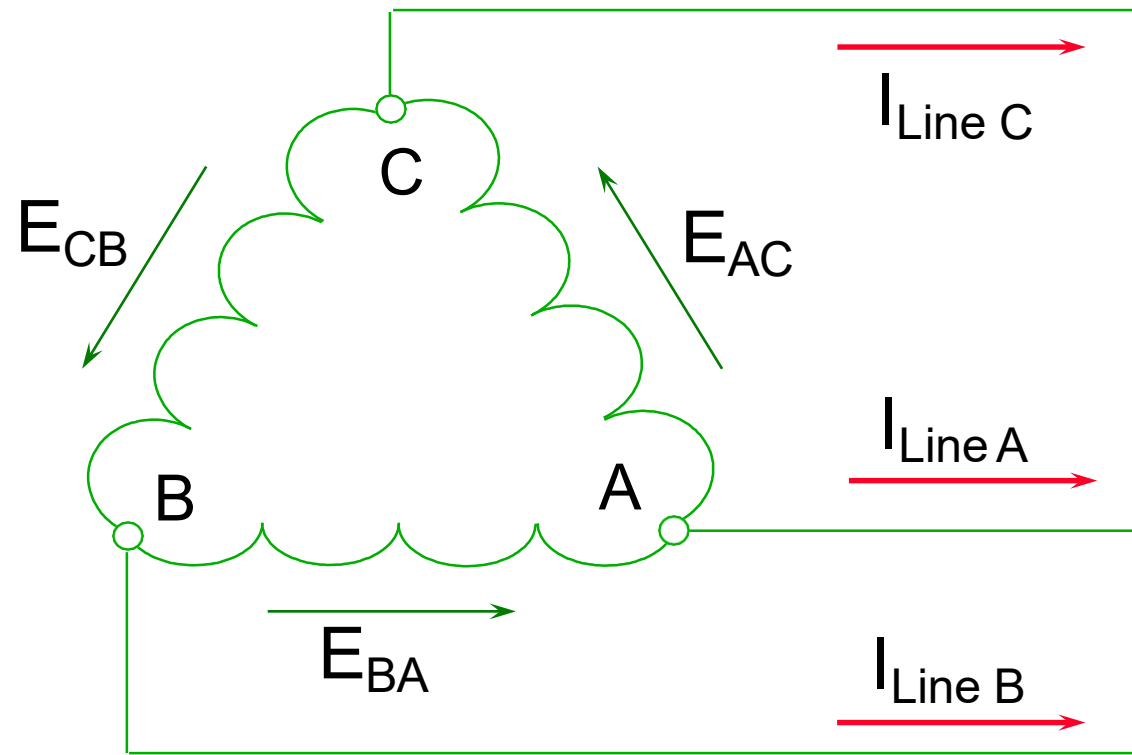

**With pure resistance balanced three-phase load, the current in each supply transformer is in phase with the voltage across each transformer.**

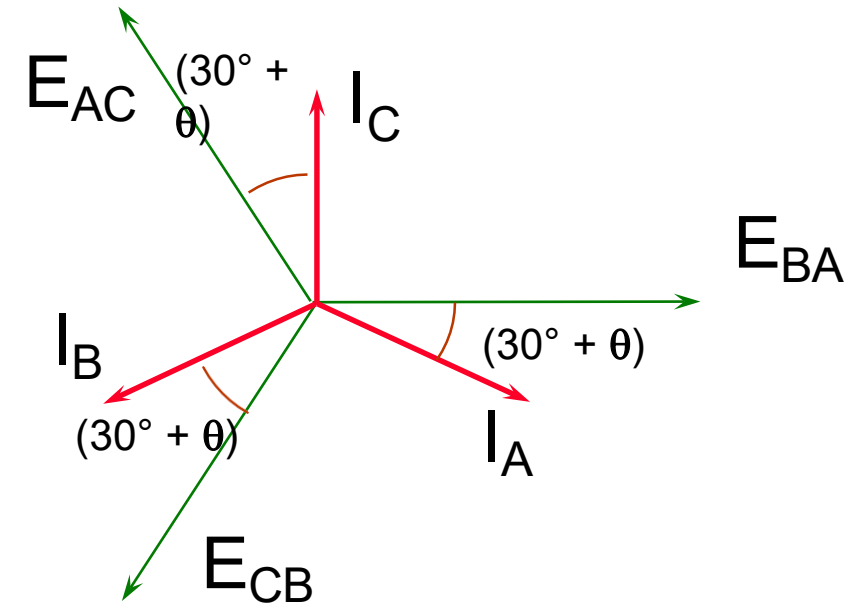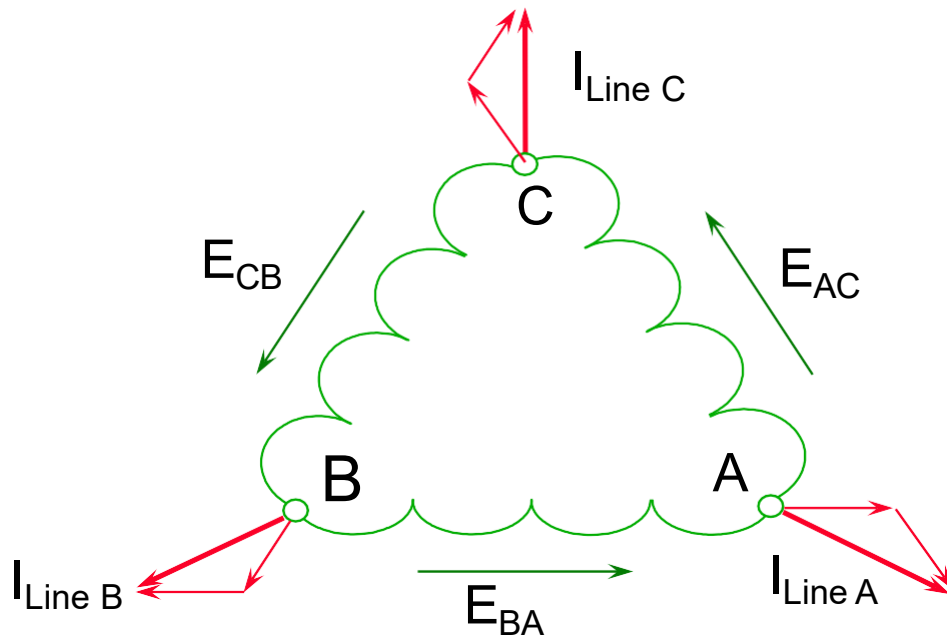
## Phasor diagram for delta-connected three-phase system with three-phase delta-connected resistance load




Phase voltages =  $E_{BA}$ ,  $E_{CB}$ , &  $E_{AC}$


Line currents =  $I_A$ ,  $I_B$ , &  $I_C$

# Phasors for Source & Meter

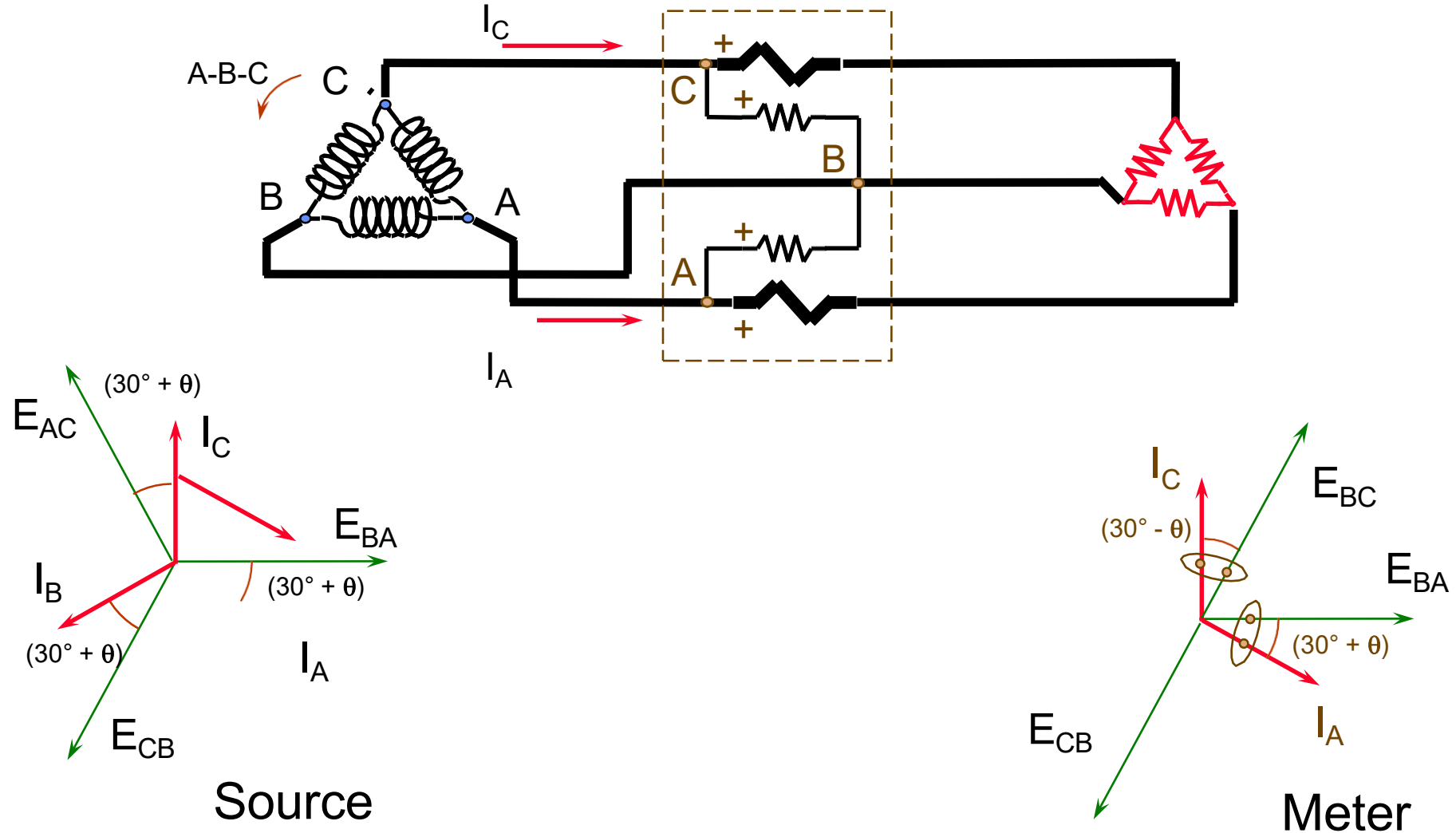


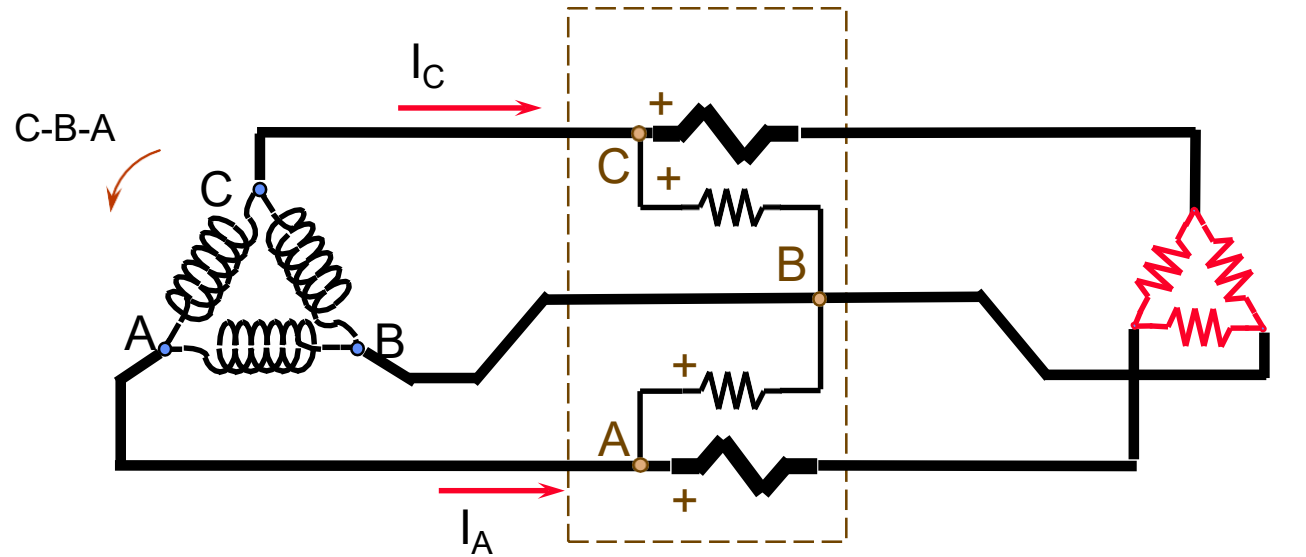


C-B-A  
Meter  
Phasors

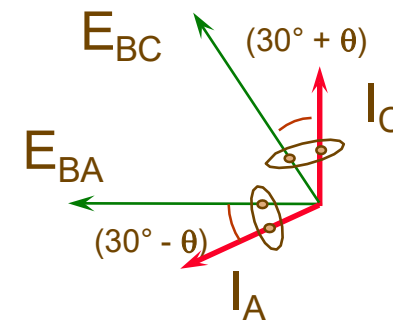


# Common Distribution Circuits

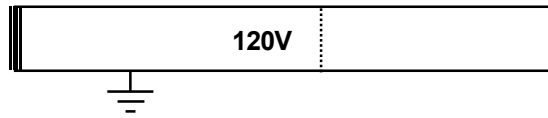


**Two-Wire  
Single Phase**

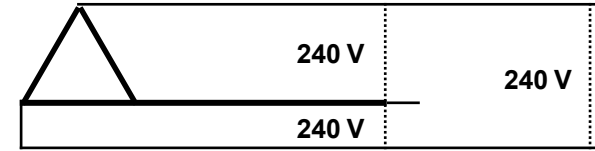


**Three-Wire  
Three Phase  
Delta**

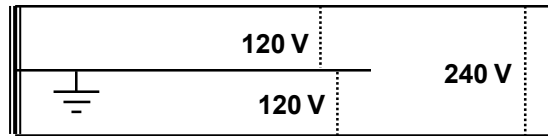


**Three-Wire  
Single Phase**

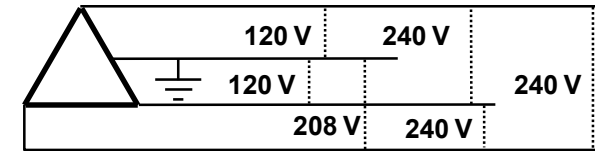

**Four-Wire  
Three Phase  
Delta**

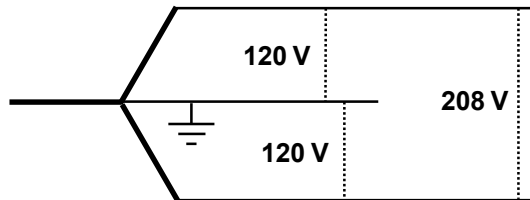


**Three-Wire  
Network**

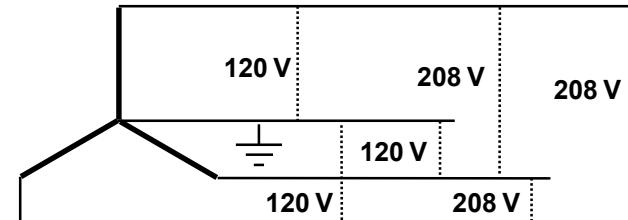

**Four-Wire  
Three Phase  
Wye**
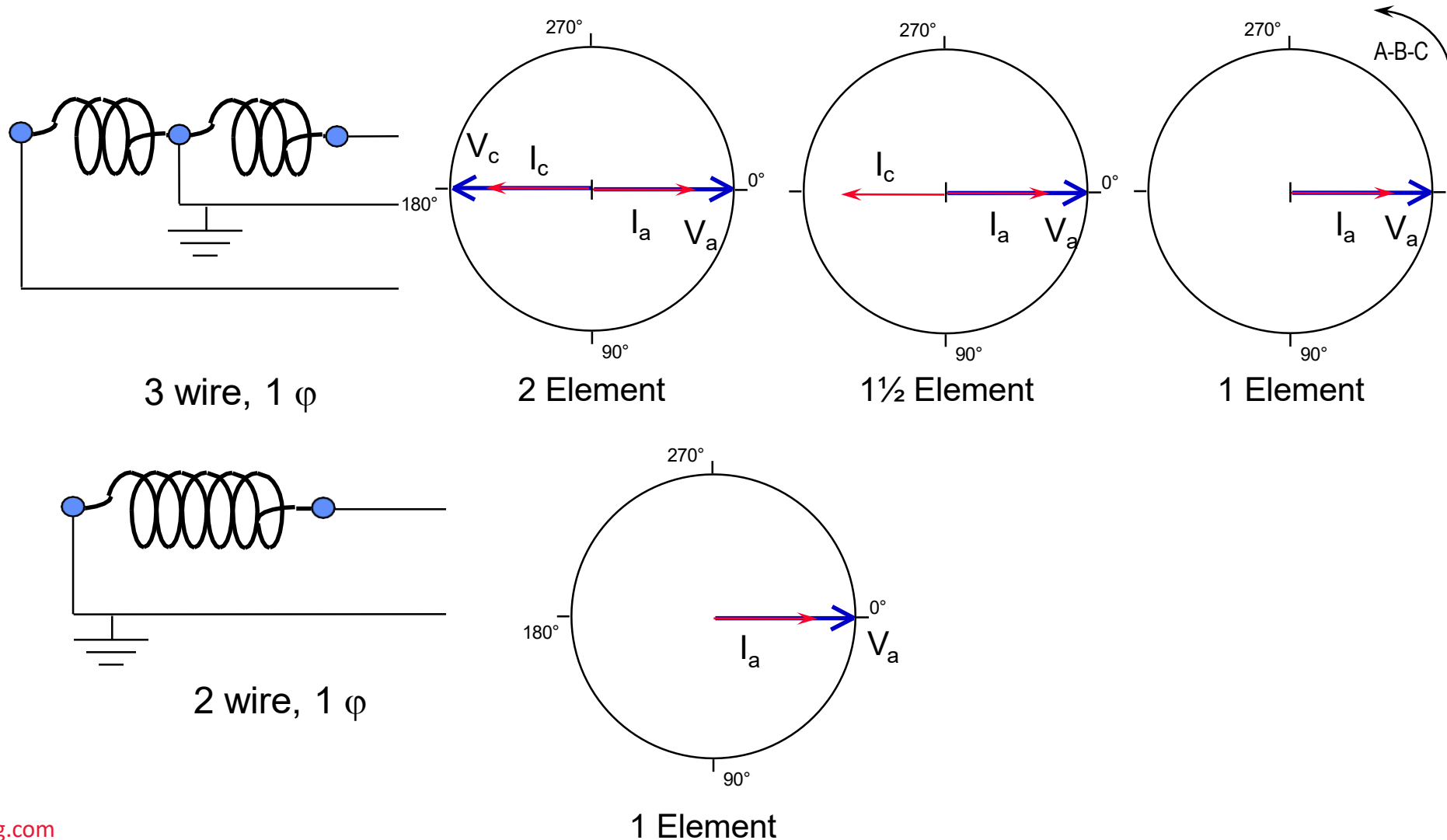
# 1 $\phi$ Expected Meter Phasors


(BALANCED LOAD AT POWER FACTOR = 1, ABC PHASE SEQUENCE)





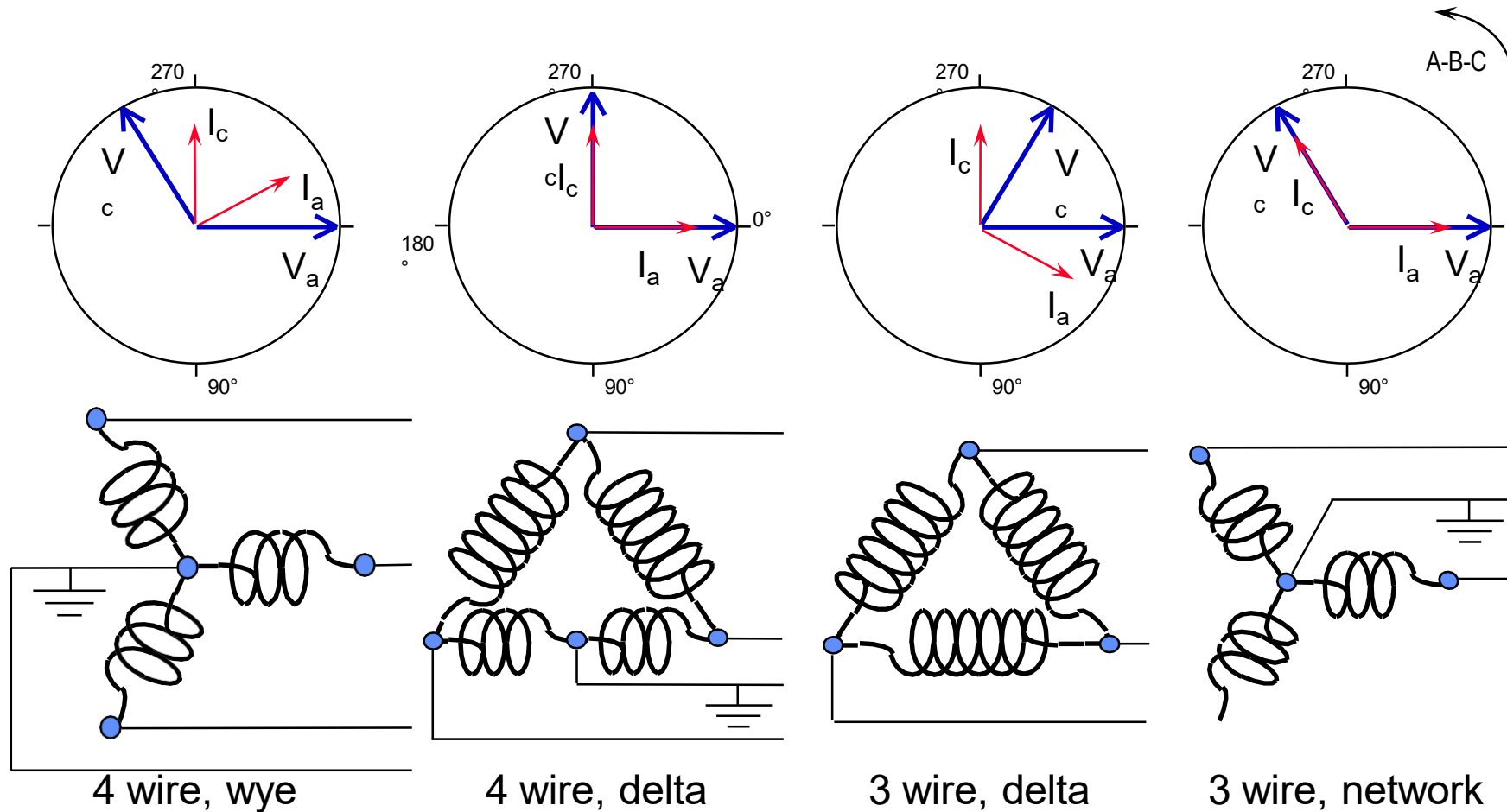
# 2 Element Expected Meter Phasors

(BALANCED LOAD AT POWER FACTOR = 1, ABC PHASE SEQUENCE)



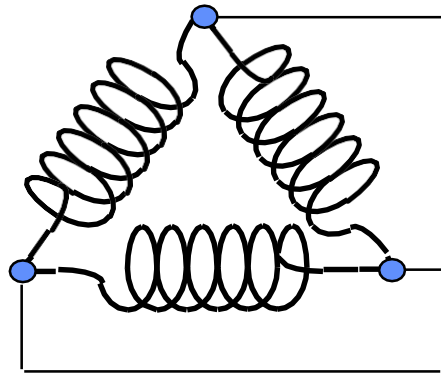
# Expected Meter Phasors


(AT POWER FACTOR = 1, ABC PHASE SEQUENCE)




3 wire, delta

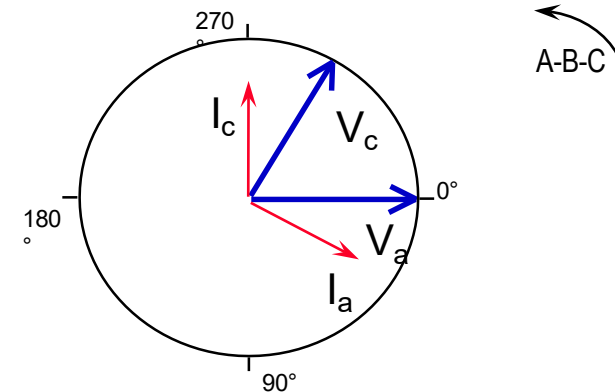

2 Element

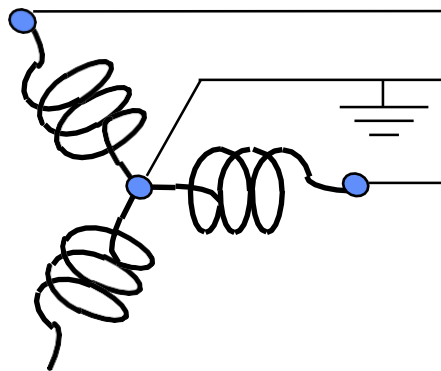



3 wire, network

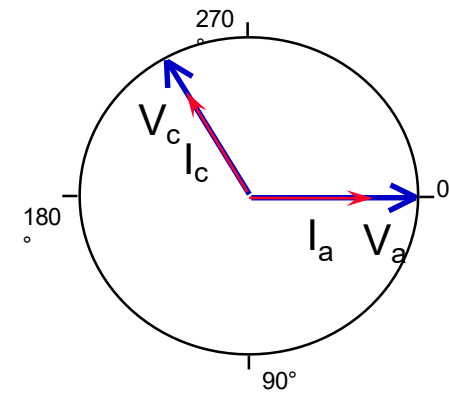


2 Element
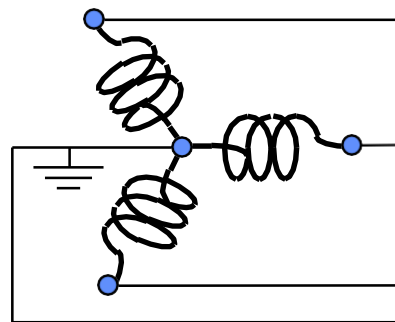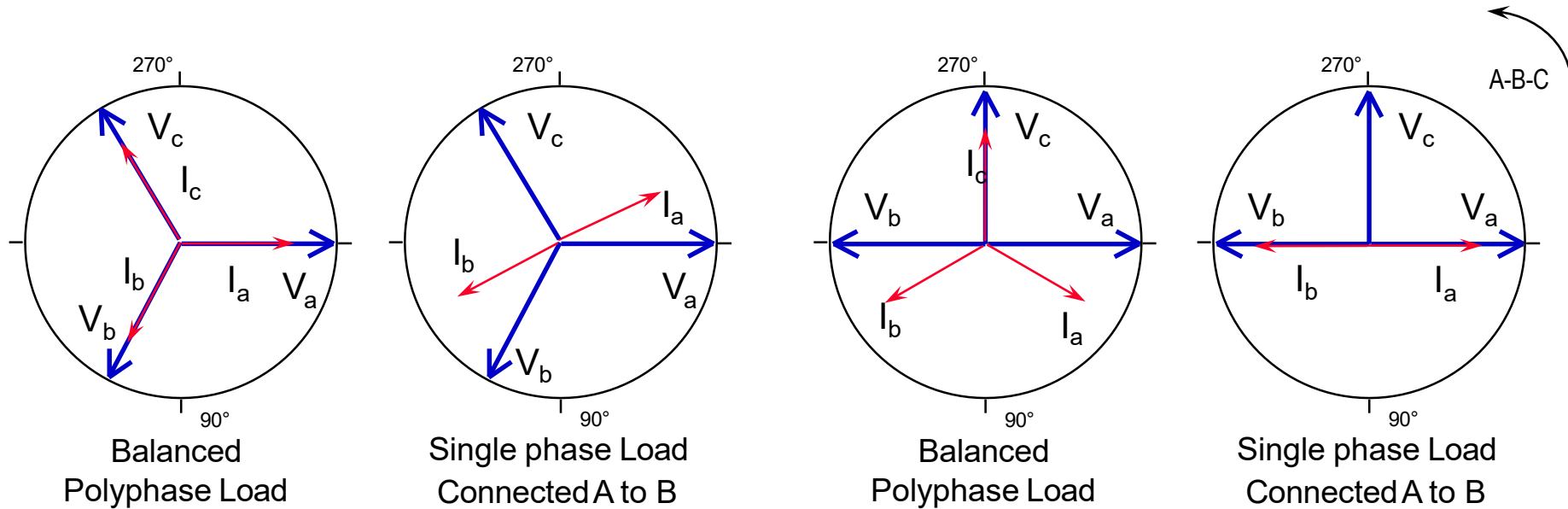
# 3 Element Expected Meter Phasors

(AT POWER FACTOR = 1, ABC PHASE SEQUENCE)




4 wire, wye

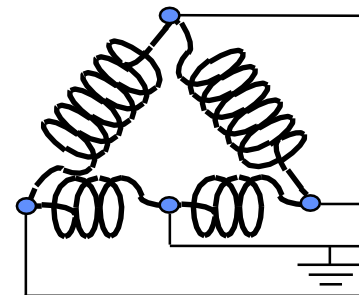


4 wire, delta
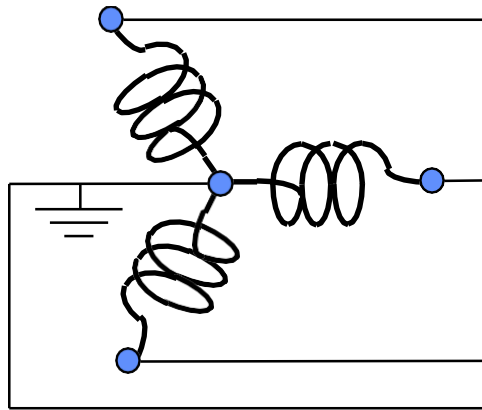
# Expected Meter Phasors


(AT POWER FACTOR = 1, ABC PHASE SEQUENCE)




4 wire, wye

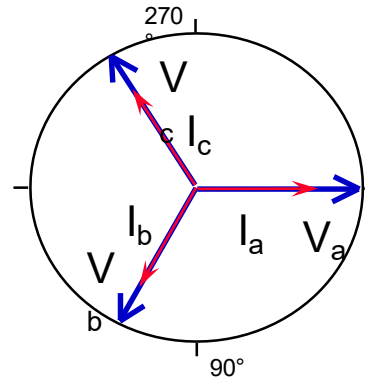


3 Element

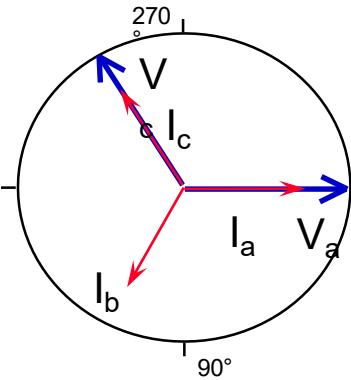


2½ Element

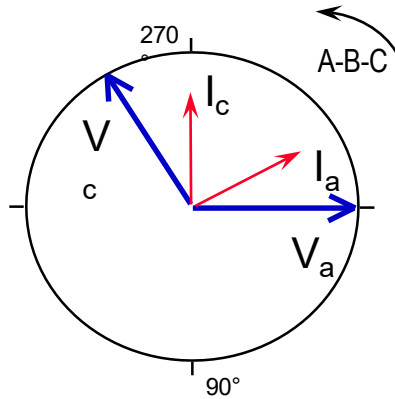


2 Element

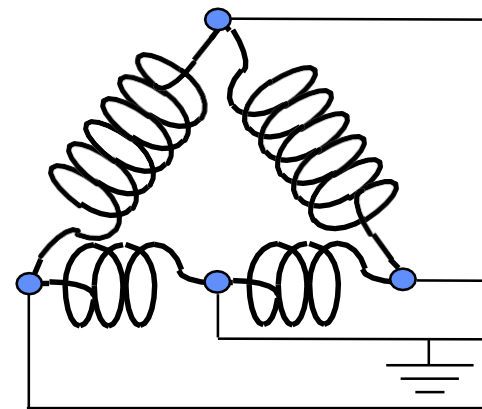

4 wire, delta

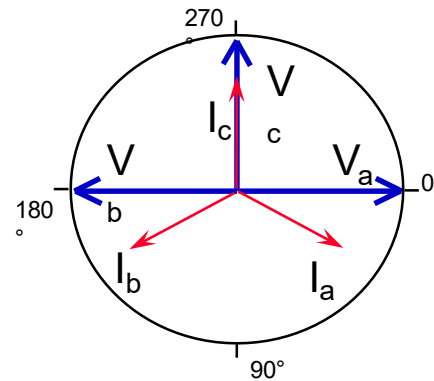


3 Element

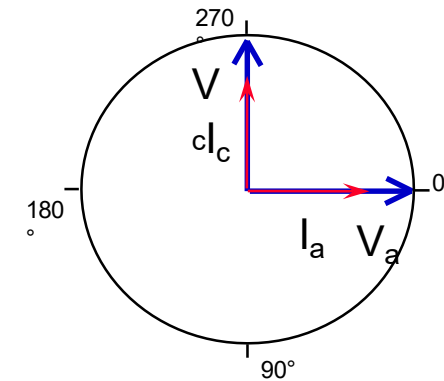

2 Element
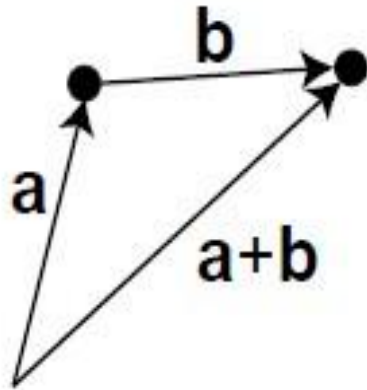
# Let's Talk about Why We Need to Understand Vectors.






Addition of vectors can be expressed by a diagram. Placing the vectors end to end, the vector from the start of the first vector to the end of the second vector is the sum of the vectors. One way to think of this is that we start at the beginning of the first vector, travel along that vector to its end, and then travel from the start of the second vector to its end. An arrow constructed between the starting and ending points defines a new vector, which is the sum of the original vectors. Algebraically, this is equivalent to adding corresponding terms of the two vectors:

$$\mathbf{a} + \mathbf{b} = \begin{bmatrix} a_x \\ a_y \end{bmatrix} + \begin{bmatrix} b_x \\ b_y \end{bmatrix} = \begin{bmatrix} a_x + b_x \\ a_y + b_y \end{bmatrix}.$$

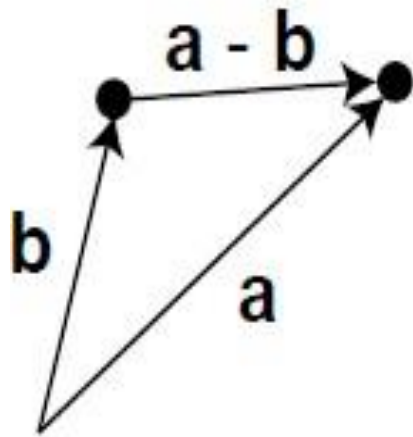
We can think of this as again making a trip from the start of the first vector to the end of the second vector, but this time traveling first horizontally the distance  $a_x + b_x$  and then vertically the distance  $a_y + b_y$ .






Subtraction of vectors can be shown in diagram form by placing the starting points of the two vectors together, and then constructing an arrow from the head of the second vector in the subtraction to the head of the first vector. Algebraically, we subtract corresponding terms:

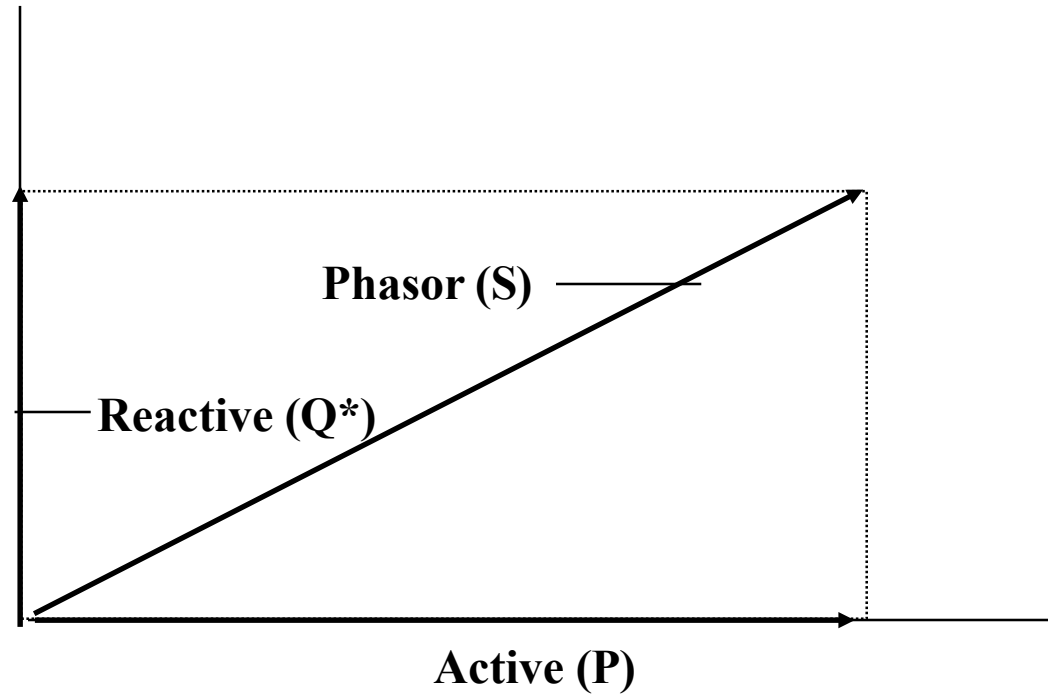Vector Subtraction  $\mathbf{a} - \mathbf{b} = \begin{bmatrix} a_x \\ a_y \end{bmatrix} - \begin{bmatrix} b_x \\ b_y \end{bmatrix} = \begin{bmatrix} a_x - b_x \\ a_y - b_y \end{bmatrix}.$



**\*Not the “Q” of Q-hour metering**




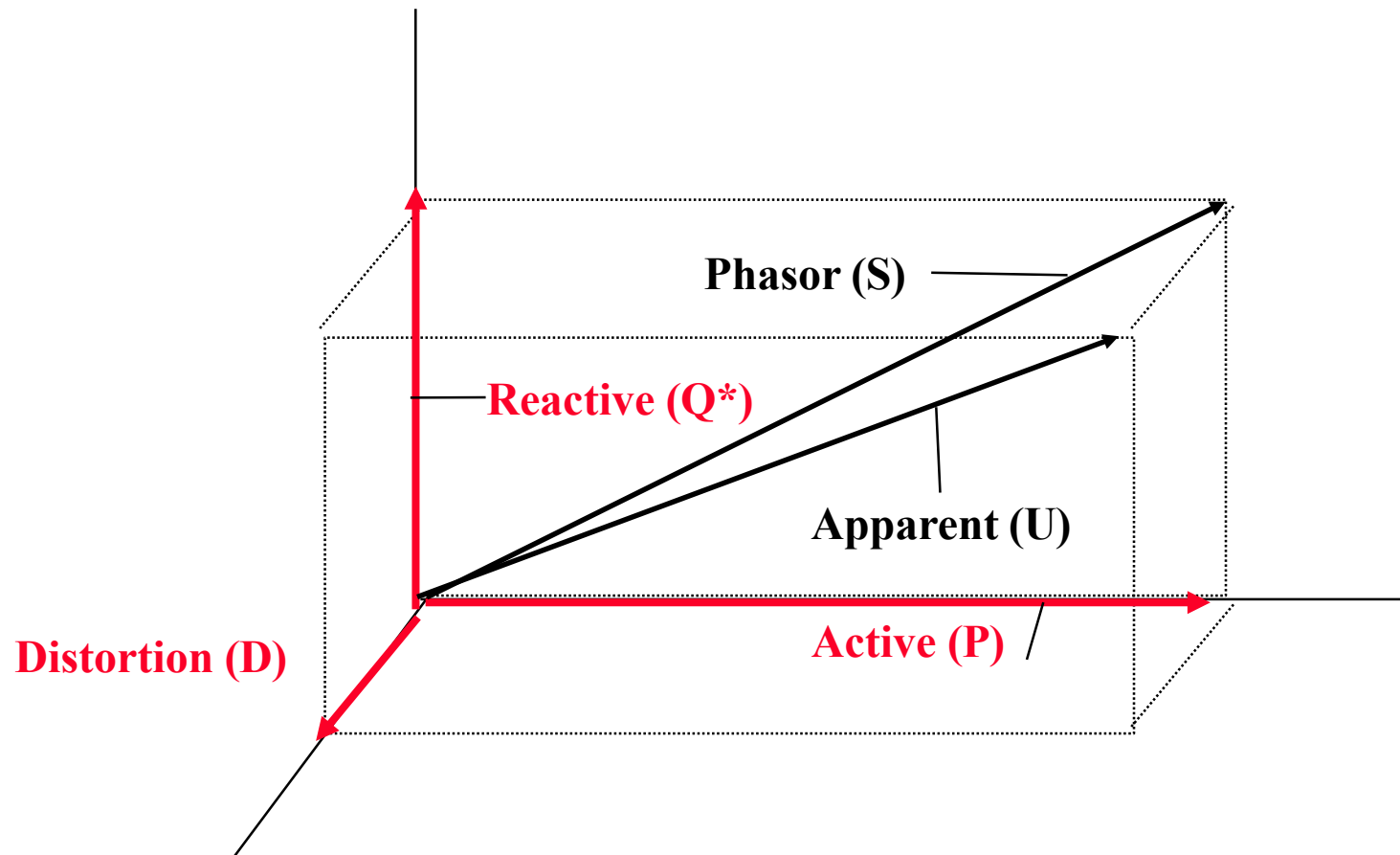

**\*Not the “Q” of Q-hour metering**

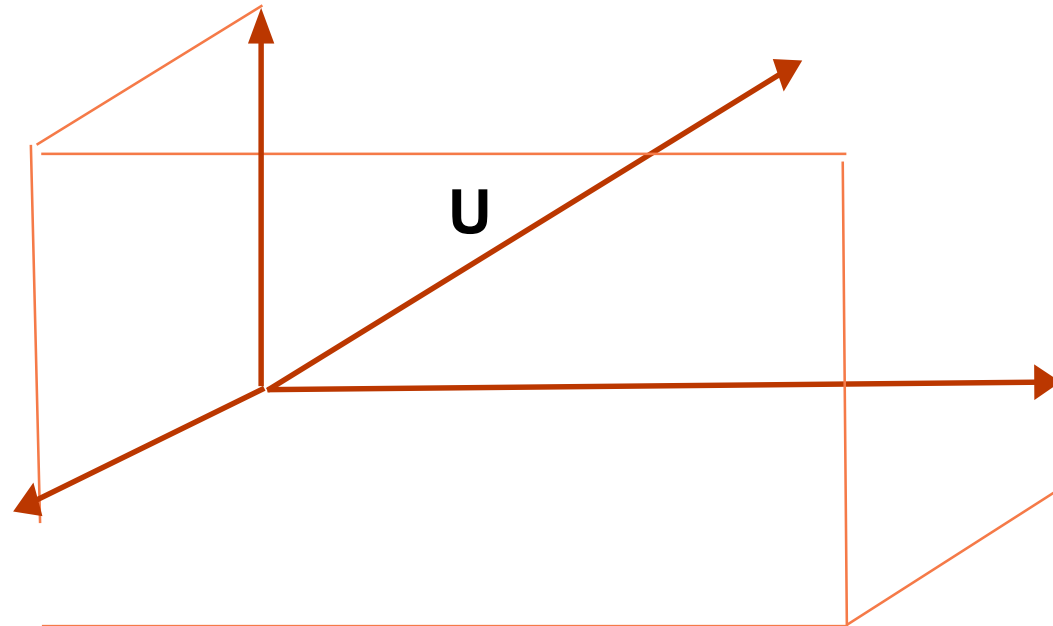
# How is 3 $\phi$ Apparent Power calculated?

- To calculate Apparent power (U), first add the components for the phases together.



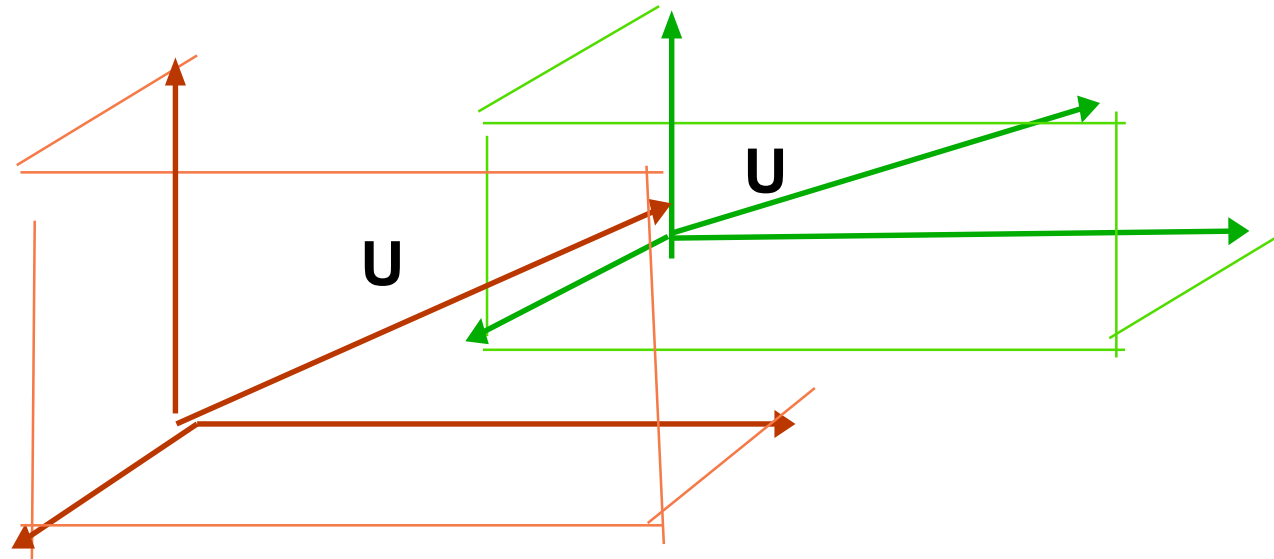
# How is 3 $\phi$ Apparent Power calculated?

- To calculate Apparent power (U), first add the components for the phases together.


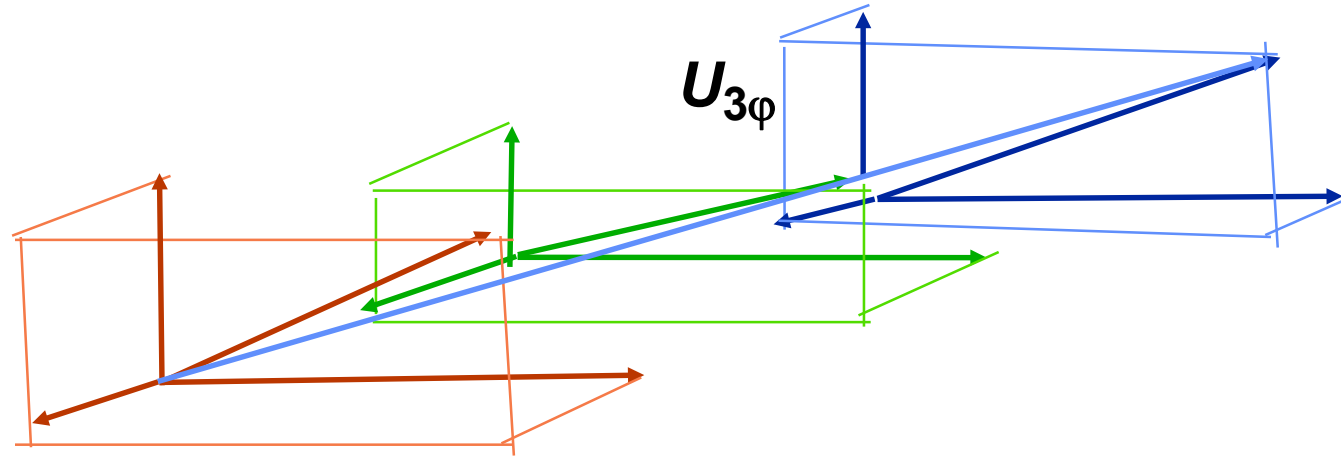
# HOW IS 3 $\phi$ APPARENT POWER CALCULATED?

- To calculate Apparent power (U), first add the components for the phases together, then solve for U.



$$U_{3\phi} = \sqrt{(P_A + P_B + P_C)^2 + (Q_A + Q_B + Q_C)^2 + (D_A + D_B + D_C)^2}$$


$$S = \sqrt{(P_A + P_B + P_C)^2 + (Q_A + Q_B + Q_C)^2}$$

$$U_{\text{(arith)}} = U_A + U_B + U_C$$
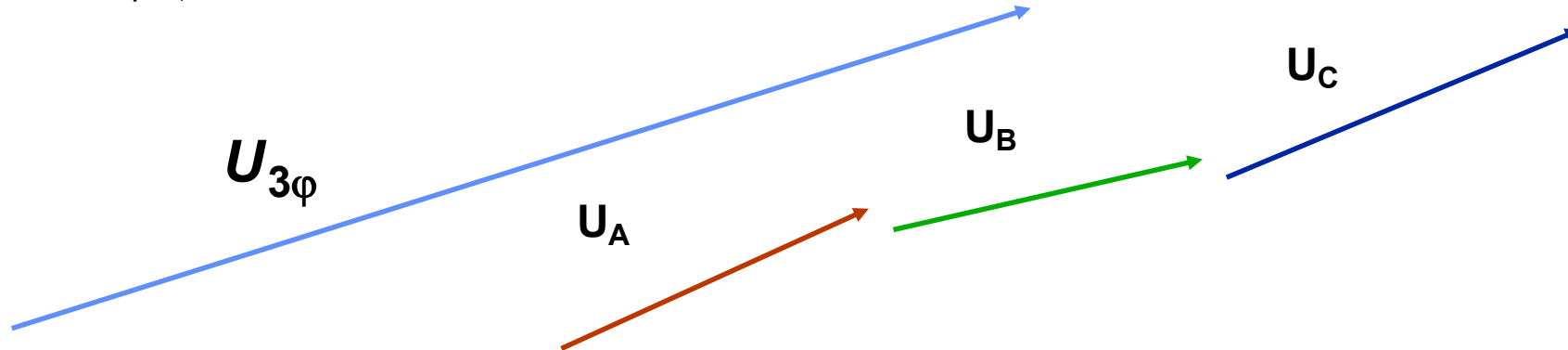
# Apparent Power vs. Arithmetic Apparent Power

- To calculate Apparent power (U), first add the components for the phases together, then solve for U.

$$U_{3\phi} = \sqrt{(P_A + P_B + P_C)^2 + (Q_A + Q_B + Q_C)^2 + (D_A + D_B + D_C)^2}$$



- To calculate *Arithmetic* Apparent power, add the Apparent power magnitudes of the three individual phases.

$$U_{Arithmetic} = U_A + U_B + U_C$$

# All KVAs are not Created Equal

Power Calculations					
<u>POWERS</u>		<u>Phase A</u>	<u>Phase B</u>	<u>Phase C</u>	<u>Total Active</u>
	(P)	3626.4	2880.0	2833.0	9339.4
Reactive	(Q)	317.3	2146.0	2112.0	4575.3
Distortion	(D)	0.0	1102.6	1784.5	2887.1
Apparent	(U)	3640	3757	3959	
PHASOR	(S)	(VA) <sub>Total</sub> = 10,400			PF = 89.8
APPARENT	(U)	(VA) <sub>Total</sub> = 10,793			PF = 86.5
ARITH.	(U <sub>arth</sub> )	(VA) <sub>Total</sub> = 11,356			PF = 82.2


- **Which “kVA” calculation method is correct?**
  - They all are “correct”, by definition.
  - Each utility needs to decide which value is appropriate for their own needs.
  - Phasor Power is what results from calculations based on traditional kWh and kvarh meter readings, using a Phase- Shifting Transformer.
  - Apparent Power provides more complete picture of “cost of service”, expected answers under all conditions.
  - Arithmetic Apparent Power may provide unexpected results (low PF, high kVA) for asymmetrical or unbalanced conditions.

<i>RMS Potential,</i>	$E_X = \sqrt{\sum_{h=1}^H E_{Xh}^2}$	<i>(Volts)</i>
<i>RMS Current,</i>	$I_X = \sqrt{\sum_{h=1}^H I_{Xh}^2}$	<i>(Amperes)</i>
<i>Apparent Power,</i>	$U_X = E_X I_X$	<i>(kVA)</i>
<i>Active Power,</i>	$P_X = \sum_{h=1}^H E_{Xh} I_{Xh} \cos(\alpha_{Xh} - \beta_{Xh})$	<i>(kW)</i>
<i>Re active Power,</i>	$Q_X = \sum_{h=1}^H E_{Xh} I_{Xh} \sin(\alpha_{Xh} - \beta_{Xh})$	<i>(k var)</i>
<i>Distortion Power,</i>	$D_X = \pm \sqrt{U_X^2 - P_X^2 - Q_X^2}$	<i>(kVA)</i>
<i>Phasor Power,</i>	$S_X = + \sqrt{P_X^2 + Q_X^2}$	<i>(kVA)</i>
<i>Fictitious Power,</i>	$F_X = + \sqrt{U_X^2 - P_X^2}$	<i>(kVA) (a.k.a." Fuzzy var s")</i>
<i>Nonreactive Power,</i>	$N_X = + \sqrt{U_X^2 - Q_X^2}$	<i>(kVA)</i>

**$E_{Xh}$  and  $I_{Xh}$  are the RMS voltage and amperage of harmonic h.  $\alpha_{Xh}$  and  $\beta_{Xh}$  are the phase angles of the voltage and current of harmonic h with respect to the reference time-frame. H is the highest harmonic ordinal.**




## Aclara kV2c Meter

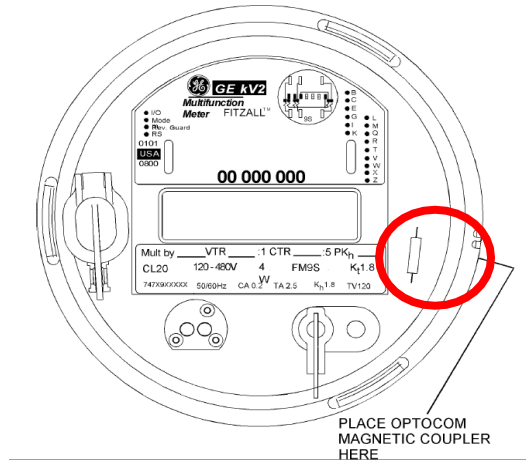


## Itron Sentinel



## Landis + Gyr S4e

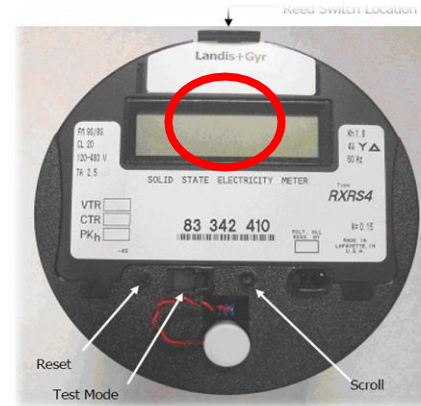

## Honeywell A3

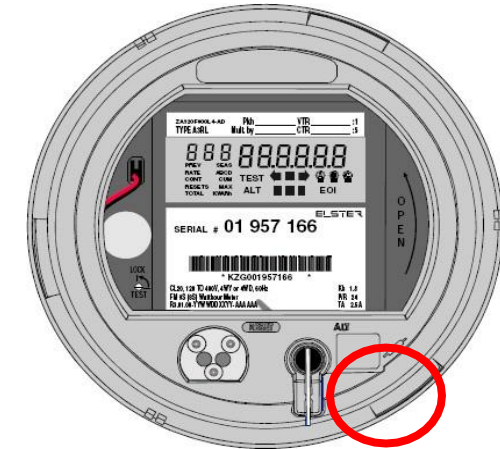

## Sensus Icon APX




# Phase Rotation & Site Measurements


## Site Measurements

Phase	Voltage	Voltage Phase	Current	Current Phase	Probe Current	Probe Phase
A	113.605	0.000°	2.901	14.345°	578.355	14.45°
B	114.364	120.147°	3.002	136.931°	599.459	137.140°
C	113.611	240.312°	2.864	256.188°	570.920	256.198°

Secondary Phasor

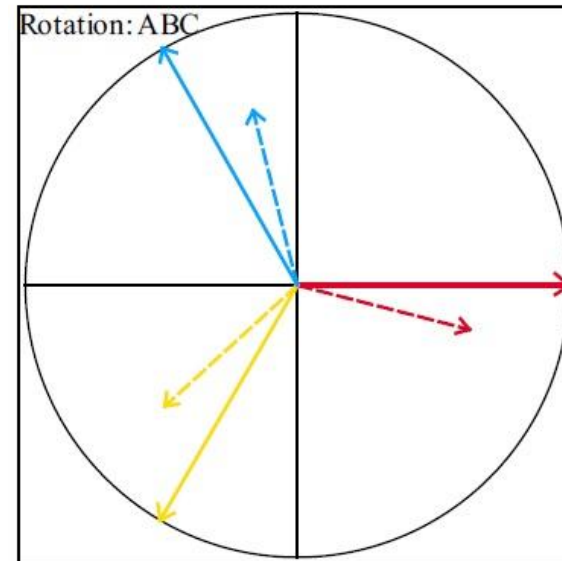

Primary Phasor

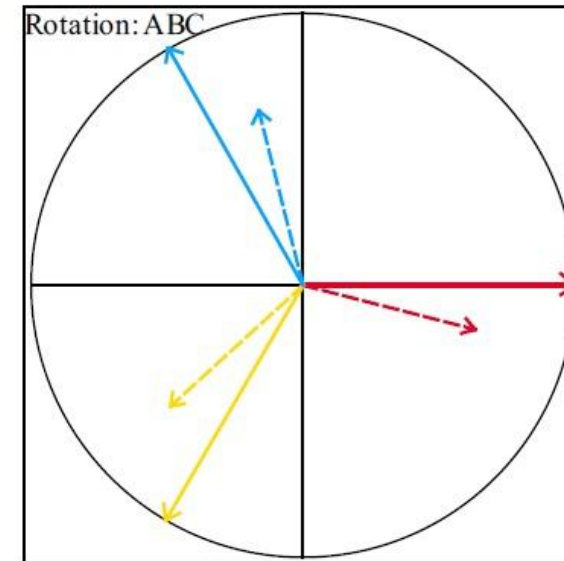

## Power

Phase	Watts	VA	VAR	Voltage THD	Current THD	Power Factor	CT Ratio
A	0.354	1.464	0.360	0.016	0.075	0.966	996.98:5
B	1.456	1.525	0.438	0.016	0.073	0.955	998.58:5
C	1.387	1.445	0.393	0.016	0.075	0.959	996.57:5

Please Take a Few  
Minutes To Provide  
Feedback About The  
Course & Instructor

Track 2 - Practical Use of Vectors in  
Electric Metering 72225 8:45AM  
Carl Chermak



**Carl Chermak**



**TESCO – The Eastern Specialty Company**

*Bristol, PA*

**215-228-0500**

This presentation can also be found under Meter Conferences and Schools on the TESCO website: [tescometering.com](http://tescometering.com)