



tescometering.com

POLYPHASE METERING 101

Prepared by Tom Lawton, TESCO
The Eastern Specialty Company

*For Mississippi State University 43rd Annual
Electric Power & Meter School
Tuesday, February 20, 2024 ♦ 8:30 AM
Meter II*




MISSISSIPPI STATE UNIVERSITY™
43RD ANNUAL ELECTRIC POWER & METERING SCHOOL



tescometering.com

TOPICS WE WILL BE COVERING

- The Basics- Differences Between Self Contained and Transformer or Instrument Rated Meter Sites
- Brief Discussion of polyphase metering for self-contained and transformer rated applications
- Transformer Rated Meter Forms
- Test Switches and CT's
- Blondel's Theorem and why this matters to us in metering
- Meter Accuracy Testing in the Field
- Checking the Health of your CT's and PT's
- Site Verification and not just meter testing

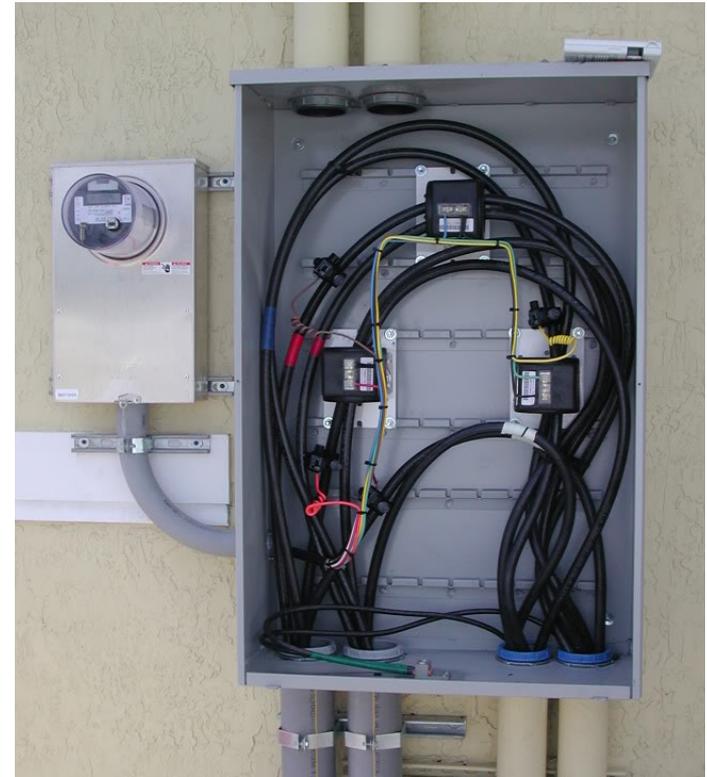




tescometering.com

SELF CONTAINED METERING

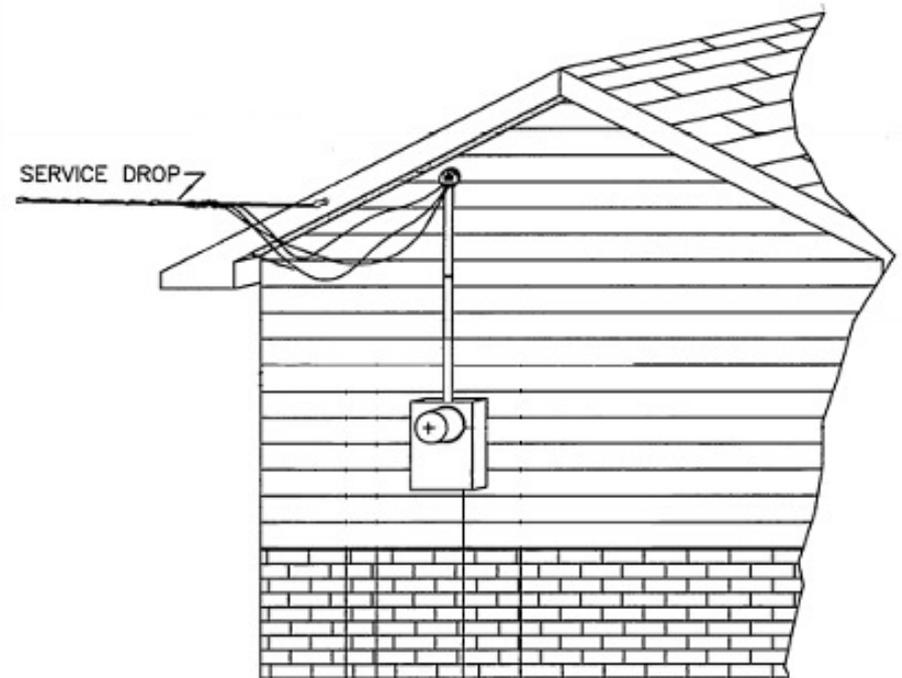- Typically found in residential metering
- Meters are capable of handling the direct incoming amperage
- Meter is connected directly to the load being measured
- Meter is part of the circuit
- When the meter is removed from the socket, power to the customer is interrupted






tescometering.com

TRANSFORMER RATED METERING

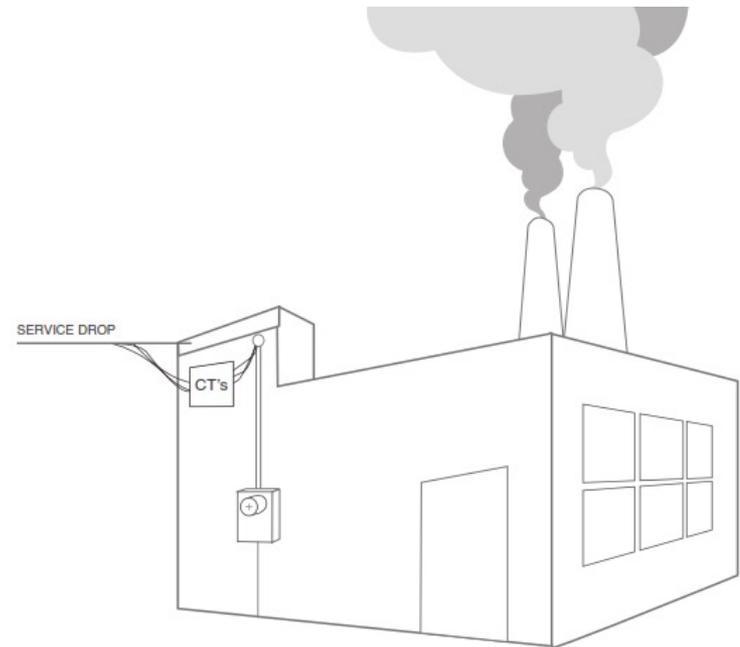
- Meter measures scaled down representation of the load.
- Scaling is accomplished by the use of external current transformers (CTs) and sometimes voltage transformers or PTs).
- The meter is NOT part of the circuit
- When the meter is removed from the socket, power to the customer is not affected.






tescometering.com

1-PHASE AND 3-PHASE POWER

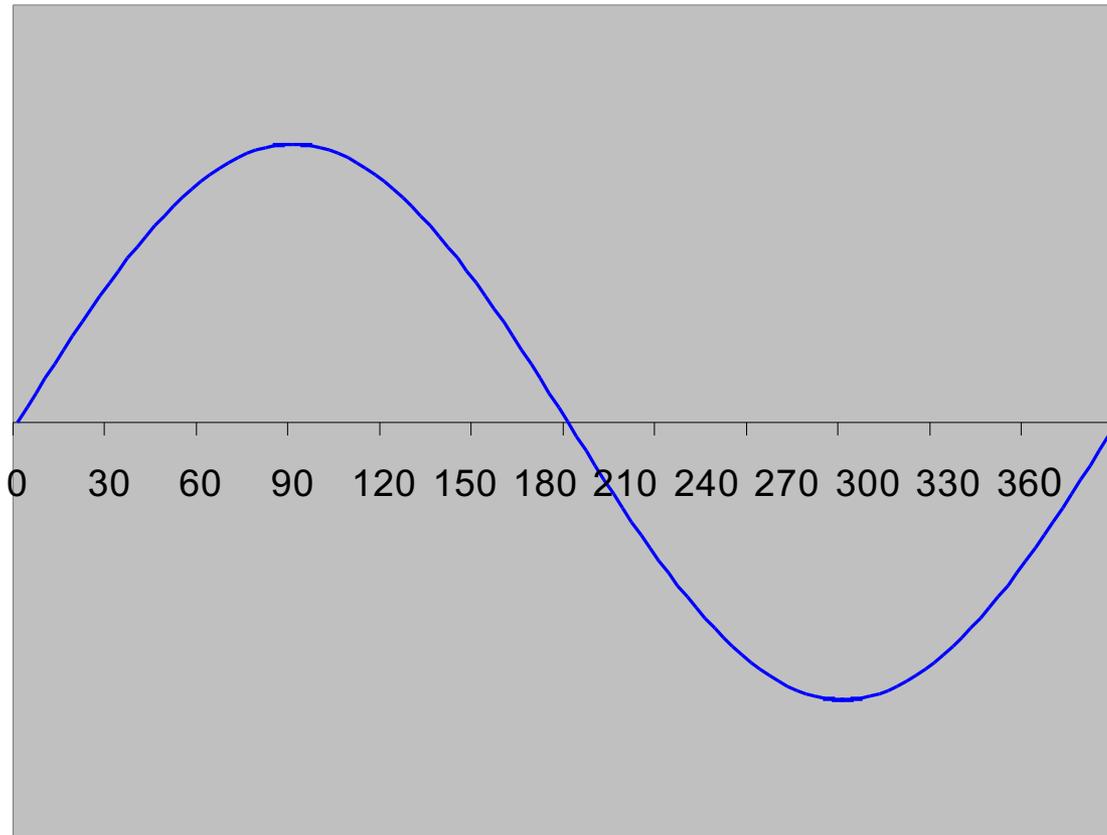

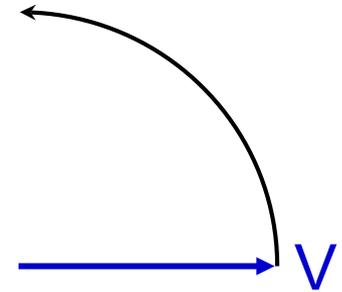
$$\text{Voltage} = V_{\max} \text{ sine } \alpha$$






tescometering.com

1-PHASE AND 3-PHASE POWER

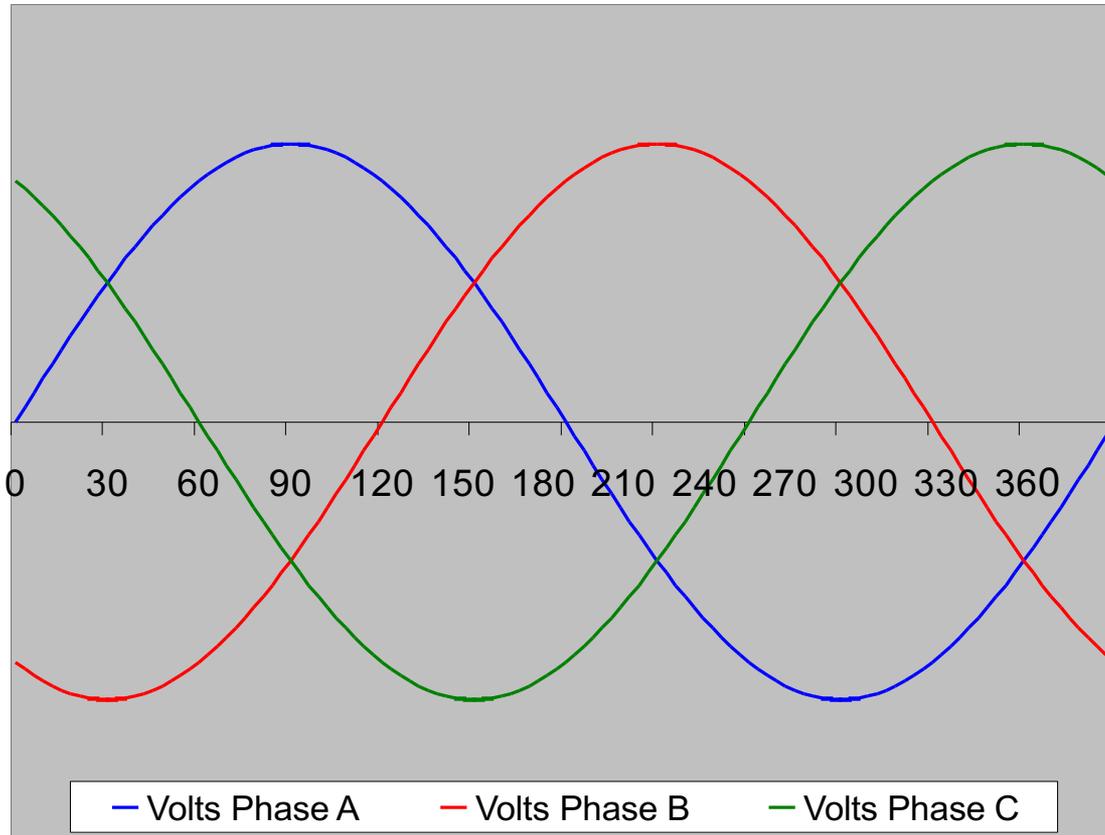


Forward Rotation, ABC

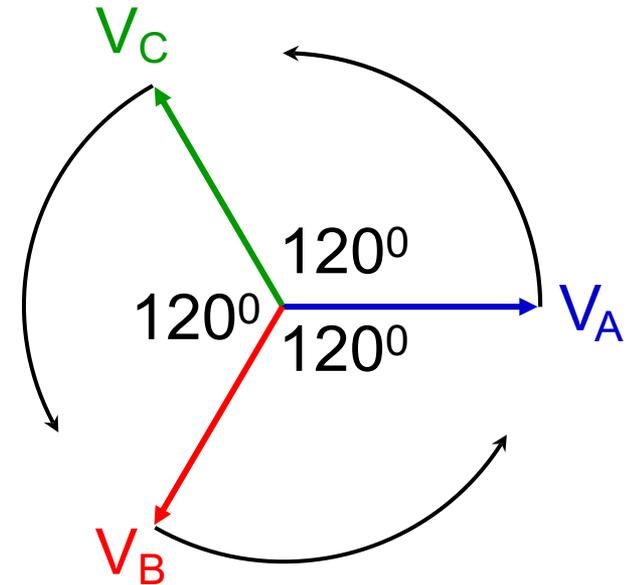

THE NEED FOR 3-PHASE POWER

Single-phase motors provide a pulsating torque to a mechanical load. Loads which require more than 10 horsepower generally also require the steadier torque of a 3-phase motor.

3 PHASE INDUCTION MOTOR

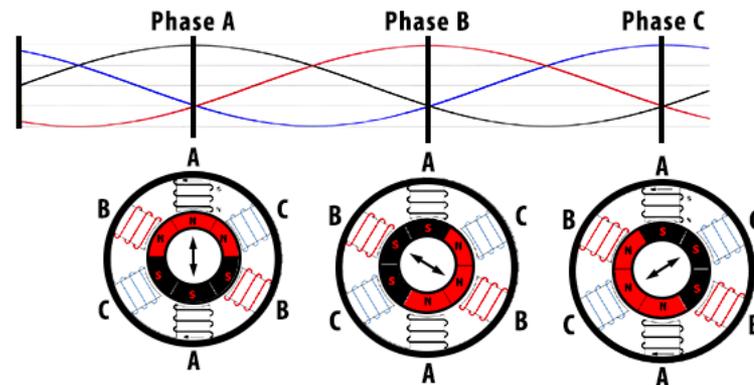




tescometering.com

BENEFITS OF 3-PHASE POWER

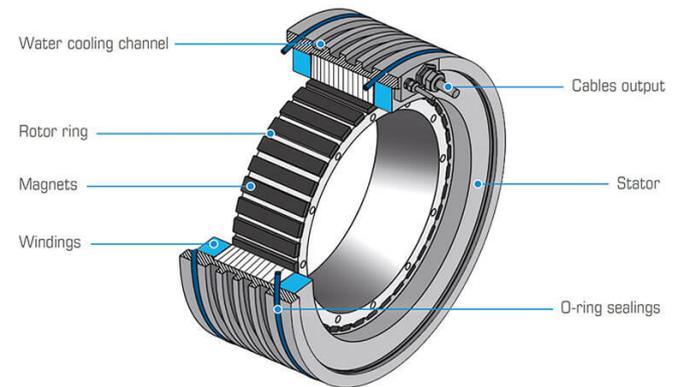- ✓ Steadier motor torque
- ✓ Less vibration in machinery
- ✓ Greater mechanical efficiency
- ✓ Better voltage regulation
- ✓ Lower heat losses
- ✓ Lighter weight conductors






tescometering.com

TRANSFORMER RATED - THE BASIC COMPONENTS


9S Meter Installation with 400:5 CT's

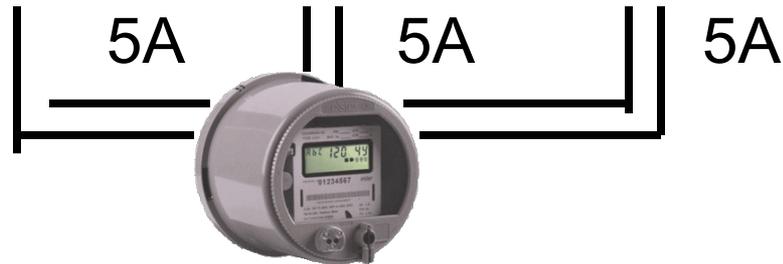



TYPICAL CONNECTIONS

tescometering.com

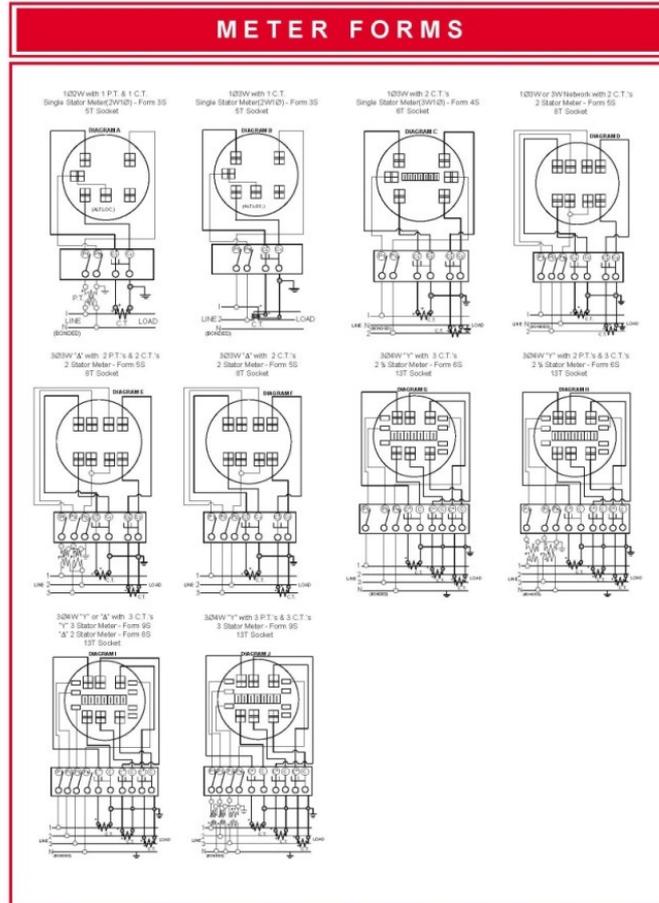


Typical Connections for Common Transformer (Instrument) Rated Meter Forms

Note: See Chapter 4 of the Power Measurement Handbook for more detailed form by form information



SELECTING THE RIGHT METER FORM

- Select the meter form based on the source, not the load.
 - The “service type” is not always obvious.
 - Loads other than the “known” load can be connected and may be unmetered.
- Meter form numbers describe certain meter characteristics not the service or application
- Consider that *ground* can be a current carrying conductor when applying Blondel’s Theorem.
- Understand the operation of present day, polyphase solid state meters and how they may be used to advantage

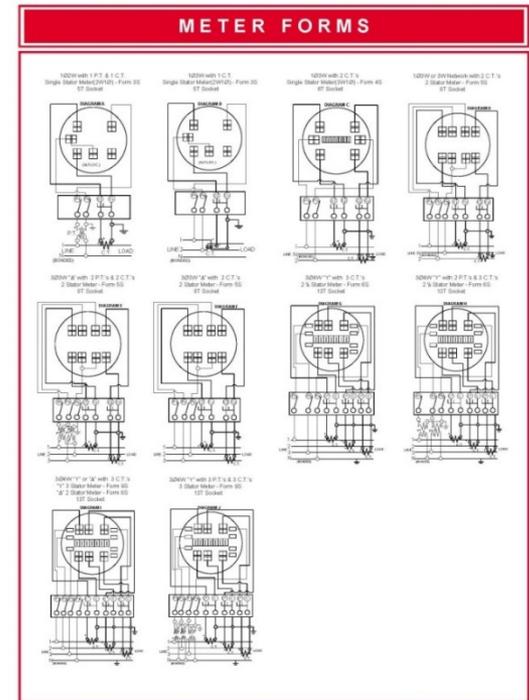



tescometering.com

THREE PHASE POWER: BLONDEL'S THEOREM

The theory of polyphase watt-hour metering was first set forth on a scientific basis in 1893 by Andre E. Blondel, engineer and mathematician. His theorem applies to the measurement of real power in a polyphase system of any number of wires. The theorem is as follows:


- If energy is supplied to any system of conductors through N wires, the total power in the system is given by the algebraic sum of the readings of N wattmeters, so arranged that each of the N wires contains one current coil, the corresponding voltage coil being connected between that wire and some common point. If this common point is on one of the N wires, the measurement may be made by the use of $N-1$ wattmeters.





THREE PHASE POWER: BLONDEL'S THEOREM

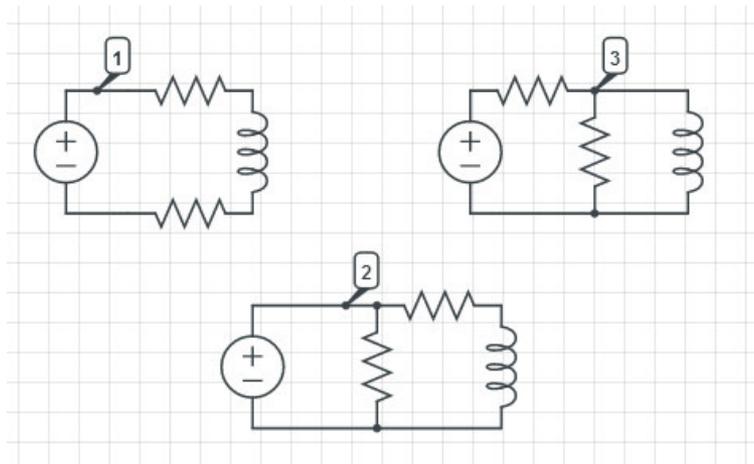- Simply – We can measure the power in a N wire system by measuring the power in N-1 conductors.
- For example, in a 4-wire, 3-phase system we need to measure the power in 3 circuits.





THREE PHASE POWER: BLONDEL'S THEOREM

- If a meter installation meets Blondel's Theorem then we will get accurate power measurements under all circumstances.
- If a metering system does not meet Blondel's Theorem then we will only get accurate measurements if certain assumptions are met.


YOU ALWAYS JUST
ASSUME THAT
EVERYONE WANTS
WHATEVER YOU
WANT.






tescometering.com

BLONDEL'S THEOREM

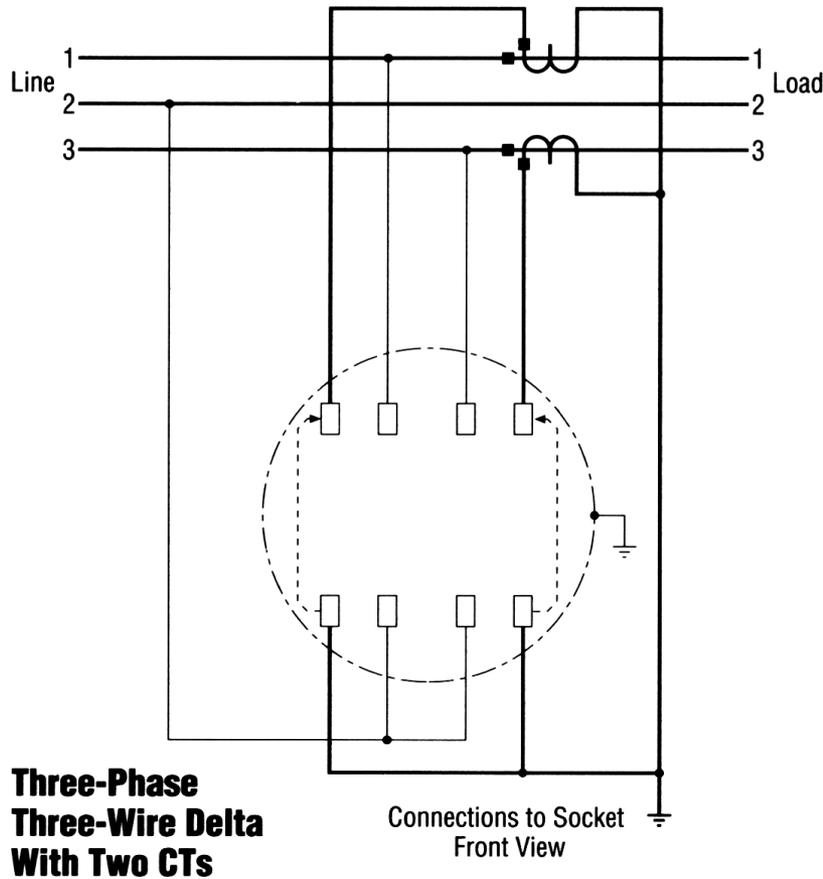

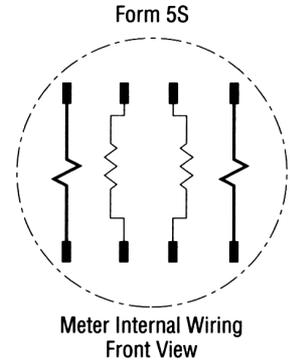**Three-Phase
Three-Wire Delta
With Two CTs**



- Three wires
- Two voltage measurements with one side common to Line 2
- Current measurements on lines 1 & 3.



This satisfies Blondel's Theorem.





tescometering.com

BLONDEL'S THEOREM

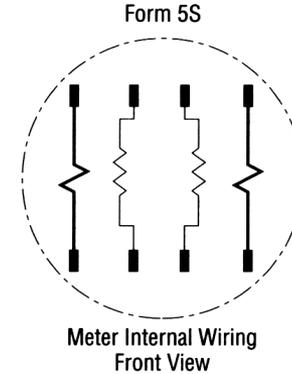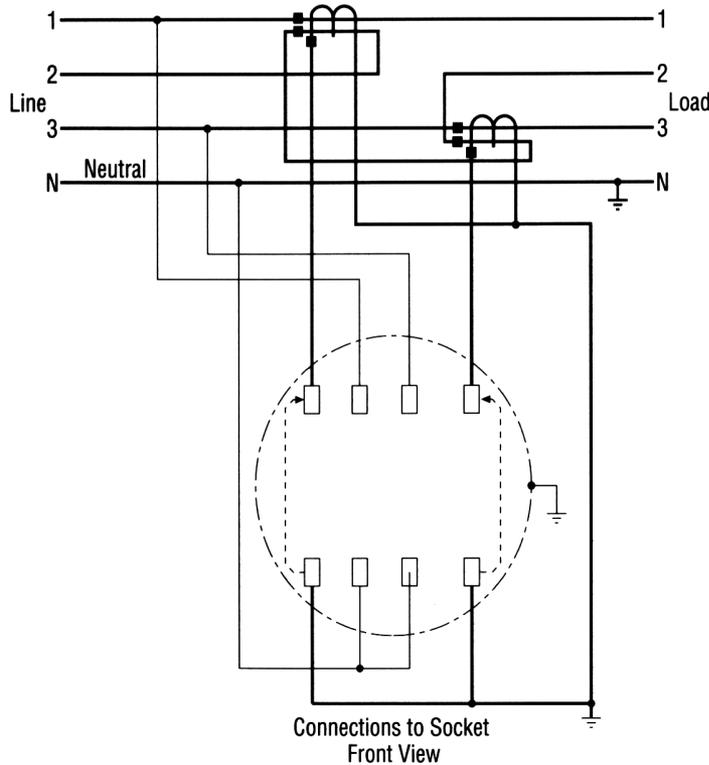

- Four wires
- Two voltage measurements to neutral
- Current measurements on lines 1 & 3.
How about line 2?

This DOES NOT satisfy Blondel's Theorem.

**Three-Phase
Four-Wire Wye
With Two Equal-Ratio CTs**



- In the previous example:
 - What are the “ASSUMPTIONS”?
 - When do we get errors?
- What would the “Right Answer” be?



$$P_{sys} = V_a I_a \cos(\theta_a) + V_b I_b \cos(\theta_b) + V_c I_c \cos(\theta_c)$$

- What did we measure?

$$P_{sys} = V_a [I_a \cos(\theta_a) - I_b \cos(\theta_b)] + V_c [I_c \cos(\theta_c) - I_b \cos(\theta_b)]$$

BLONDEL'S THEOREM

- Phase B power would be:
 - $P = V_b I_b \cos\theta$
- But we aren't measuring V_b
- What we are measuring is:
 - $I_b V_a \cos(60 - \theta) + I_b V_c \cos(60 + \theta)$
- $\cos(\alpha + \beta) = \cos(\alpha)\cos(\beta) - \sin(\alpha)\sin(\beta)$
- $\cos(\alpha - \beta) = \cos(\alpha)\cos(\beta) + \sin(\alpha)\sin(\beta)$
- So



BLONDEL'S THEOREM

- $P_b = I_b V_a \cos(60 - \theta) + I_b V_c \cos(60 + \theta)$
- Applying the trig identity
 - $I_b V_a (\cos(60)\cos(\theta) + \sin(60)\sin(\theta))$
 - $I_b V_c (\cos(60)\cos(\theta) - \sin(60)\sin(\theta))$
 - $I_b (V_a + V_c) 0.5 \cos(\theta) + I_b (V_c - V_a) 0.866 \sin(\theta)$
- Assuming
 - Assume $V_b = V_a = V_c$
 - And, they are exactly 120° apart
- $P_b = I_b (2V_b) (0.5 \cos \theta) = I_b V_b \cos \theta$



**HAPPINESS IS
ASSUMING THE
WORLD IS LINEAR**



tescometering.com


BLONDEL'S THEOREM

- If $V_a \neq V_b \neq V_c$ then the error is
- %Error =
$$-I_b \left\{ \frac{(V_a + V_c)}{(2V_b)} - (V_a - V_c) \right.$$
$$\left. 0.866 \sin(\theta) / (V_b \cos(\theta)) \right\}$$

How big is this in reality? If

$V_a=117, V_b=120, V_c=119, PF=1$ then $E=-1.67\%$

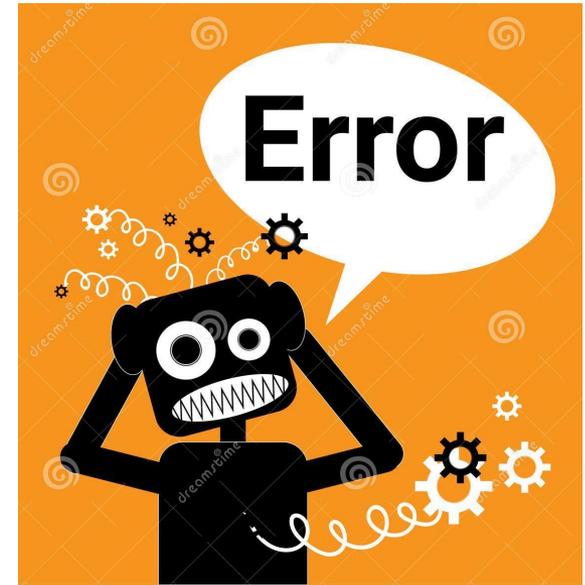$V_a=117, V_b=116, V_c=119, PF=.866$ then $E=-1.67\%$





tescometering.com

BLONDEL'S THEOREM


Power Measurements Handbook

Condition	% V	% I	Phase A				Phase B				non-Blondel
	I _{mb}	I _{mb}	V	φ _{van}	I	φ _{ian}	V	φ _{vbn}	I	φ _{ibn}	% Err
All balanced	0	0	120	0	100	0	120	180	100	180	0.00%
Unbalanced voltages PF=1	18%	0%	108	0	100	0	132	180	100	180	0.00%
Unbalanced current PF=1	0%	18%	120	0	90	0	120	180	110	180	0.00%
Unbalanced V&I PF=1	5%	18%	117	0	90	0	123	180	110	180	-0.25%
Unbalanced V&I PF=1	8%	18%	110	0	90	0	120	180	110	180	-0.43%
Unbalanced V&I PF=1	8%	50%	110	0	50	0	120	180	100	180	-1.43%
Unbalanced V&I PF=1	18%	40%	108	0	75	0	132	180	125	180	-2.44%
Unbalanced voltages PF≠1 P _{Fa} = P _{Fb}	18%	0%	108	0	100	30	132	180	100	210	0.00%
Unbalanced current PF≠1 P _{Fa} = P _{Fb}	0%	18%	120	0	90	30	120	180	110	210	0.00%
Unbalanced V&I PF≠1 P _{Fa} = P _{Fb}	18%	18%	108	0	90	30	132	180	110	210	-0.99%
Unbalanced V&I PF≠1 P _{Fa} = P _{Fb}	18%	40%	108	0	75	30	132	180	125	210	-2.44%
Unbalanced voltages PF≠1 P _{Fa} ≠ P _{Fb}	18%	0%	108	0	100	60	132	180	100	210	-2.61%
Unbalanced current PF≠1 P _{Fa} ≠ P _{Fb}	0%	18%	120	0	90	60	120	180	110	210	0.00%
Unbalanced V&I PF≠1 P _{Fa} ≠ P _{Fb}	18%	18%	108	0	90	60	132	180	110	210	-3.46%
Unbalanced V&I PF≠1 P _{Fa} ≠ P _{Fb}	18%	40%	108	0	75	60	132	180	125	210	-4.63%




tescometering.com

NETWORK SERVICE & LOADS

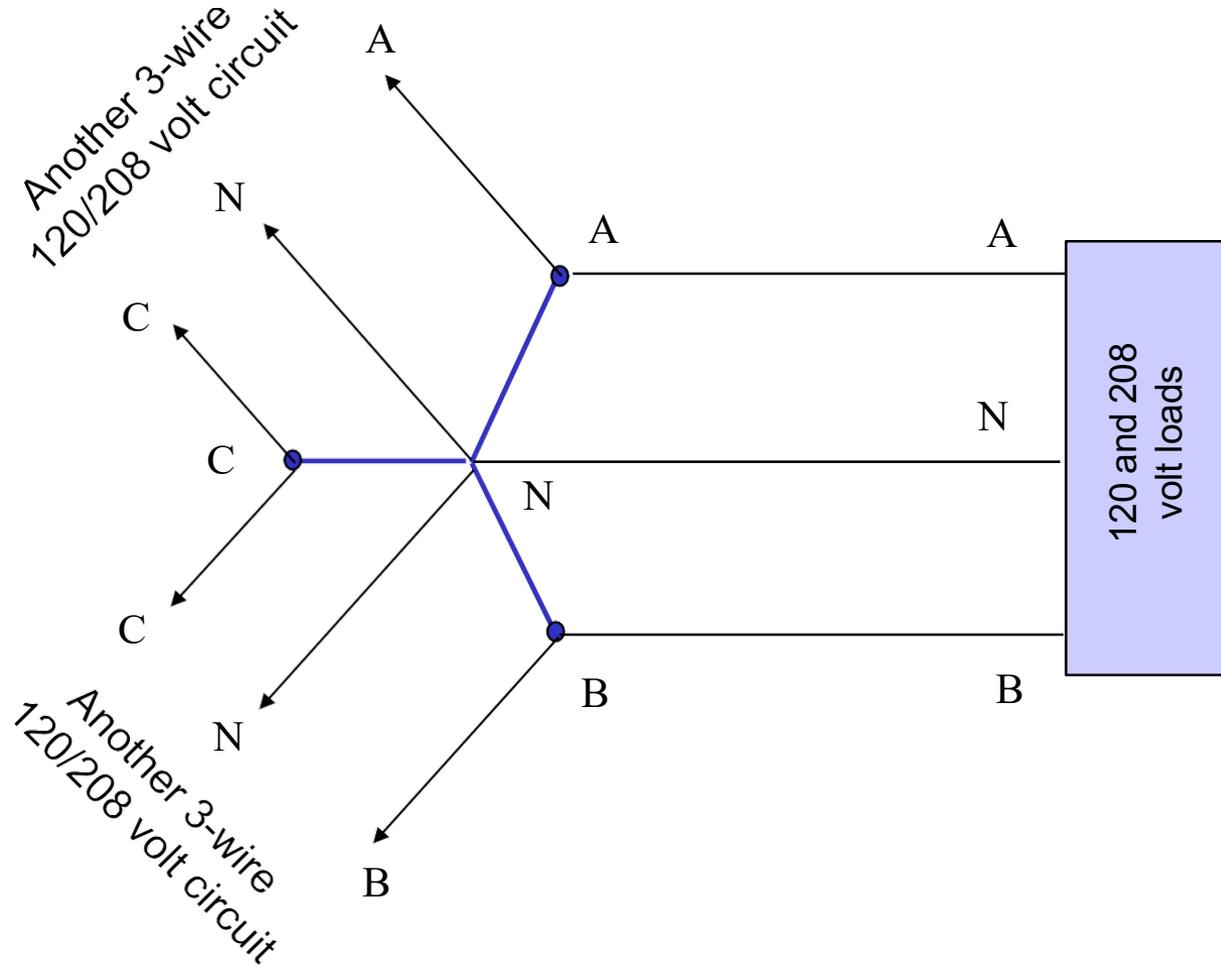


3-WIRE DELTA SERVICE & LOADS

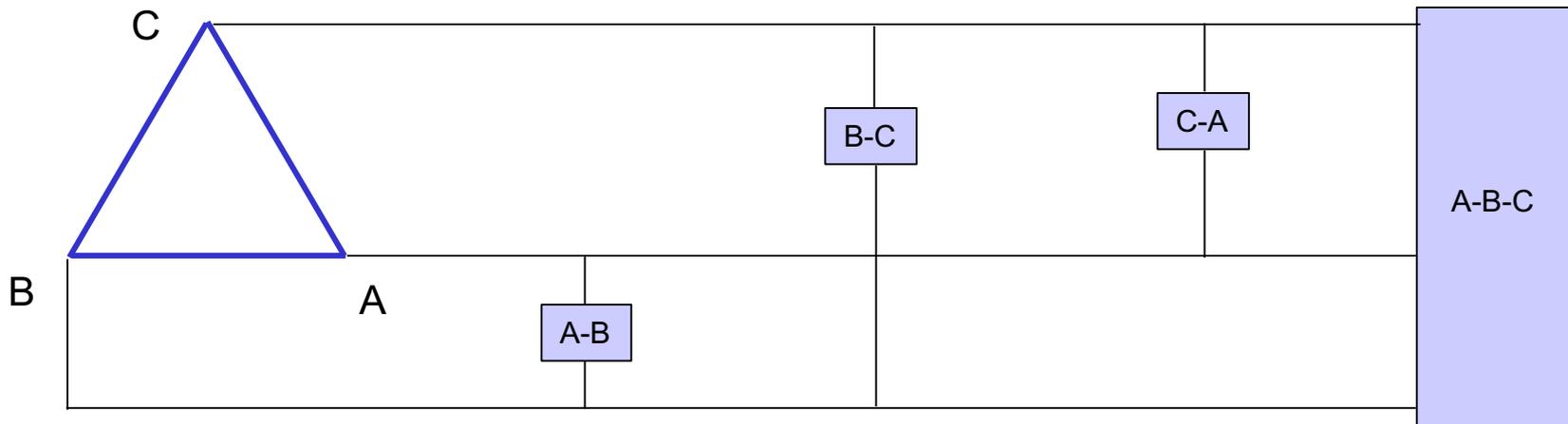

Need to meter single phase line-line loads, as well as three phase loads. Form 12 for Self Contained and Form for Transformer Rated. You need a two element meter only. Network metering is less expensive than Transformer rated. If you need to be transformer rated you save by using a single bushing VT and one less PT since you are only two element (typically do not meter B element).



4-WIRE DELTA SERVICE & LOADS

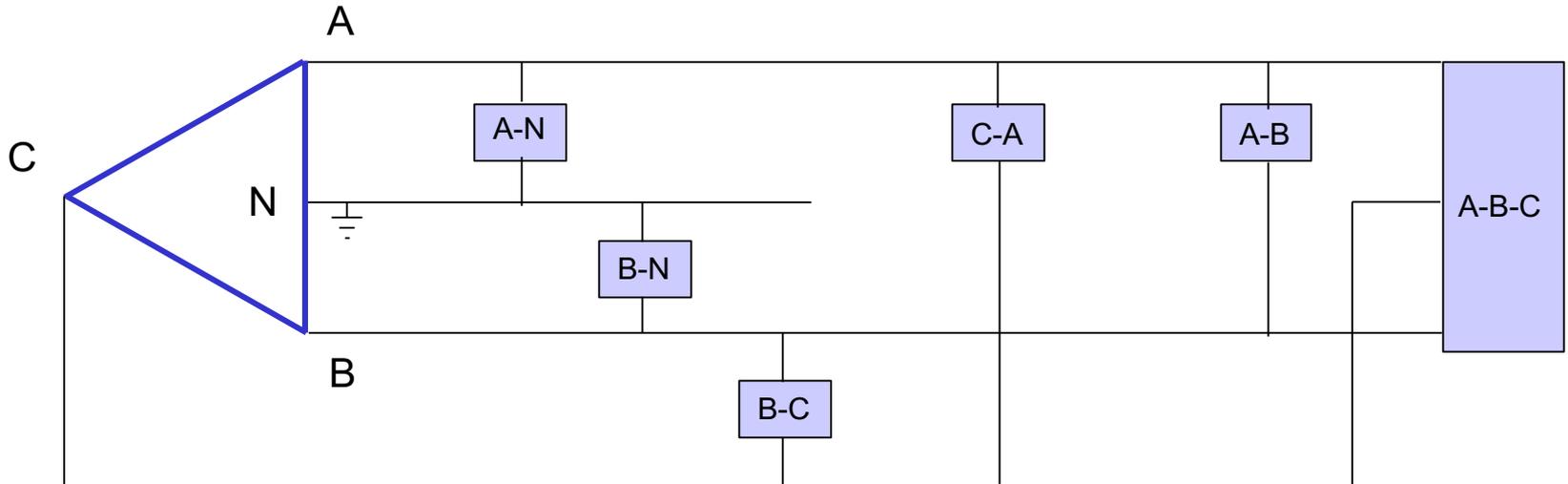


Need to meter single phase line-neutral and line-line loads, as well as three phase loads. For self contained a Form 16 network meter and Transformer rated a 9S meter. We need to be Blondel Compliant and use a three-element meter. Note: For electro-mechanicals common practice was a Form 15S which was not Blondel compliant. Similarly, a 5S is not Blondel compliant for these services.



tescometering.com

4-WIRE WYE SERVICE & LOADS

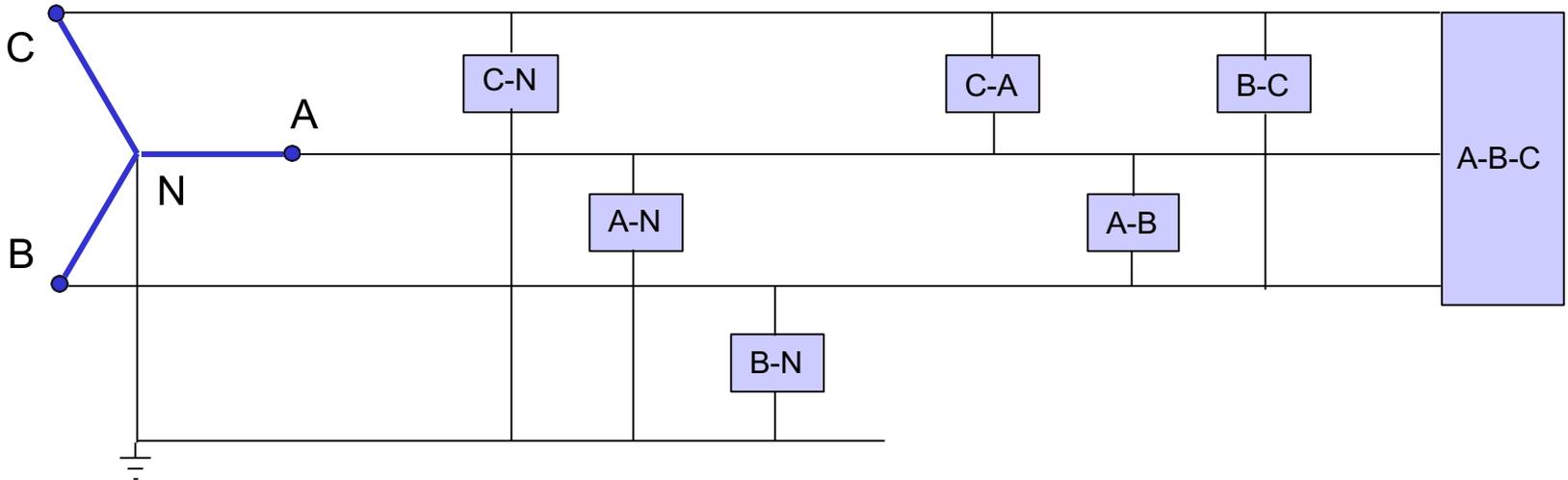

Need to meter single phase line-neutral and line-line loads, as well as three phase loads. Use a Form 16 Network meter and a Form 9S Current Meter.





tescometering.com

METER ACCURACY TESTING

Meter Accuracy Testing in a Nutshell



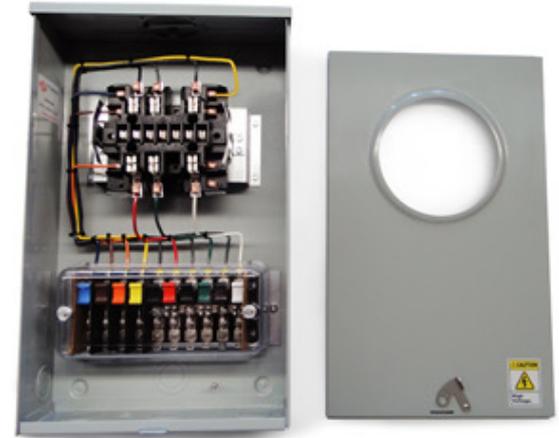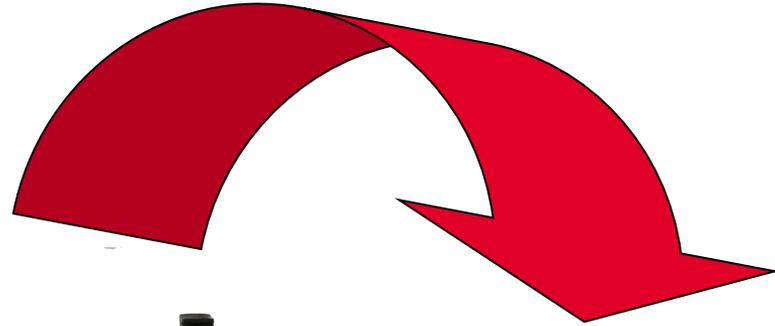- ✓ Full Load
- ✓ Light Load
- ✓ Power Factor






tescometering.com

THE IMPORTANCE OF CT TESTING IN THE FIELD

- One transformer in three wired backwards will give the customer a bill of 1/3rd the actual bill.
- One broken wire to a single transformer will give the customer a bill of 2/3rd the actual bill
- One dual ratio transformer inappropriately marked in the billing system as 400:5 instead of 800:5 provides a bill that is 1/2 of the actual bill. And the inverse will give a bill double of what should have been sent. Both are lose-lose situations for the utility.



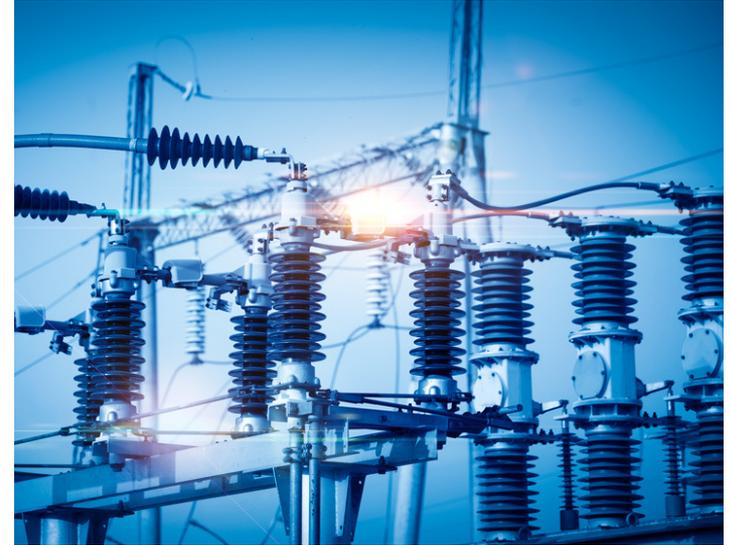- Cross Phasing (wiring errors)
- Loose or Corroded Connections
- CT Mounted Backwards
- CT's with Shorted Turns
- Wrong Selection of Dual Ratio CT
- Detect Magnetized CT's
- Burden Failure in Secondary Circuit
- Open or Shorted Secondary
- Mislabeled CT's
- Ensures all Shorting Blocks have been Removed





tescometering.com


TESTING AT TRANSFORMER RATED SITES

- ✓ Meter Accuracy
- ✓ Full Load
- ✓ Light Load
- ✓ Power Factor
- ✓ CT Health
- ✓ Burden Testing
- ✓ Ratio Testing
- ✓ Admittance Testing
- ✓ Site Verification





Functionality with Burden Present on the Secondary Loop

PHASE A

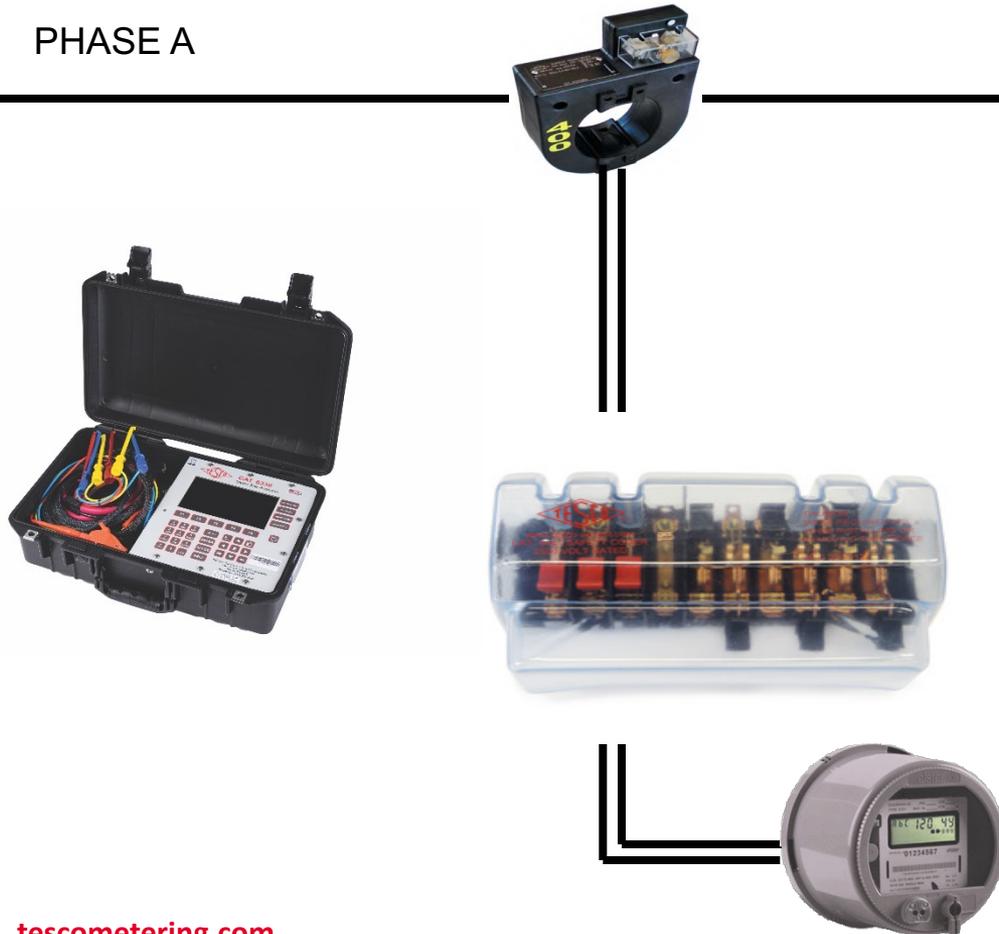

- Some burden will always be present – junctions, meter coils, test switches, cables, etc.
- CT's must be able to maintain an accurate ratio with burden on the secondary.
- Admittance testing?

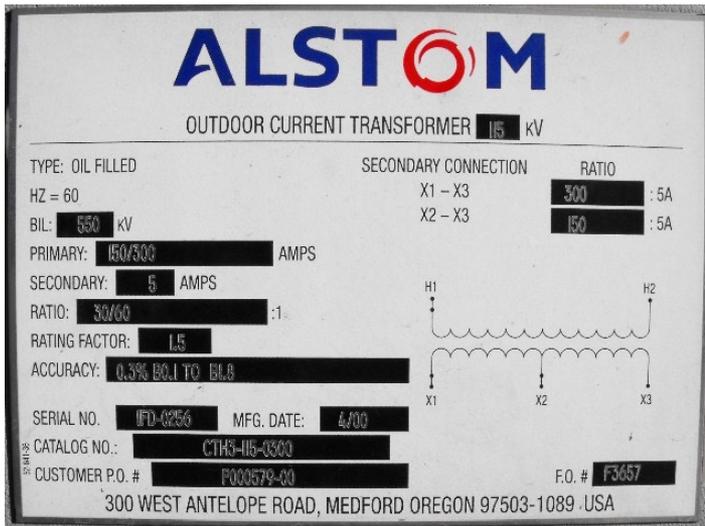
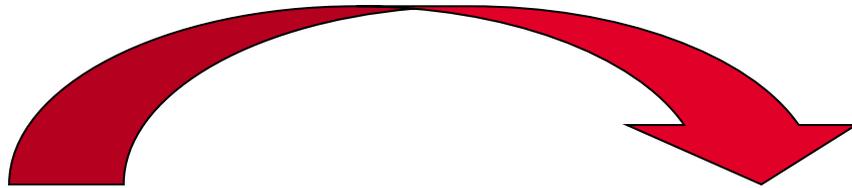
Functionality with Burden Present on the Secondary Loop



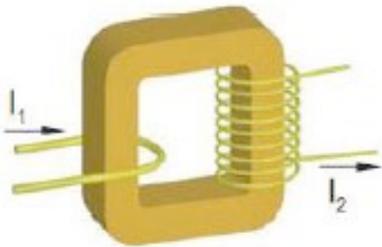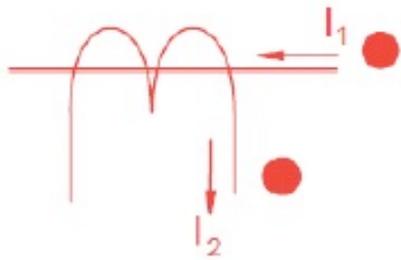Example Burden Spec:
0.3% @ B0.1, B0.2, B0.5
or


There should be less than the 0.3% change in secondary current from initial ("0" burden) reading, when up to 0.5 Ohms of burden is applied

FUNDAMENTALS OF POLYPHASE FIELD METER TESTING AND SITE VERIFICATION (CONT)




$$I_1 \times N_1 = I_2 \times N_2$$

Ideal. No losses

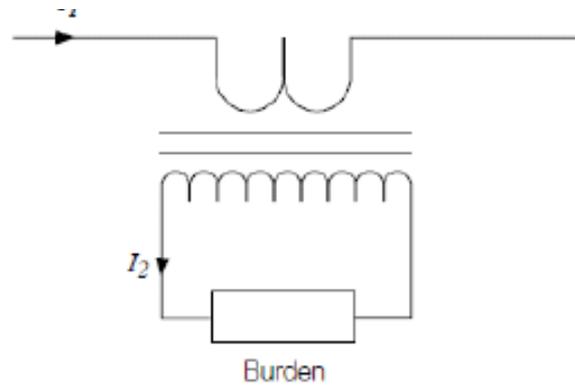

$$I_2 = \frac{N_1}{N_2} \times I_1$$

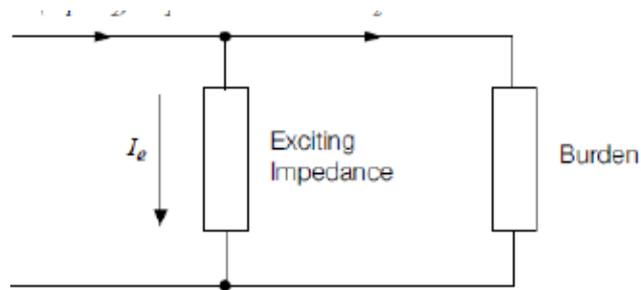

$$I_2 = \frac{N_1}{N_2} \times I_1 - I_e$$

Real, with core losses




FUNDAMENTALS OF POLYPHASE FIELD METER TESTING AND SITE VERIFICATION (CONT)

Functionality with Burden Present on the Secondary Loop

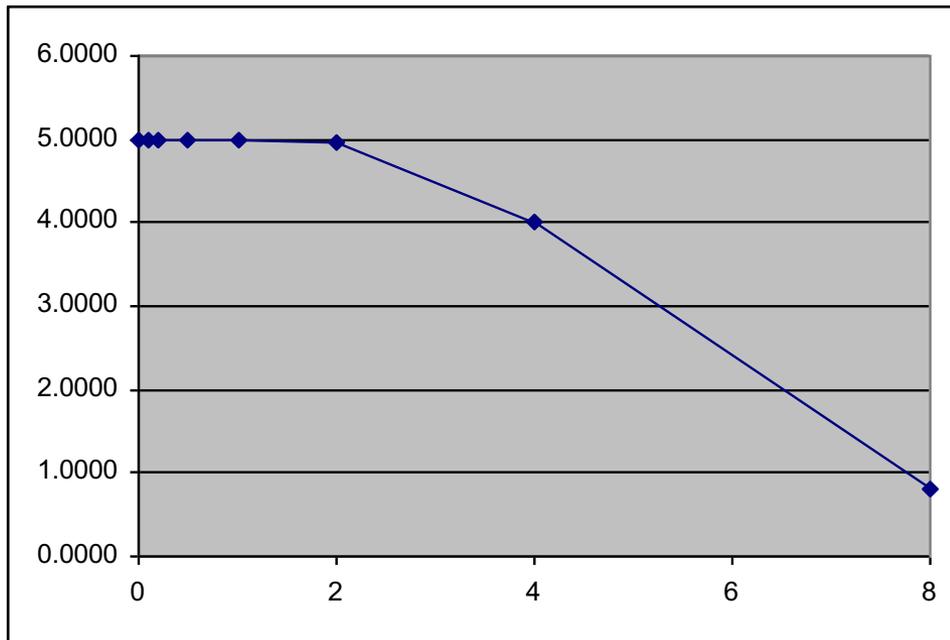
0.3% @ B0.1, B0.2, B0.5

Initial Reading = 5Amps
 $0.3\% \times 5A = 0.015A$
 $5A - 0.015 = 4.985A$



Burden	Reading
0	5.0000
0.1	4.9999
0.2	4.9950
0.5	4.9900
1	4.9800
2	4.9500
4	4.0000
8	0.8000

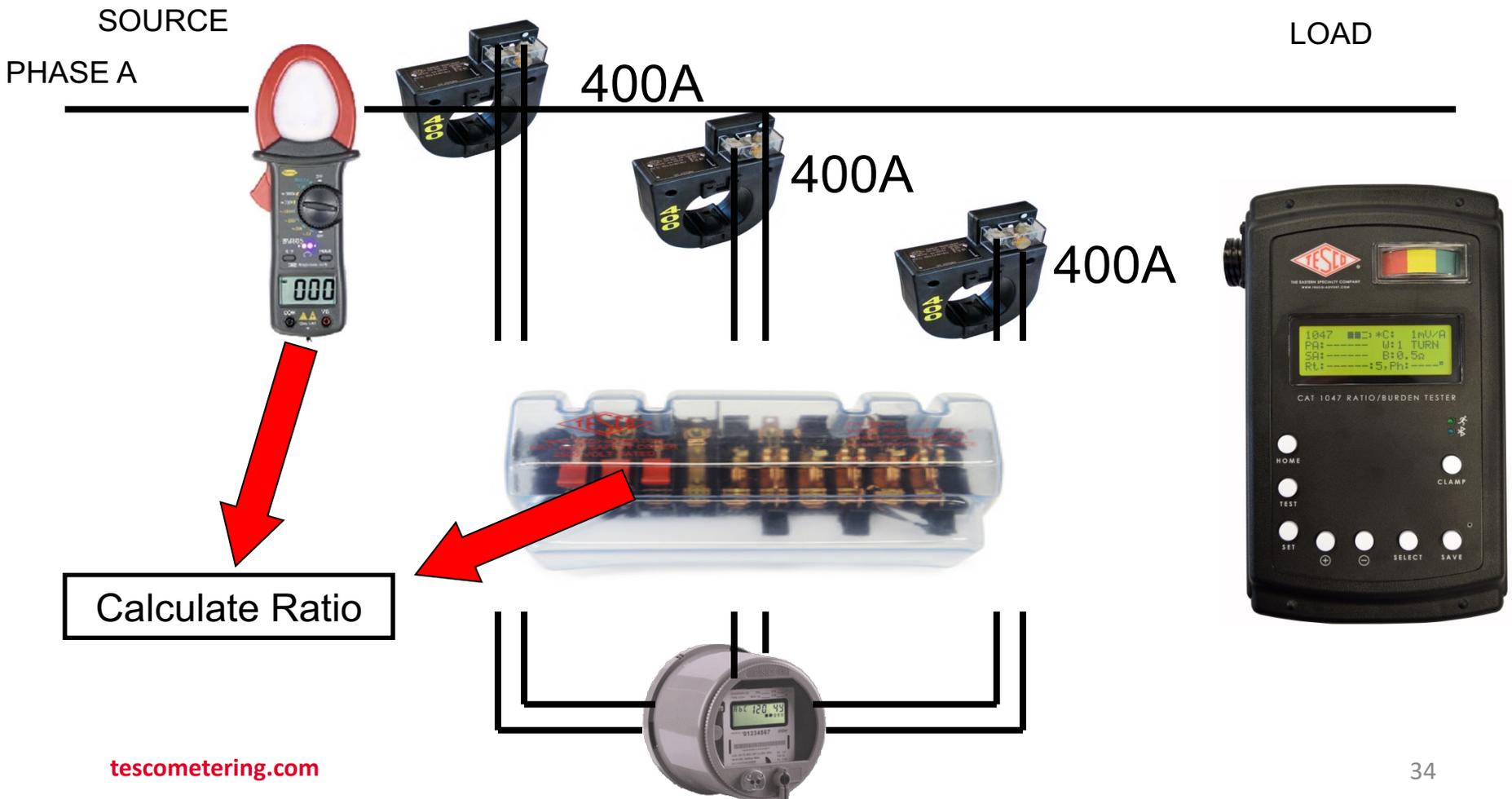Ratio of Primary Current to Secondary Current





QUESTIONS AND DISCUSSION



Tom Lawton

President

tom.lawton@tescometering.com

TESCO – The Eastern Specialty Company

Bristol, PA

215.228.0500

This presentation can also be found under Meter Conferences and Schools on the TESCO website: tescometering.com

ISO 9001:2015 Certified Quality Company
ISO 17025:2017 Accredited Laboratory