

TESCO METERING

PRINCIPLES OF POLYPHASE METERING

44th Annual Mississippi Power and Meter School

Tuesday February 11, 2025 - 8:30 AM

Tom Lawton



MISSISSIPPI STATE UNIVERSITY™
44TH ANNUAL ELECTRIC POWER & METERING SCHOOL

THANK YOU MISSISSIPPI STATE & THE SEC!



Jalen Carter (Defensive Tackle) – University of Georgia
Jordan Davis (Defensive Tackle) – University of Georgia
Nakobe Dean (Linebacker) – University of Georgia
Kelee Ringo (Cornerback) – University of Georgia
Lewis Cine (Safety) – University of Georgia

Jalen Hurts (Quarterback) – University of Alabama
Landon Dickerson (Guard) – University of Alabama
DeVonta Smith (Wide Receiver) – University of Alabama
A.J. Brown (Wide Receiver) – University of Mississippi (Ole Miss)
Darius Slay Jr. (Cornerback) – Mississippi State University

Haason Reddick (Linebacker) – University of Tennessee
Sydney Brown (Safety) – University of Florida
Oren Burks (Linebacker) – Vanderbilt University
Grant Calcaterra (Tight End) – University of Oklahoma
Parris Campbell (Wide Receiver) – University of Florida




Darius Slay, Jr.

TOPICS WE WILL BE COVERING

- The Basics- Differences Between Self Contained and Transformer or Instrument Rated Meter Sites
- Brief Discussion of polyphase metering for self-contained and transformer rated applications
- Transformer Rated Meter Forms
- Test Switches and CT's
- Blondel's Theorem and why this matters to us in metering
- Meter Accuracy Testing in the Field
- Checking the Health of your CT's and PT's
- Site Verification and not just meter testing




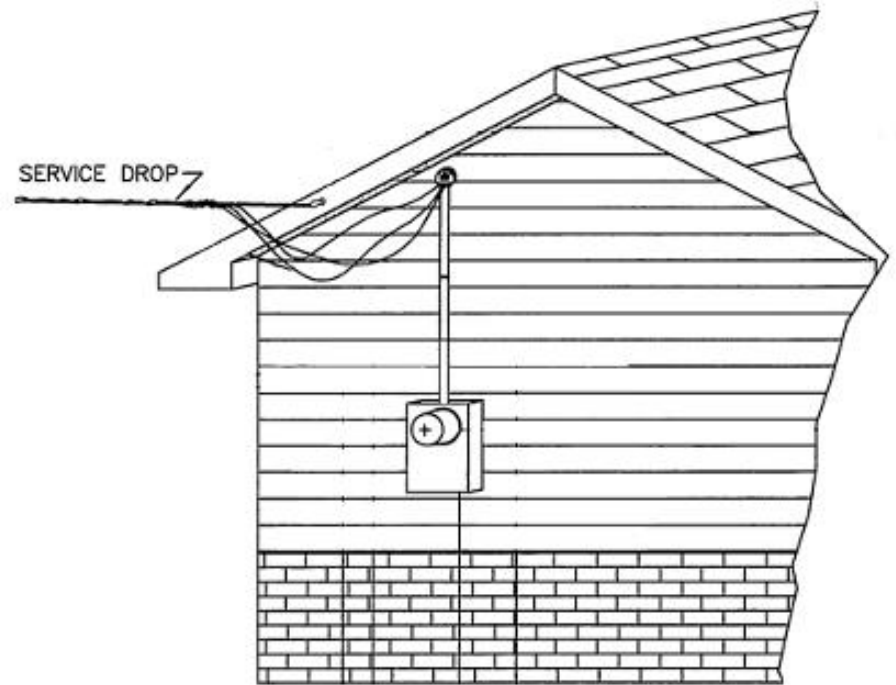- Typically found in residential metering
- Meters are capable of handling the direct incoming amperage
- Meter is connected directly to the load being measured
- Meter is part of the circuit
- When the meter is removed from the socket, power to the customer is interrupted





TRANSFORMER RATED METERING

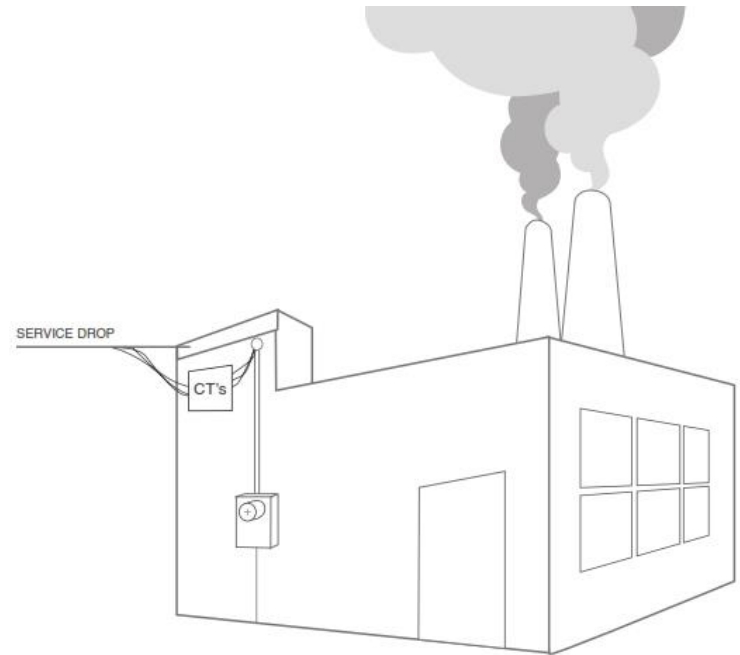- Meter measures scaled down representation of the load.
- Scaling is accomplished by the use of external current transformers (CTs) and sometimes voltage transformers or PTs).
- The meter is NOT part of the circuit
- When the meter is removed from the socket, power to the customer is not affected.




1-PHASE AND 3-PHASE POWER

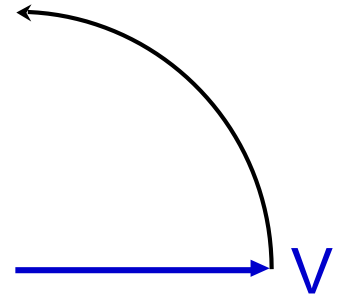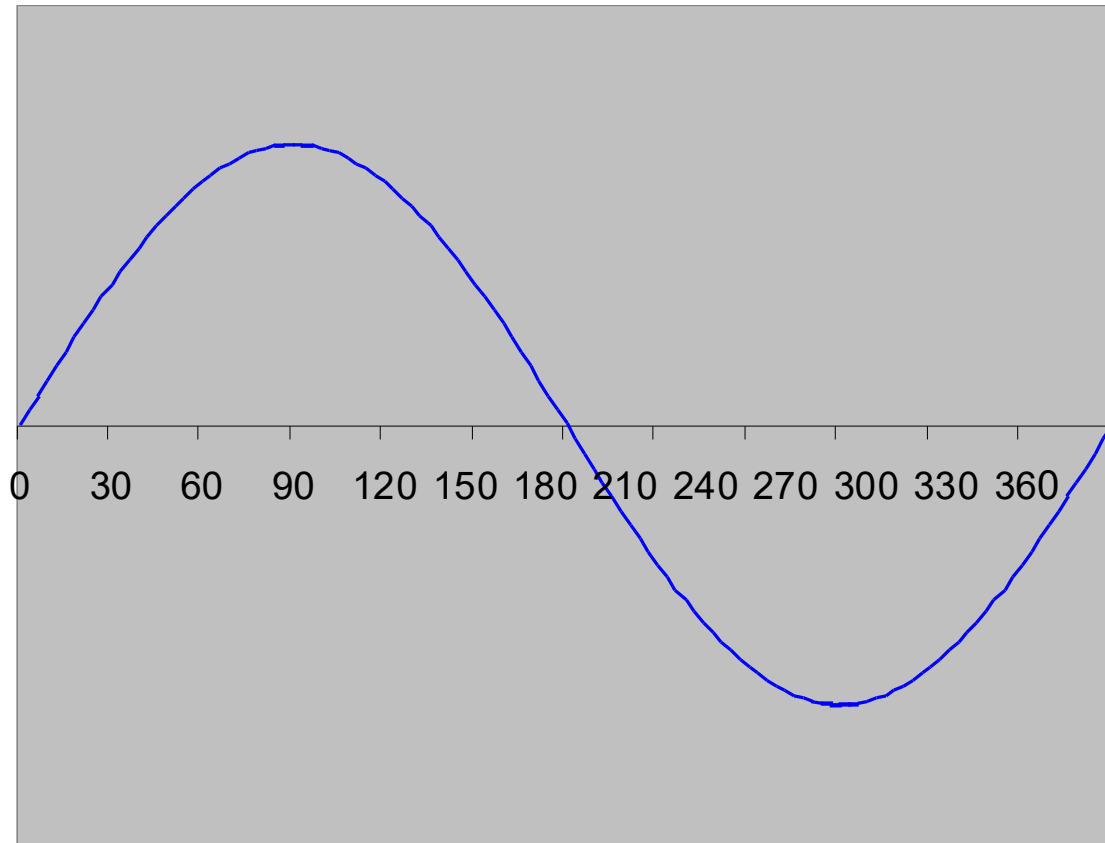


$$\text{Voltage} = V_{\max} \sin \alpha$$

1-PHASE AND 3-PHASE POWER

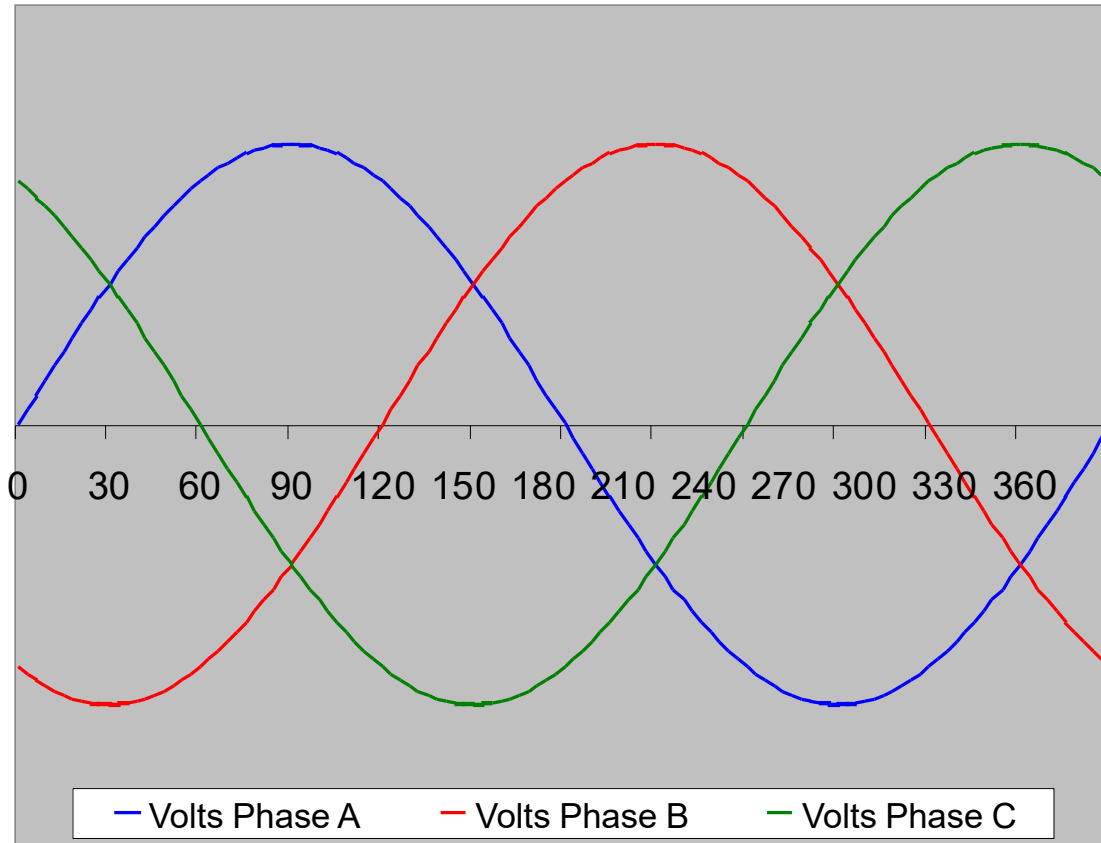


Forward Rotation, ABC

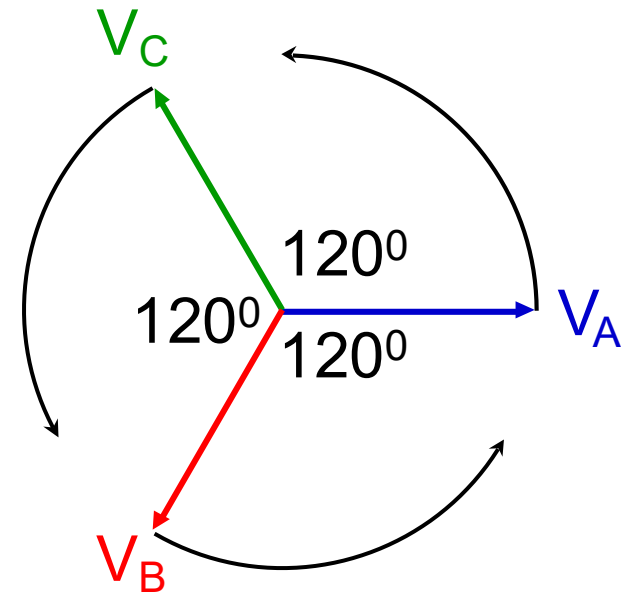


THE NEED FOR 3-PHASE POWER

Single-phase motors provide a pulsating torque to a mechanical load. Loads which require more than 10 horsepower generally also require the steadier torque of a 3-phase motor.

3 PHASE INDUCTION MOTOR


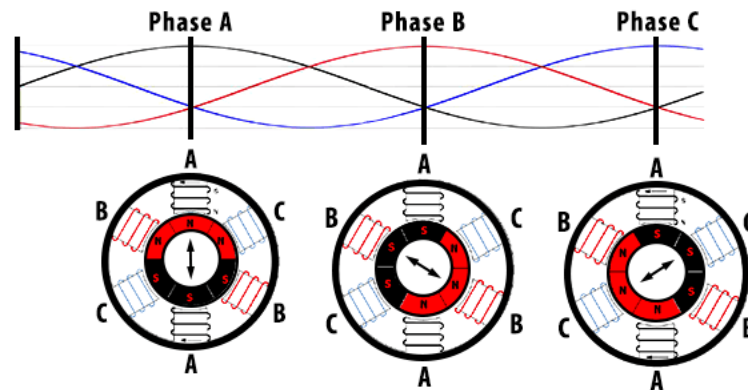


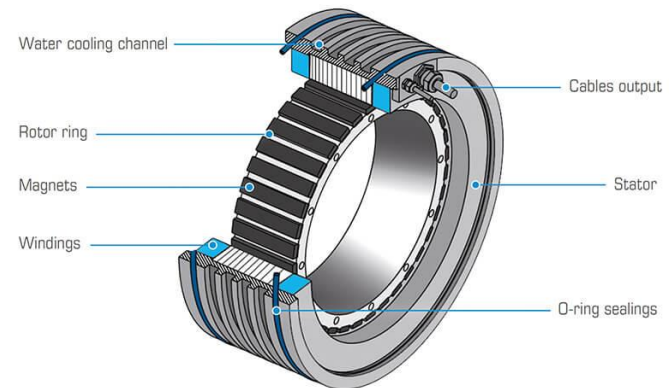
- ✓ Steadier motor torque
- ✓ Less vibration in machinery
- ✓ Greater mechanical efficiency
- ✓ Better voltage regulation
- ✓ Lower heat losses
- ✓ Lighter weight conductors



TRANSFORMER RATED - THE BASIC COMPONENT

9S Meter Installation with 400:5 CT's

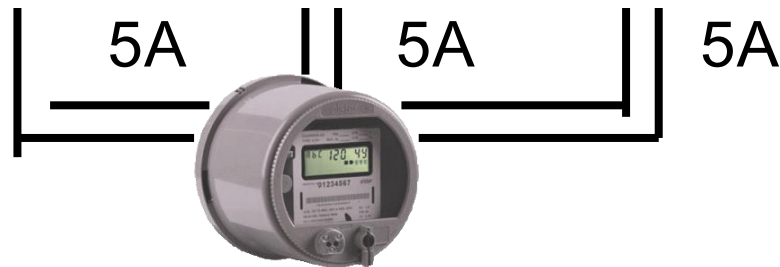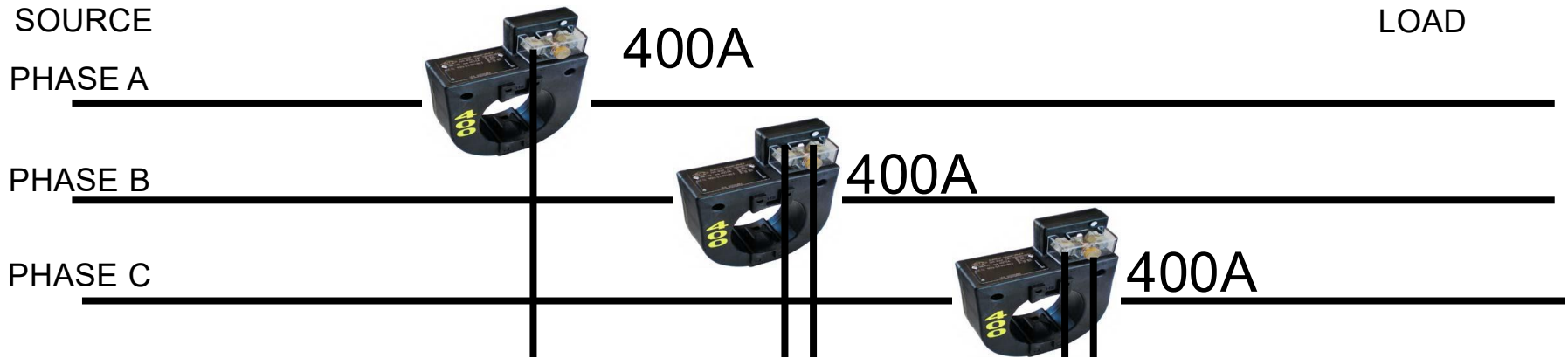

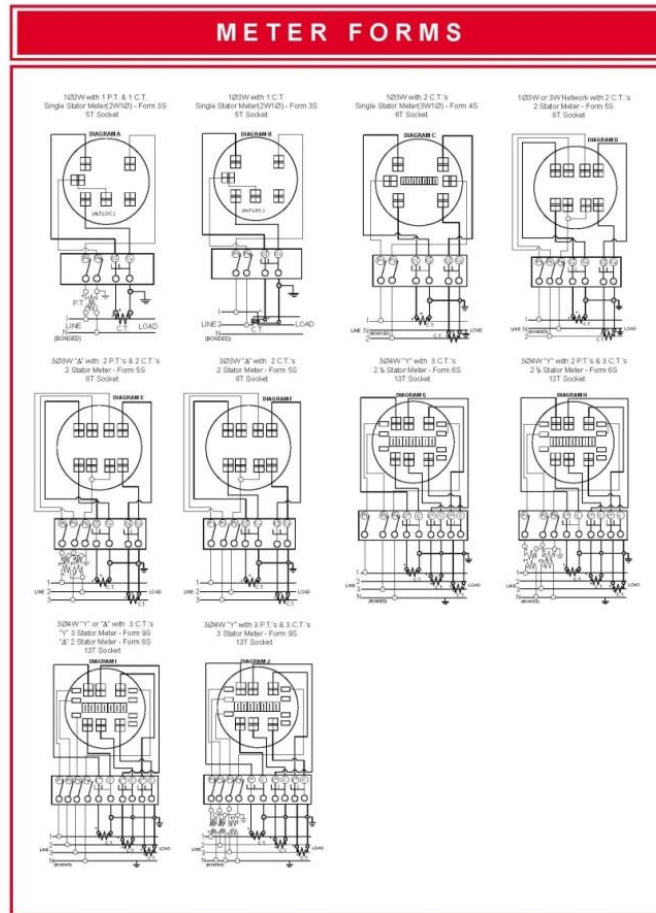


Typical Connections for Common Transformer (Instrument) Rated Meter Forms

Note: See Chapter 4 of the Power Measurement Handbook for more detailed form by form information

SELECTING THE RIGHT METER FORM

- Select the meter form based on the source, not the load.
 - The “service type” is not always obvious.
 - Loads other than the “known” load can be connected and may be unmetered.
- Meter form numbers describe certain meter characteristics not the service or application
- Consider that *ground* can be a current carrying conductor when applying Blondel’s Theorem.
- Understand the operation of present day, polyphase solid state meters and how they may be used to advantage

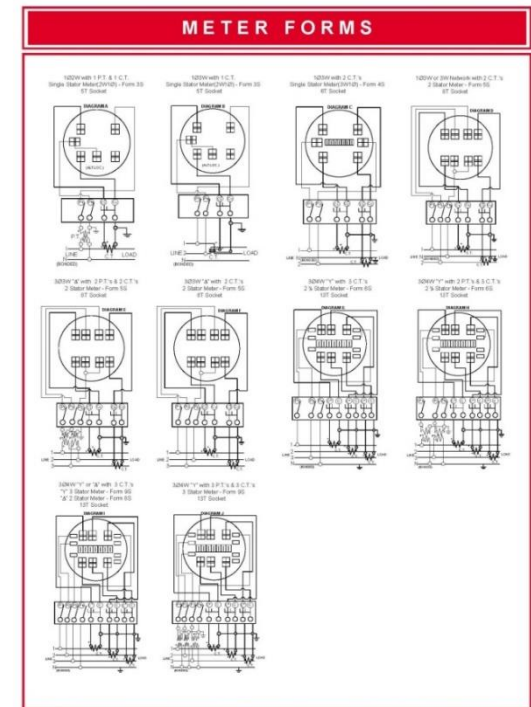


THREE PHASE POWER: BLONDEL'S THEOREM

The theory of polyphase watt-hour metering was first set forth on a scientific basis in 1893 by Andre E. Blondel, engineer and mathematician. His theorem applies to the measurement of real power in a polyphase system of any number of wires. The theorem is as follows:

- If energy is supplied to any system of conductors through N wires, the total power in the system is given by the algebraic sum of the readings of N wattmeters, so arranged that each of the N wires contains one current coil, the corresponding voltage coil being connected between that wire and some common point. If this common point is on one of the N wires, the measurement may be made by the use of $N-1$ wattmeters.



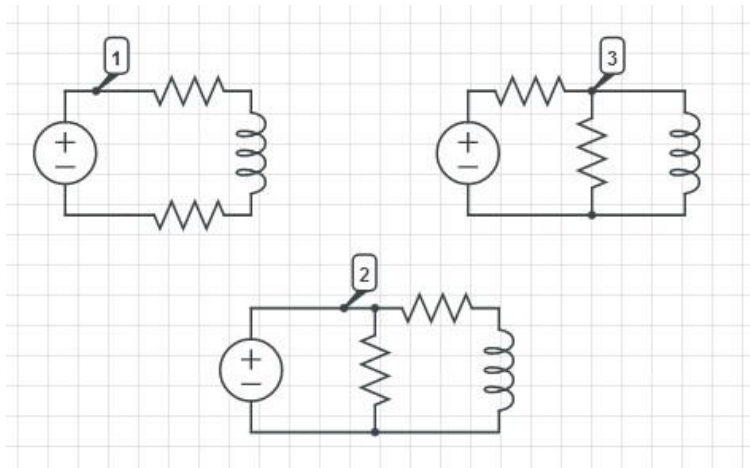- Simply – We can measure the power in a N wire system by measuring the power in N-1 conductors.
- For example, in a 4-wire, 3-phase system we need to measure the power in 3 circuits.





THREE PHASE POWER: BLONDEL'S THEOREM

- If a meter installation meets Blondel's Theorem then we will get accurate power measurements under all circumstances.
- If a metering system does not meet Blondel's Theorem then we will only get accurate measurements if certain assumptions are met.



BLONDEL'S THEOREM

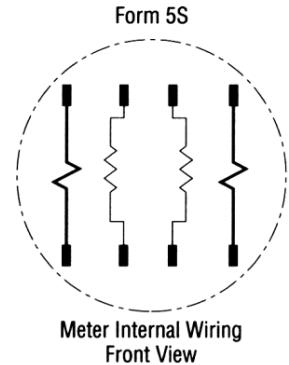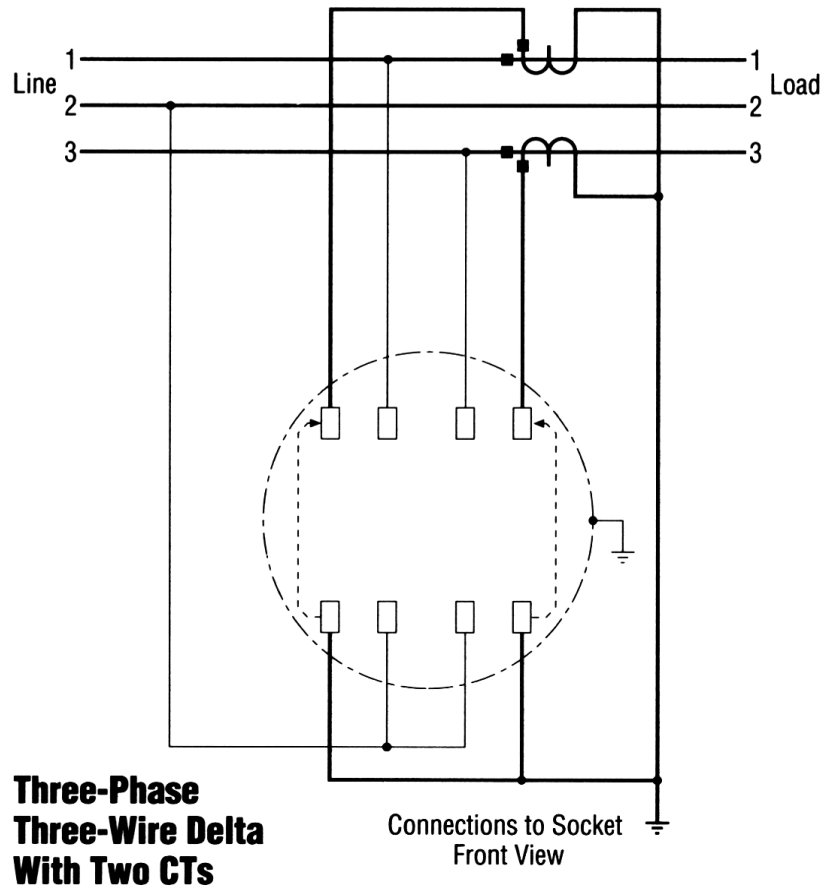


- Three wires
- Two voltage measurements with one side common to Line 2
- Current measurements on lines 1 & 3.

This satisfies Blondel's Theorem.




BLONDEL'S THEOREM

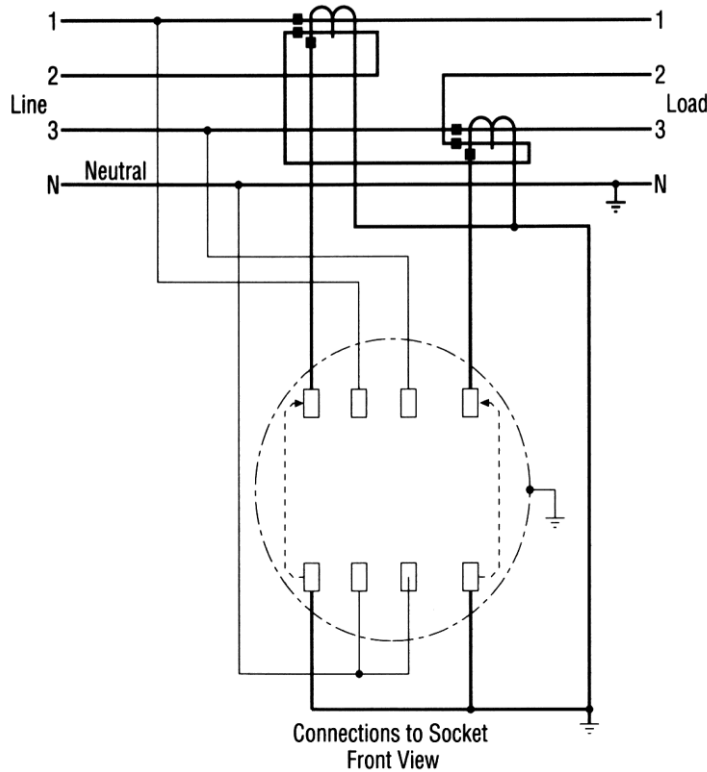

**Three-Phase
Four-Wire Wye
With Two Equal-Ratio CTs**

Form 5S

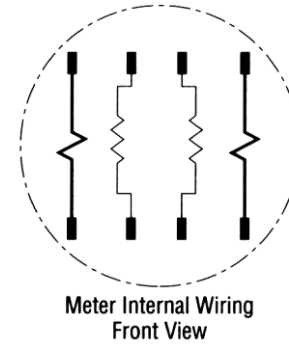


- Four wires
- Two voltage measurements to neutral
- Current measurements on lines 1 & 3.
How about line 2?

This DOES NOT satisfy Blondel's Theorem.



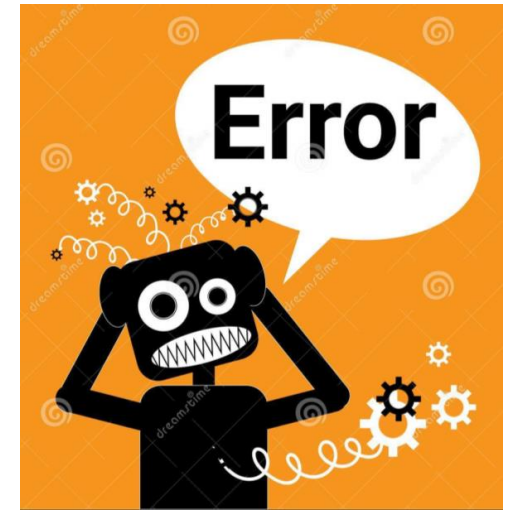- In the previous example:
 - What are the “ASSUMPTIONS”?
 - When do we get errors?
- What would the “Right Answer” be?



$$P_{\text{sys}} = V_a I_a \cos(\theta_a) + V_b I_b \cos(\theta_b) + V_c I_c \cos(\theta_c)$$


- What did we measure?

$$P_{\text{sys}} = V_a [I_a \cos(\theta_a) - I_b \cos(\theta_b)] + V_c [I_c \cos(\theta_c) - I_b \cos(\theta_b)]$$

- Phase B power would be:
 - $P = V_b I_b \cos\theta$
- But we aren't measuring V_b
- What we are measuring is:
 - $I_b V_a \cos(60 - \theta) + I_b V_c \cos(60 + \theta)$
- $\cos(\alpha + \beta) = \cos(\alpha)\cos(\beta) - \sin(\alpha)\sin(\beta)$
- $\cos(\alpha - \beta) = \cos(\alpha)\cos(\beta) + \sin(\alpha)\sin(\beta)$
- So



- $P_b = I_b V_a \cos(60^\circ - \theta) + I_b V_c \cos(60^\circ + \theta)$
- Applying the trig identity
 - $I_b V_a (\cos(60^\circ)\cos(\theta) + \sin(60^\circ)\sin(\theta))$
 $I_b V_c (\cos(60^\circ)\cos(\theta) - \sin(60^\circ)\sin(\theta))$
 - $I_b (V_a + V_c) 0.5 \cos(\theta) + I_b (V_c - V_a) 0.866 \sin(\theta)$
- Assuming
 - Assume $V_b = V_a = V_c$
 - And, they are exactly 120° apart
- $P_b = I_b (2V_b) (0.5 \cos \theta) = I_b V_b \cos \theta$

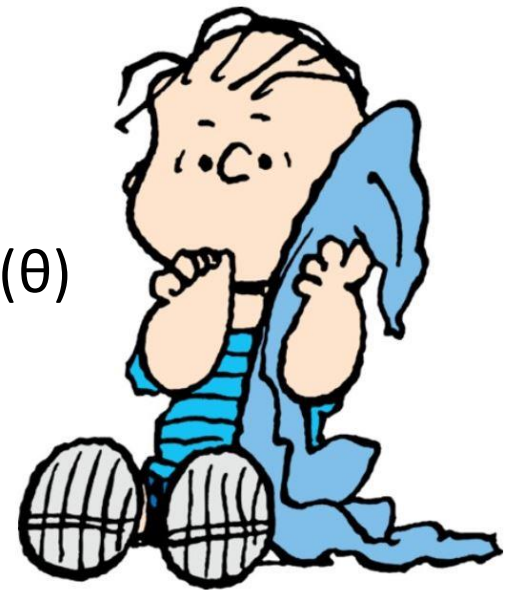


**HAPPINESS IS
ASSUMING THE
WORLD IS LINEAR**

- If $V_a \neq V_b \neq V_c$ then the error is
- %Error =
$$-I_b \left\{ \frac{(V_a + V_c)}{(2V_b)} - \frac{(V_a - V_c)}{0.866 \sin(\theta)} \right\} / (V_b \cos(\theta))$$

How big is this in reality? If

$V_a=117, V_b=120, V_c=119, PF=1$ then $E=-1.67\%$

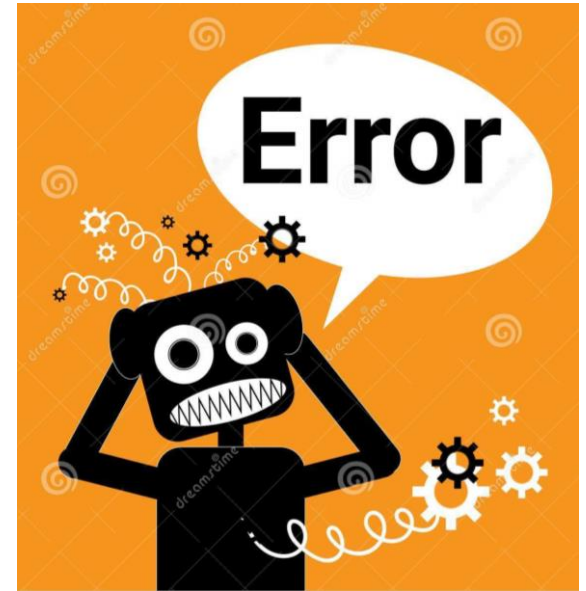$V_a=117, V_b=116, V_c=119, PF=.866$ then $E=-1.67\%$




Power Measurements Handbook

Condition	% V	% I	Phase A				Phase B				non-Blondel
	Imb	Imb	V	ϕ_{van}	I	ϕ_{ian}	V	ϕ_{vbn}	I	ϕ_{ibn}	% Err
All balanced	0	0	120	0	100	0	120	180	100	180	0.00%
Unbalanced voltages PF=1	18%	0%	108	0	100	0	132	180	100	180	0.00%
Unbalanced current PF=1	0%	18%	120	0	90	0	120	180	110	180	0.00%
Unbalanced V&I PF=1	5%	18%	117	0	90	0	123	180	110	180	-0.25%
Unbalanced V&I PF=1	8%	18%	110	0	90	0	120	180	110	180	-0.43%
Unbalanced V&I PF=1	8%	50%	110	0	50	0	120	180	100	180	-1.43%
Unbalanced V&I PF=1	18%	40%	108	0	75	0	132	180	125	180	-2.44%
Unbalanced voltages PF \neq 1 PFa = PFb	18%	0%	108	0	100	30	132	180	100	210	0.00%
Unbalanced current PF \neq 1 PFa = PFb	0%	18%	120	0	90	30	120	180	110	210	0.00%
Unbalanced V&I PF \neq 1 PFa = PFb	18%	18%	108	0	90	30	132	180	110	210	-0.99%
Unbalanced V&I PF \neq 1 PFa = PFb	18%	40%	108	0	75	30	132	180	125	210	-2.44%
Unbalanced voltages PF \neq 1 PFa \neq PFb	18%	0%	108	0	100	60	132	180	100	210	-2.61%
Unbalanced current PF \neq 1 PFa \neq PFb	0%	18%	120	0	90	60	120	180	110	210	0.00%
Unbalanced V&I PF \neq 1 PFa \neq PFb	18%	18%	108	0	90	60	132	180	110	210	-3.46%
Unbalanced V&I PF \neq 1 PFa \neq PFb	18%	40%	108	0	75	60	132	180	125	210	-4.63%




3-WIRE DELTA SERVICE & LOADS

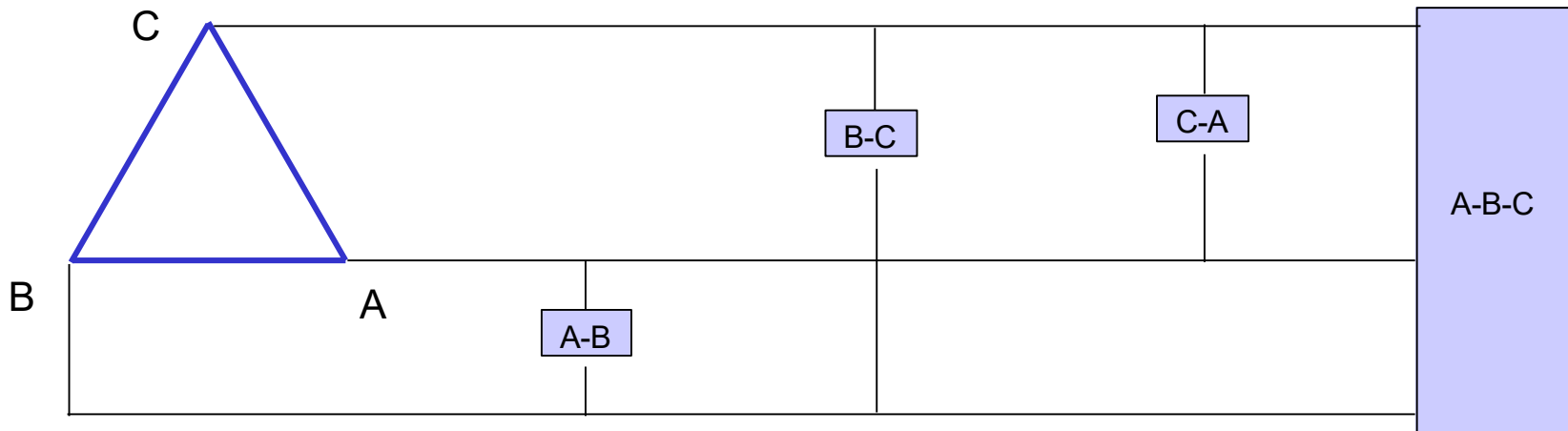


Need to meter single phase line-line loads, as well as three phase loads. Form 12 for Self Contained and Form for Transformer Rated. You need a two element meter only. Network metering is less expensive than Transformer rated. If you need to be transformer rated you save by using a single bushing VT and one less PT since you are only two element (typically do not meter B element).

4-WIRE DELTA SERVICE & LOADS

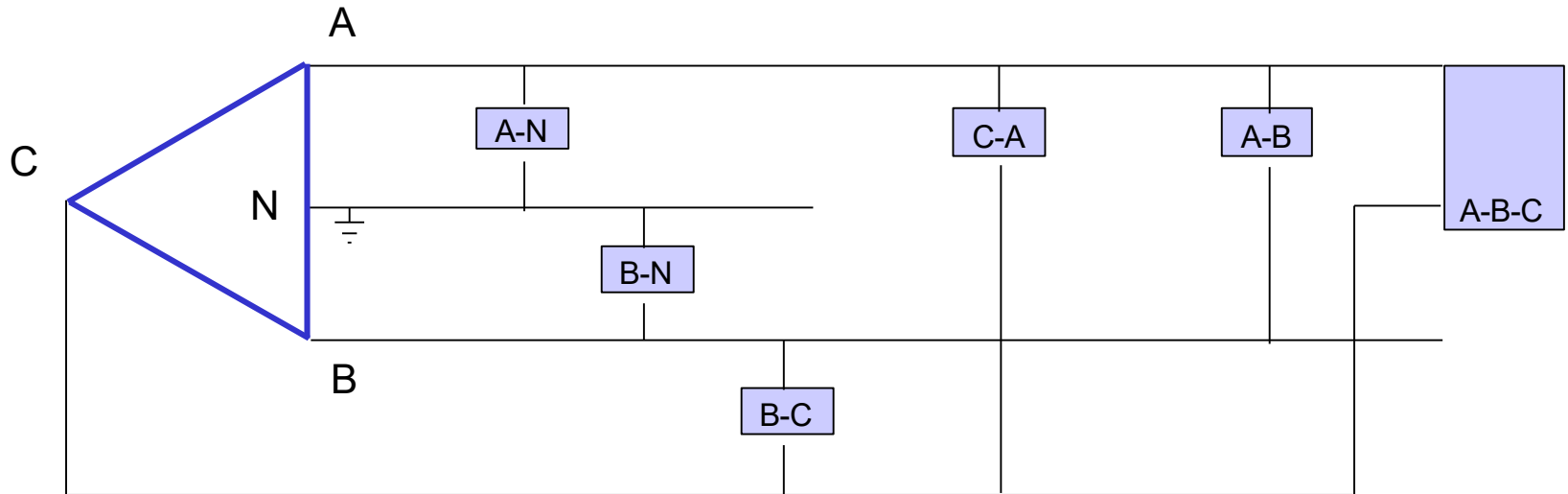

Need to meter single phase line-neutral and line-line loads, as well as three phase loads. For self contained a Form 16 network meter and Transformer rated a 9S meter. We need to be Blondel Compliant and use a three-element meter. Note: For electro-mechanicals common practice was a Form 15S which was not Blondel compliant. Similarly, a 5S is not Blondel compliant for these services.

4-WIRE WYE SERVICE & LOADS


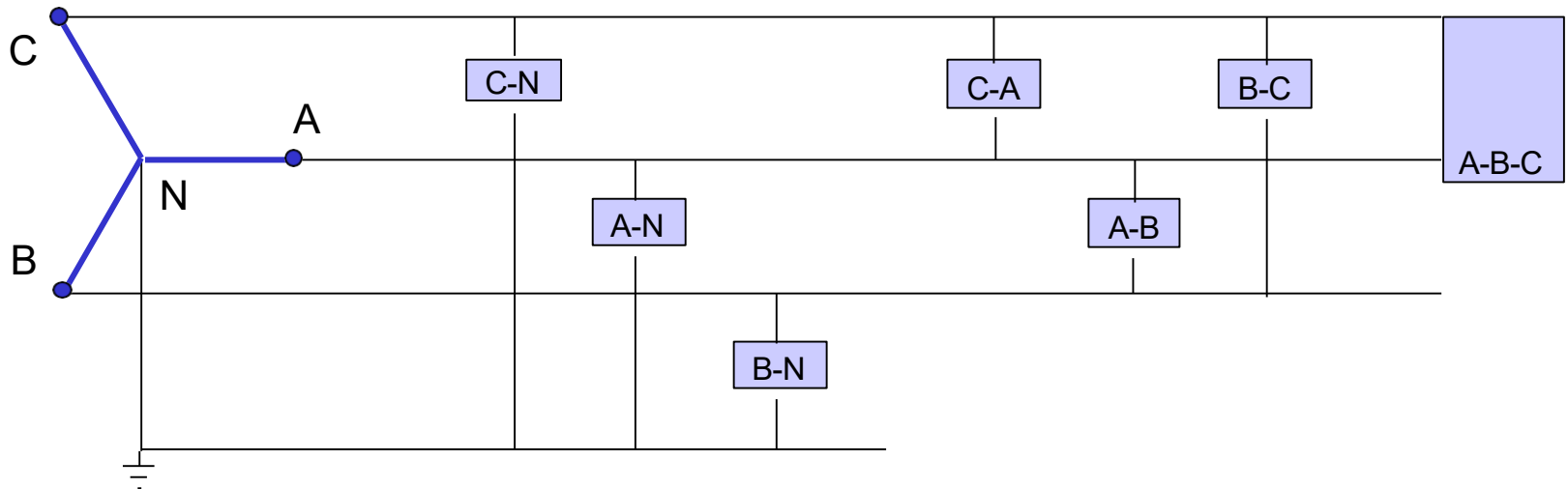


Need to meter single phase line-neutral and line-line loads, as well as three phase loads. Use a Form 16 Network meter and a Form 9S Current Meter.

Meter Accuracy Testing in a Nutshell



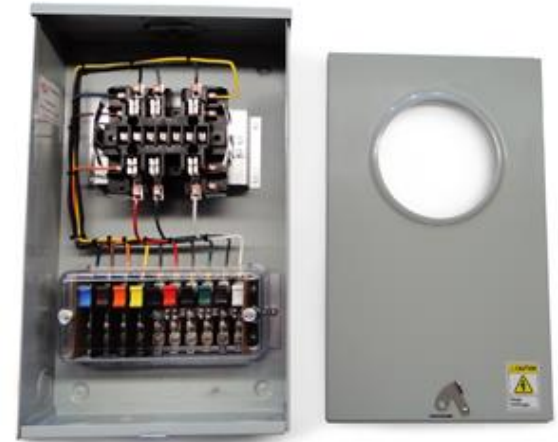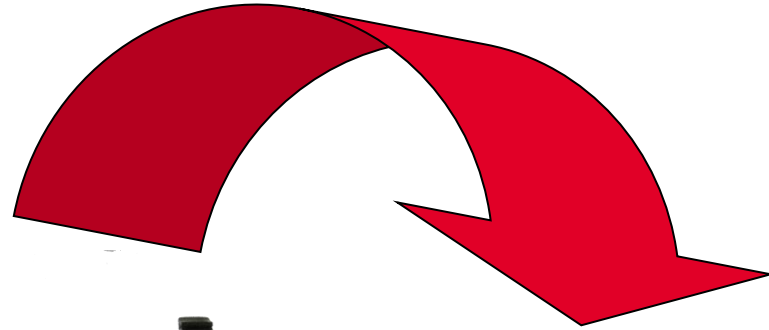
- ✓ Full Load
- ✓ Light Load
- ✓ Power Factor



- One transformer in three wired backwards will give the customer a bill of $\frac{1}{3}$ rd the actual bill.
- One broken wire to a single transformer will give the customer a bill of $\frac{2}{3}$ rd the actual bill
- One dual ratio transformer inappropriately marked in the billing system as 400:5 instead of 800:5 provides a bill that is $\frac{1}{2}$ of the actual bill. And the inverse will give a bill double of what should have been sent. Both are lose-lose situations for the utility.



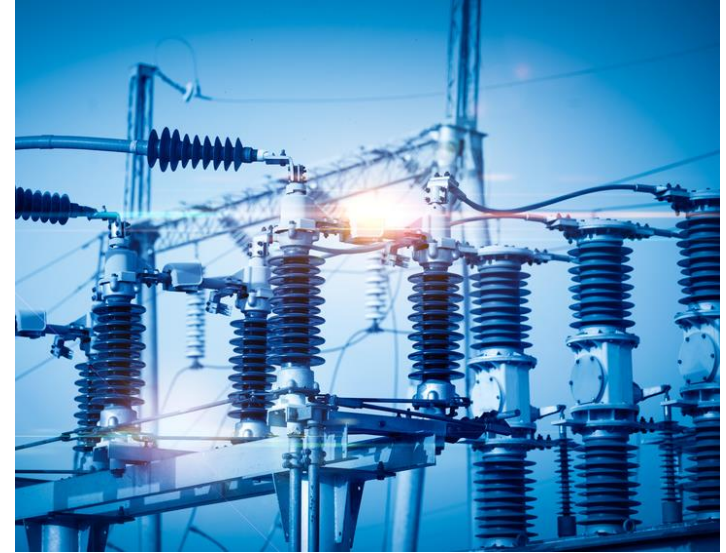- Cross Phasing (wiring errors)
- Loose or Corroded Connections
- CT Mounted Backwards
- CT's with Shorted Turns
- Wrong Selection of Dual Ratio CT
- Detect Magnetized CT's
- Burden Failure in Secondary Circuit
- Open or Shorted Secondary
- Mislabeled CT's
- Ensures all Shorting Blocks have been Removed





- ✓ Meter Accuracy
- ✓ Full Load
- ✓ Light Load
- ✓ Power Factor
- ✓ CT Health
- ✓ Burden Testing
- ✓ Ratio Testing
- ✓ Admittance Testing
- ✓ Site Verification




Functionality with Burden Present on the Secondary Loop

PHASE A

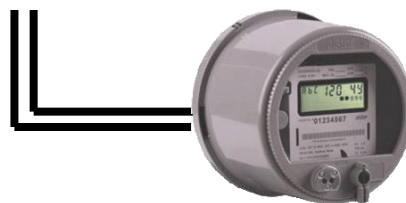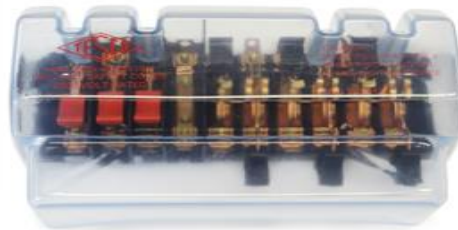

- Some burden will always be present – junctions, meter coils, test switches, cables, etc.
- CT's must be able to maintain an accurate ratio with burden on the secondary.
- Admittance testing?


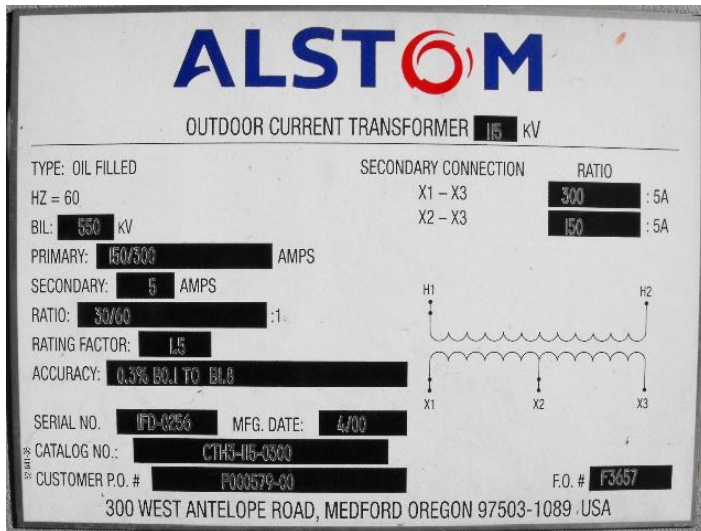
Functionality with Burden Present on the Secondary Loop



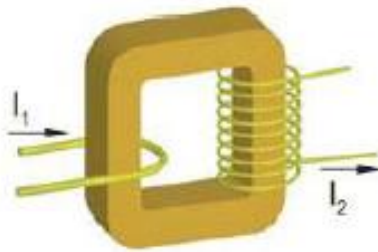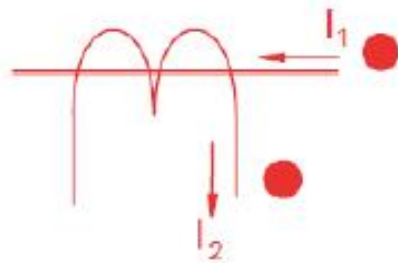Example Burden Spec:
0.3% @ B0.1, B0.2, B0.5
or


There should be less than the 0.3% change in secondary current from initial ("0" burden) reading, when up to 0.5 Ohms of burden is applied

FUNDAMENTALS OF POLYPHASE FIELD METER TESTING AND SITE VERIFICATION (CONT)




$$I_1 \times N_1 = I_2 \times N_2$$

Ideal. No losses

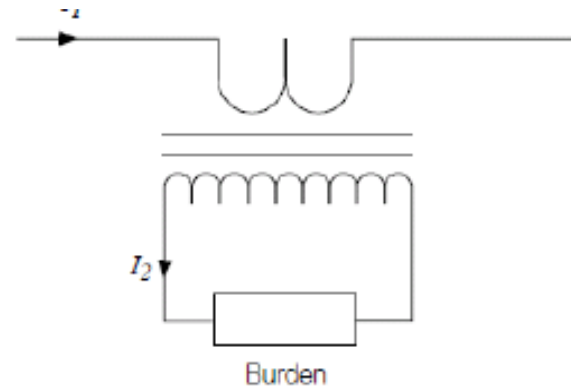

$$I_2 = \frac{N_1}{N_2} \times I_1$$

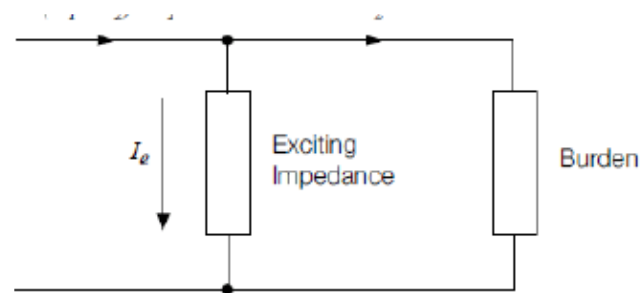

$$I_2 = \frac{N_1}{N_2} \times I_1 - I_e$$

Real, with core losses


Functionality with Burden Present on the Secondary Loop

0.3% @ B0.1, B0.2, B0.5

Initial Reading = 5Amps

$0.3\% \times 5A = 0.015A$


$5A - 0.015 = 4.985A$

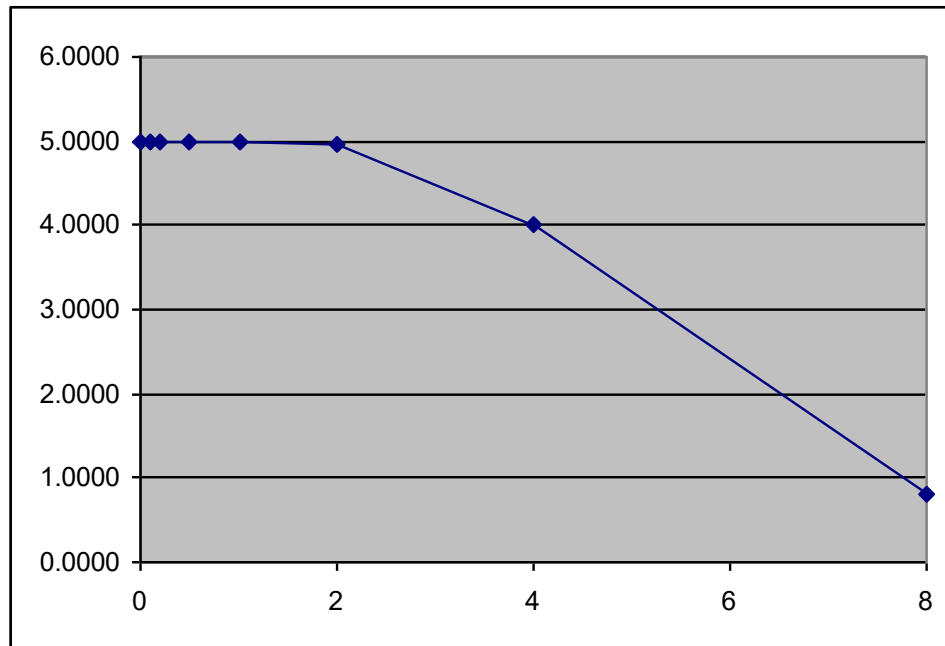

Burden	Reading
0	5.0000
0.1	4.9999
0.2	4.9950
0.5	4.9900
1	4.9800
2	4.9500
4	4.0000
8	0.8000

FUNDAMENTALS OF POLYPHASE FIELD METER TESTING AND SITE VERIFICATION (CONT)

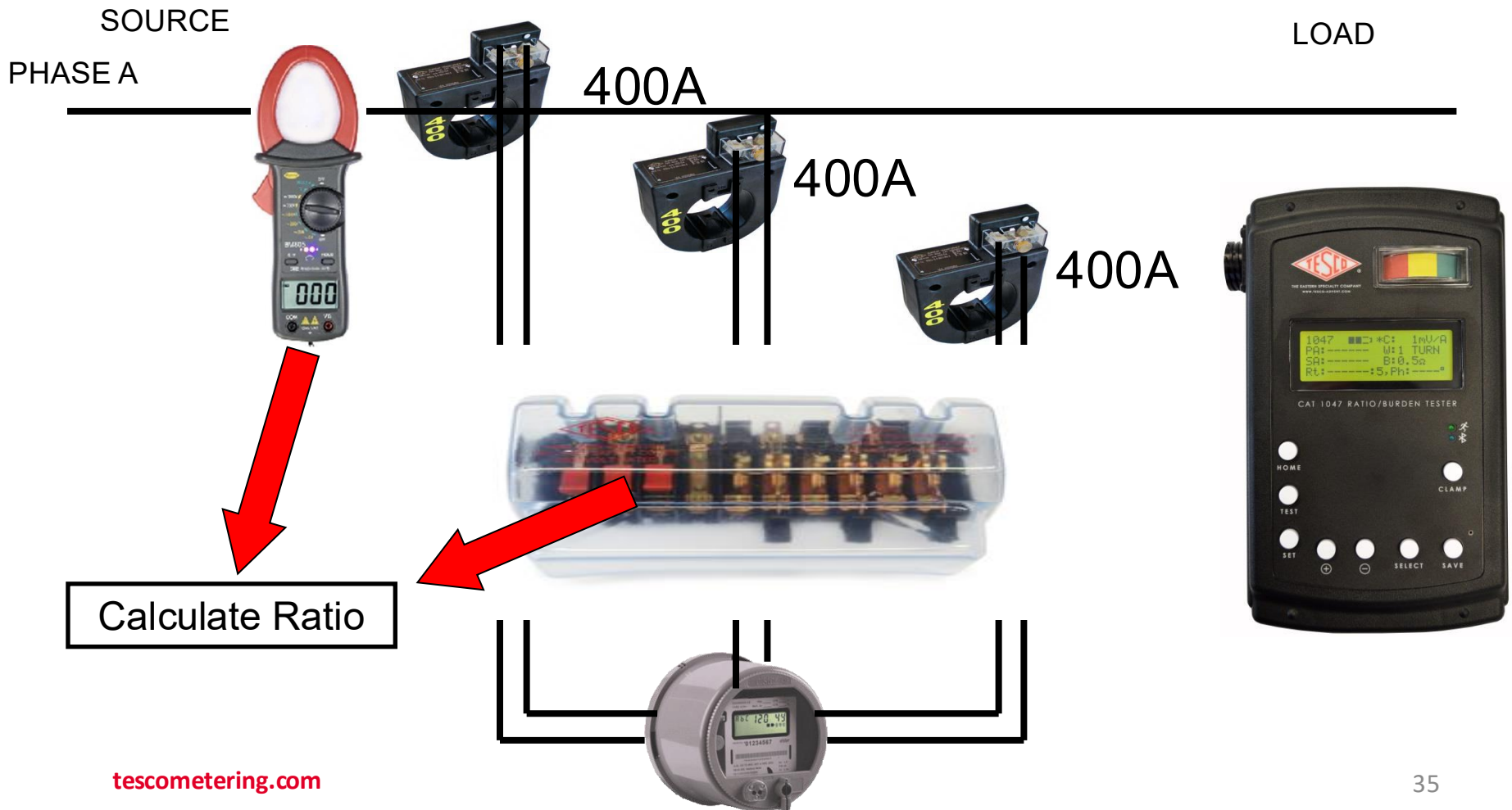Ratio of Primary Current to Secondary Current



Tom Lawton

President

tom.lawton@tescometering.com



TESCO Metering

Bristol, PA

215.228.0500

This presentation can also be found under Meter Conferences and Schools on the TESCO website: tescometering.com

ISO 9001:2015 Certified Quality Company
ISO 17025:2017 Accredited Laboratory