



THE EASTERN SPECIALTY COMPANY

Meter Forms: Wiring and Uses



Prepared by Rob Reese, TESCO
The Eastern Specialty Company

*For PREA
March 14, 2023*

Agenda

Meters 101 - Electro-Mechanical vs Solid-State

Meter Forms

Self-Contained vs Transformer Rated

Blondel's Theorem


Available References (Hardy's, UGLY's Elect Ref)

Examples

1S, 2S, 9S, 16S


Meters 101 – Electro-mechanical

Overview of Functionality

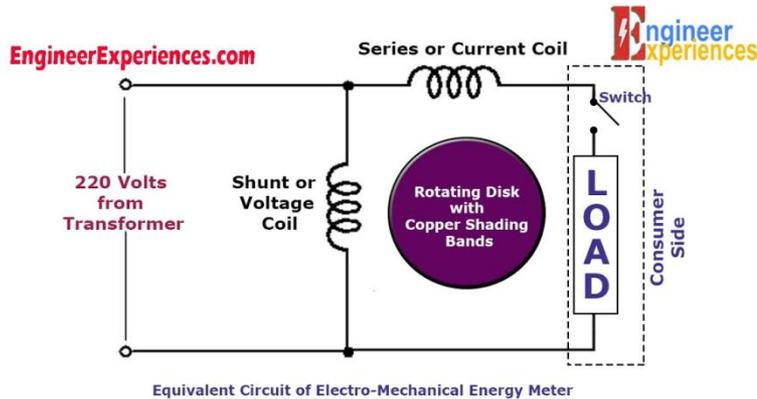

- The electromechanical induction meter operates through [electromagnetic induction](#)
- A non-magnetic, but electrically conductive, metal disc which is made to rotate at a speed proportional to the power passing through the meter
- The disc is acted upon by two sets of [induction coils](#), which form, in effect, a two phase [linear induction motor](#).
- One coil is connected in such a way that it produces a [magnetic flux](#) in proportion to the voltage
- The other coil produces a magnetic flux in proportion to the [current](#).
- The field of the voltage coil is delayed by 90 degrees, due to the coil's inductive nature, and calibrated using a lag coil
- This produces [eddy currents](#) in the disc and the effect is such that a [force](#) is exerted on the disc in proportion to the product of the instantaneous current and instantaneous voltage
- A [permanent magnet](#) acts as an [eddy current brake](#), exerting an opposing force proportional to the [speed of rotation](#) of the disc
- The equilibrium between these two opposing forces results in the disc rotating at a speed [proportional](#) to the power or rate of energy usage
- The disc drives a register mechanism which counts revolutions, much like the [odometer](#) in a car, in order to render a measurement of the total energy used.
- The amount of energy represented by one revolution of the disc is denoted by the symbol Kh which is given in units of watt-hours per revolution.
- A Kh of 7.2 is typical. In this example, each full rotation of the disc is equivalent to 7.2Wh of energy.


Electromechanical energy meter continue...

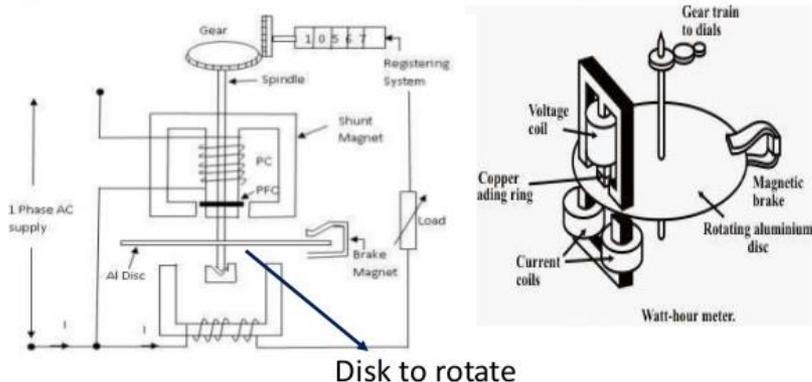

Meters 101 – Solid-state

Overview of Functionality

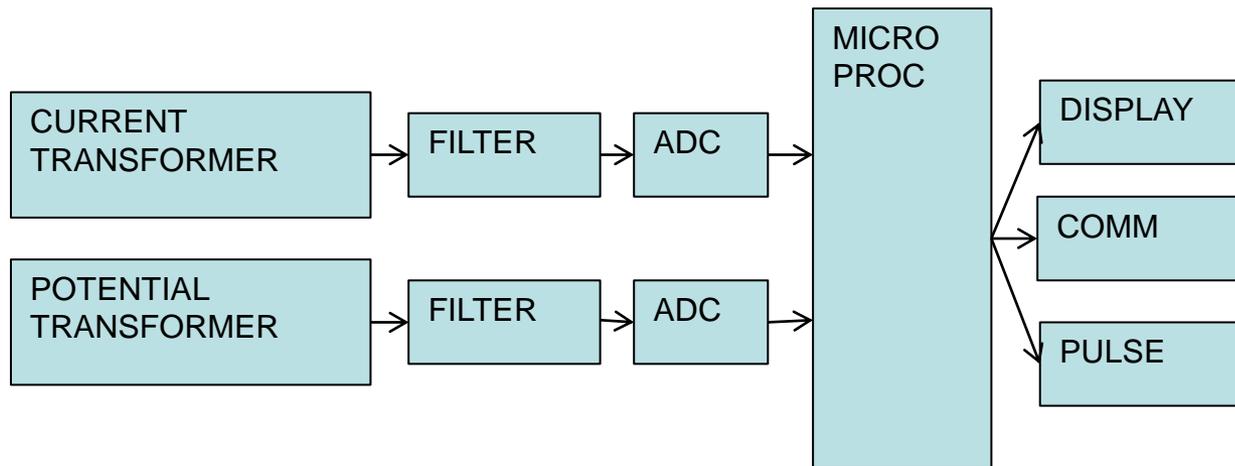- Potential and Current is scaled down and conditioned with transformers and filters
- ADC's (analog to digital converters) digitize the signals
- A micro-processor or DSP executes the calculations
- Resulting data is displayed, sent externally via the communication circuits, and used for the calibrated pulse output



Meter Forms

ANSI C12.10

Meter Forms

1S 14S 39S 17S
3S 12S 2S 35S
76S 4S 10S 25S
45S 46S 66S
5S 11S 6S 32S
26S 9S 13S 16S
15S 24S 56S



Meter Forms



Meter Forms

1S 14S 39S 17S
2S
3S 12S 35S
4S 25S
76S 46S 10S
45S 66S
5S 11S 32S
26S 6S
15S 9S 13S 16S
24S 56S



Meter Forms

SELF-CONTAINED


1S
2S
14S
25S
17S
13S
15S
12S
16S
32S

TRANSFORMER-RATED


39S
76S
4S
11S
6S
56S
3S
36S
29S
5S
8S
66S
10S
7S
35S
46S
26S
45S
9S
24S

Self-Contained Meters

Primarily Residential

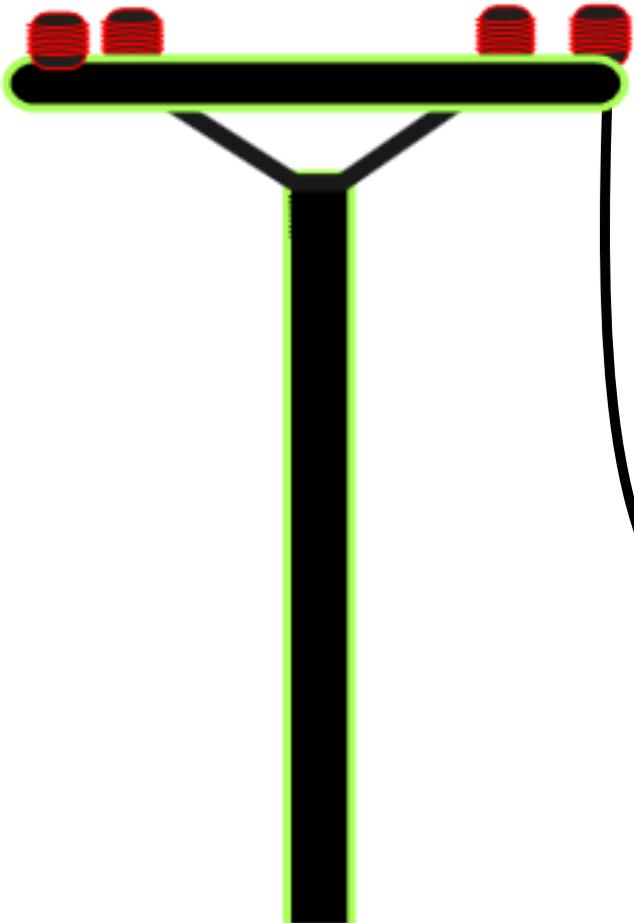


Relatively Low Current
Example: 100A

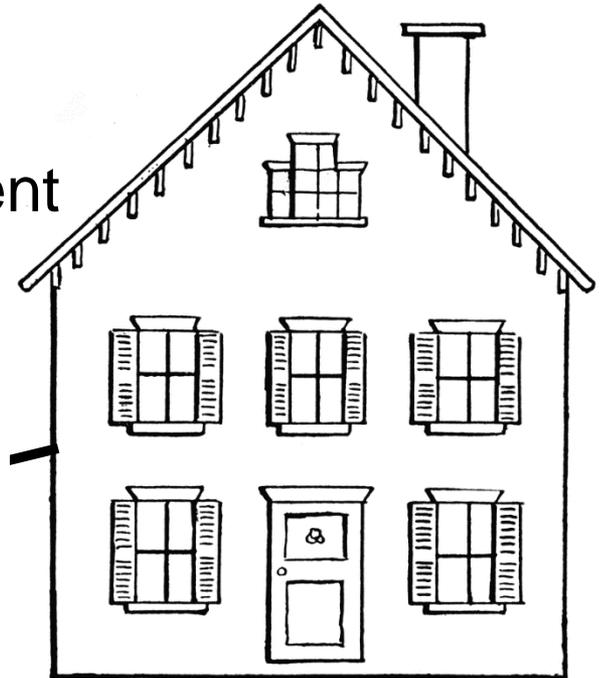

Self-Contained


Primarily Residential

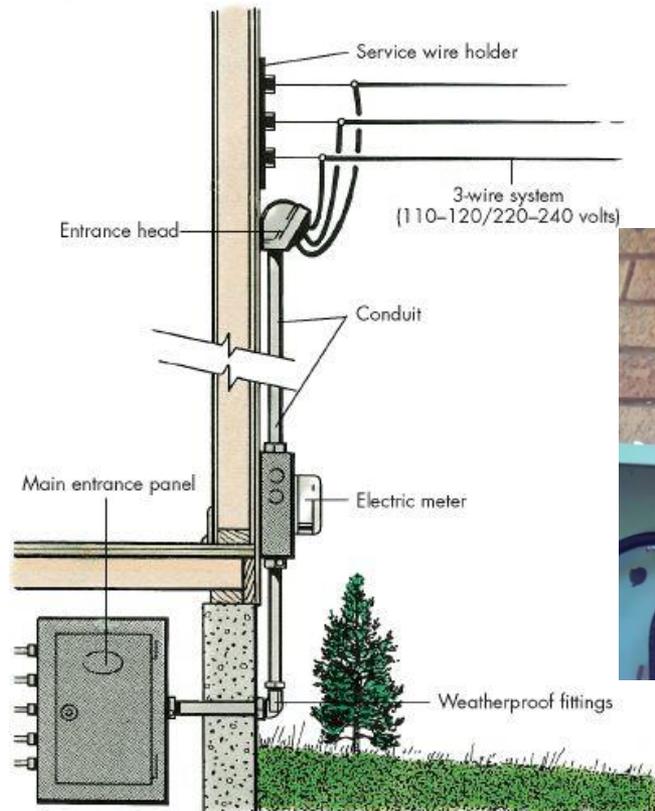

Transformer-Rated Meters


Primarily Commercial/Industrial

Relatively High Current
Example: 4000A

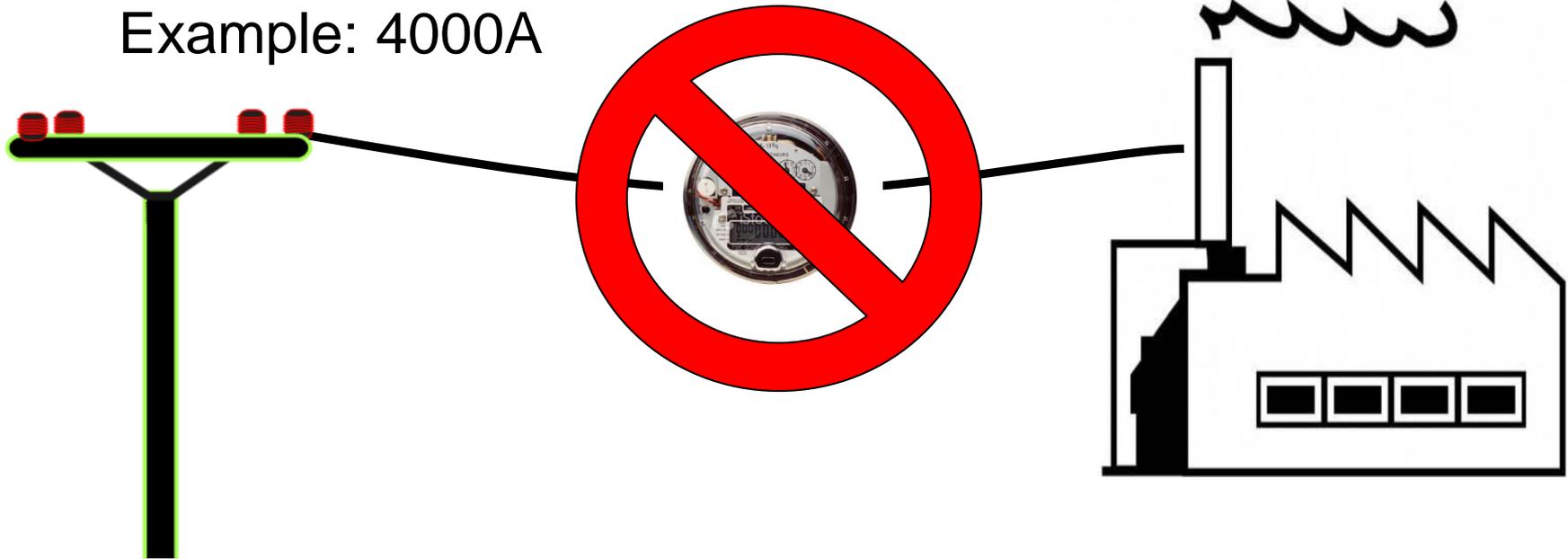


Transformer-Rated Meters

Primarily Commercial/Industrial

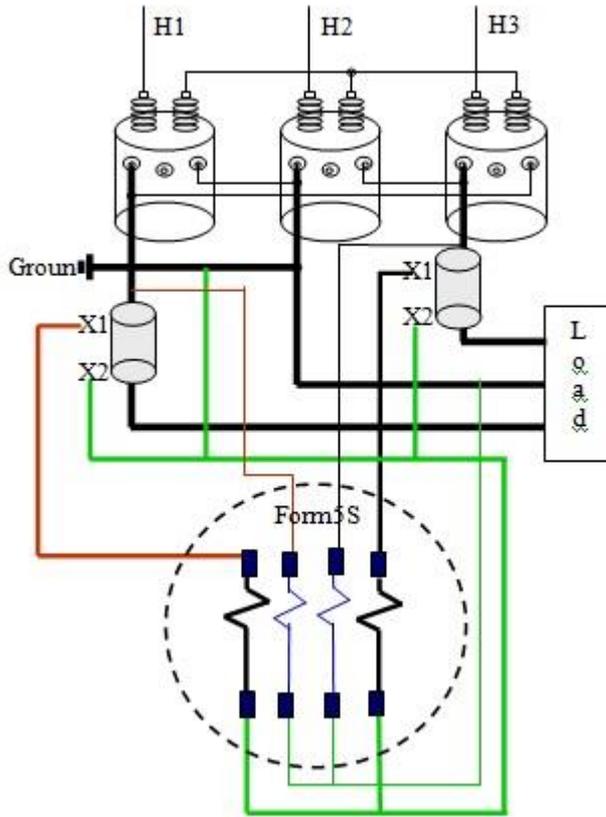

Transformer-Rated Meters

Safety Test Switch

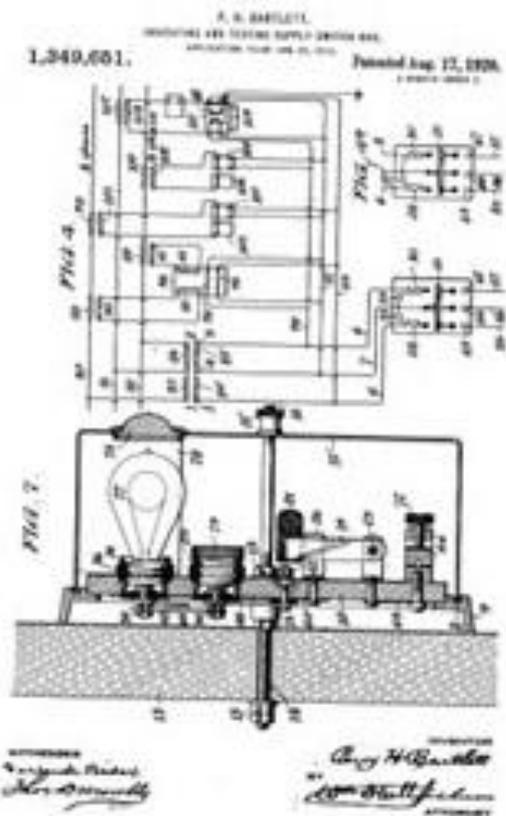

- August 17, 1920
- **TESCO** founders
Joseph Seaman and
Burleigh Currier, along
with Percy Bartlett

Transformer-Rated Meters


Safety Test Switch



Diagram Example

Meter Forms

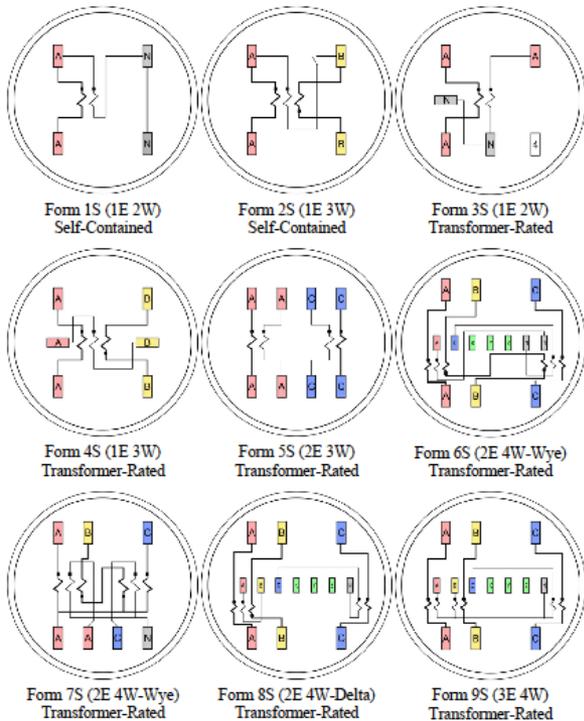Documentation of approved meter forms can be found in ANSI C12.10. "nE" number of elements. "nW" number of wires.




References

- Power Measurements Handbook, Dr. Bill Hardy
- UGLY's Electrical References
- Meterman's Handbook
- Manufacturer's websites

Diagram Example

Meter Forms

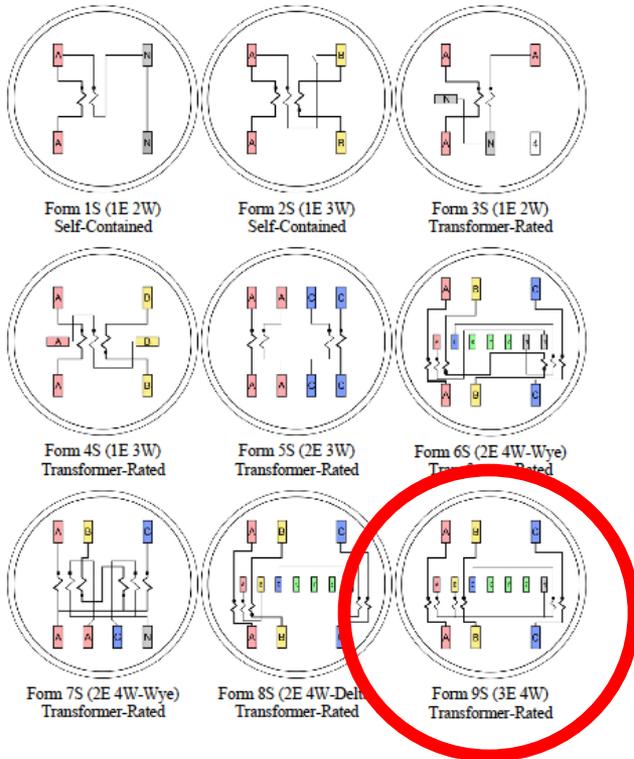Documentation of approved meter forms can be found in ANSI C12.10. "nE" number of elements. "nW" number of wires.




References

- Power Measurements Handbook, Dr. Bill Hardy
- UGLY's Electrical References
- Meterman's Handbook
- Manufacturer's websites

Diagram Example

Form 9S

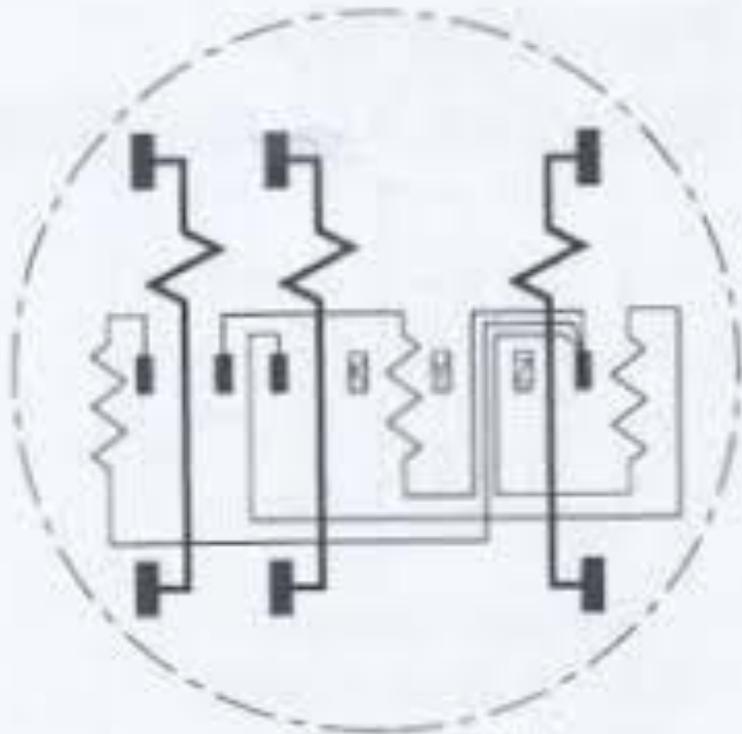

Meter Internal Wiring
Front View

- 3 Current Coils
- 3 Potential Coils

Blondel's Theorem



- French Electrical Engineer Andre Blondel
- Attempt to simplify electrical measurements and validation of the results
- Paper submitted to the International Electric Congress in Chicago in 1893.


$$E = n - 1$$

The theorem states that the power provided to a system of N conductors is equal to the algebraic sum of the power measured by N watt-meters. The N watt-meters are separately connected such that each one measures the current level in one of the N conductors and the potential level between that conductor and a common point. In a further simplification, if that common point is located on one of the conductors, that conductor's meter can be removed and only $N-1$ meters are required.

Blondel's Theorem

$$E = n - 1$$

Blondel Compliant

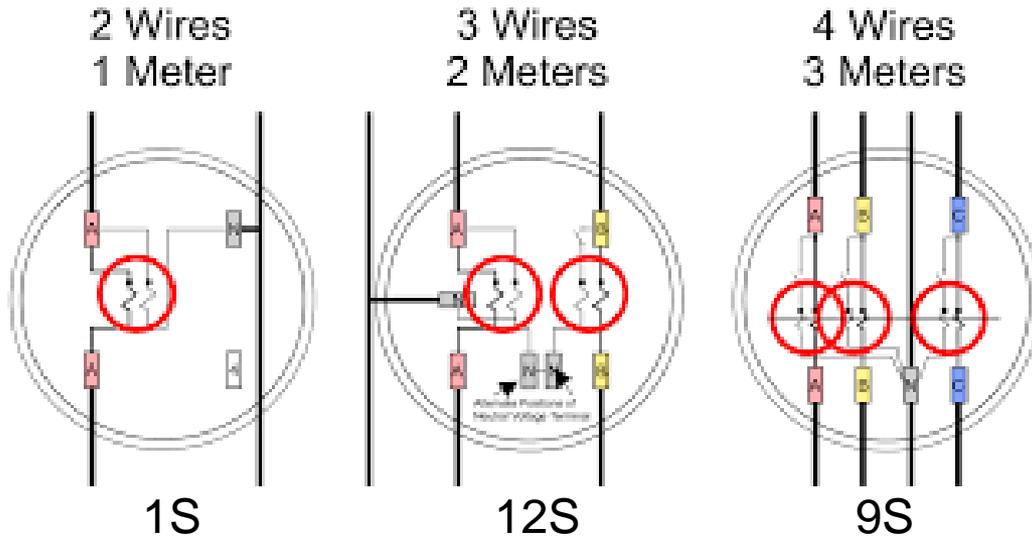


The theorem states that the power provided to a system of N conductors is equal to the algebraic sum of the power measured by N watt-meters. The N watt-meters are separately connected such that each one measures the current level in one of the N conductors and the potential level between that conductor and a common point. In a further simplification, if that common point is located on one of the conductors, that conductor's meter can be removed and only $N-1$ meters are required.

Blondel's Theorem

Non-Blondel Compliant

$$E = n - 1$$

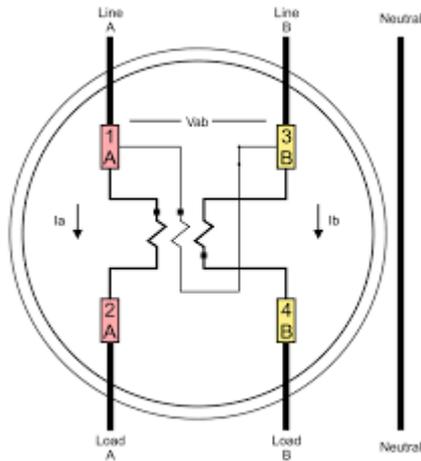

2S

The theorem states that the power provided to a system of N conductors is equal to the algebraic sum of the power measured by N watt-meters. The N watt-meters are separately connected such that each one measures the current level in one of the N conductors and the potential level between that conductor and a common point. In a further simplification, if that common point is located on one of the conductors, that conductor's meter can be removed and only $N-1$ meters are required.

Blondel's Theorem

Why is non-Blondel metering bad?

- Makes assumptions about the service
- Example: balanced voltages
- Assumptions might not be true
- When these assumptions are not true, then there are power measurement errors even if the meter is working perfectly.

The theorem states that the power provided to a system of N conductors is equal to the algebraic sum of the power measured by N watt-meters. The N watt-meters are separately connected such that each one measures the current level in one of the N conductors and the potential level between that conductor and a common point. In a further simplification, if that common point is located on one of the conductors, that conductor's meter can be removed and only $N-1$ meters are required.


Blondel's Theorem

Why are non-Blondel meters used?

- Fewer elements (meters) = lower cost
- Especially true for electro-mechanical meters
- Fewer CT's and PT's = lower cost
- Less wiring and cheaper sockets

The theorem states that the power provided to a system of N conductors is equal to the algebraic sum of the power measured by N watt-meters. The N watt-meters are separately connected such that each one measures the current level in one of the N conductors and the potential level between that conductor and a common point. In a further simplification, if that common point is located on one of the conductors, that conductor's meter can be removed and only $N-1$ meters are required.

Metering Examples

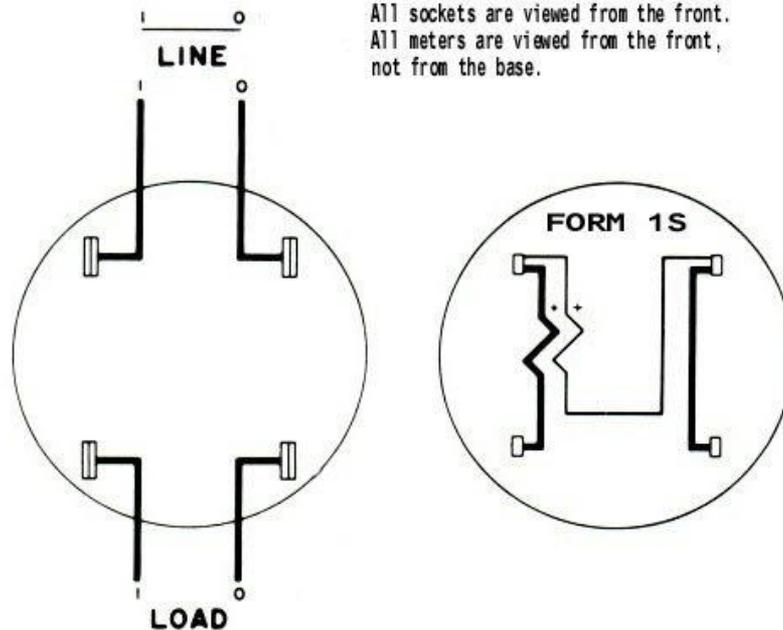


All sockets are viewed from the front.
All meters are viewed from the front,
not from the base.

FORM 1S
1 ϕ , 2 W CIRCUIT
1 Stator, 2 W Meter, Self-Contained

 **BCM**
Bay City Metering
P: 212-575-0785

Metering Examples

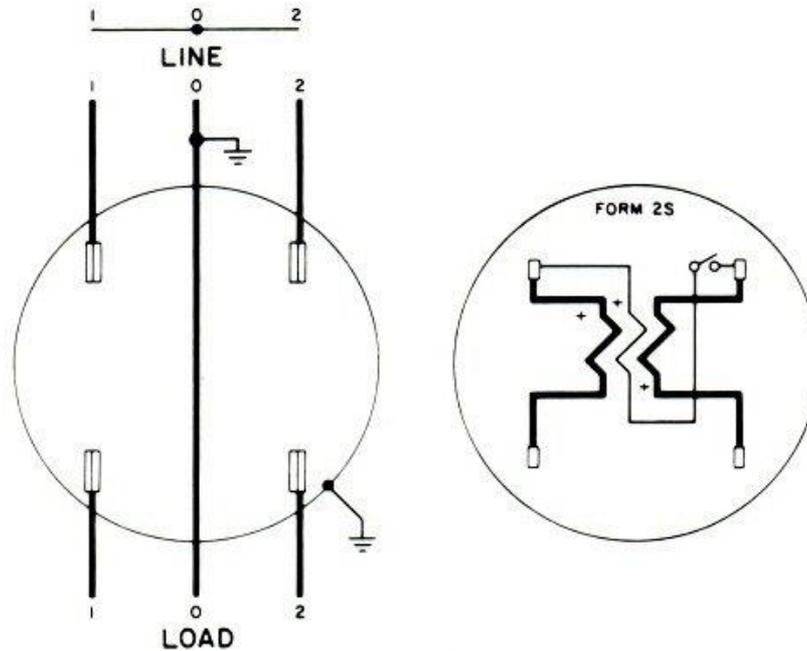


1 ϕ , 3 W CIRCUIT
1 Stator, 1 ϕ , 3 W Meter, Self-Contained

 **BCM**
Bay City Metering
P: 212-575-0785

Slide 25


Metering Examples

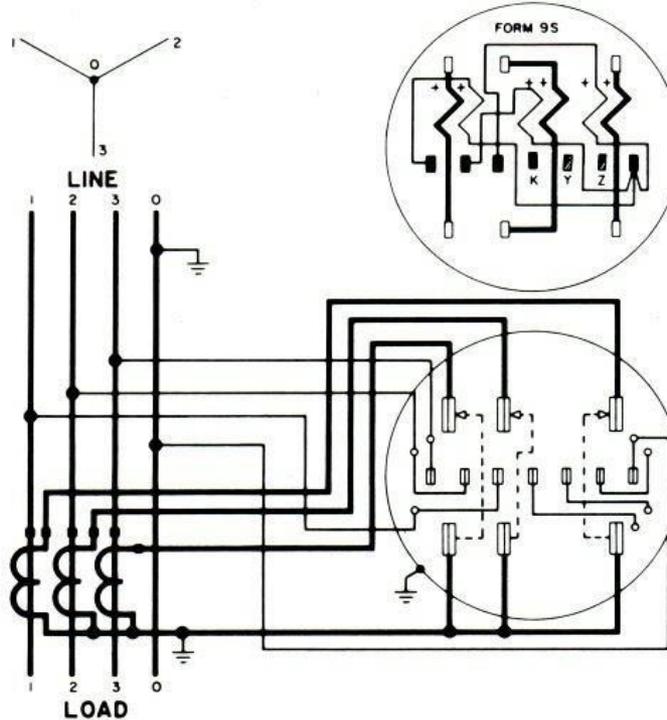

3 ϕ , 4 W, Y CIRCUIT
3 Stator, 3 ϕ , 4 W, Y Meter with 3-2 W CT's




Metering Examples

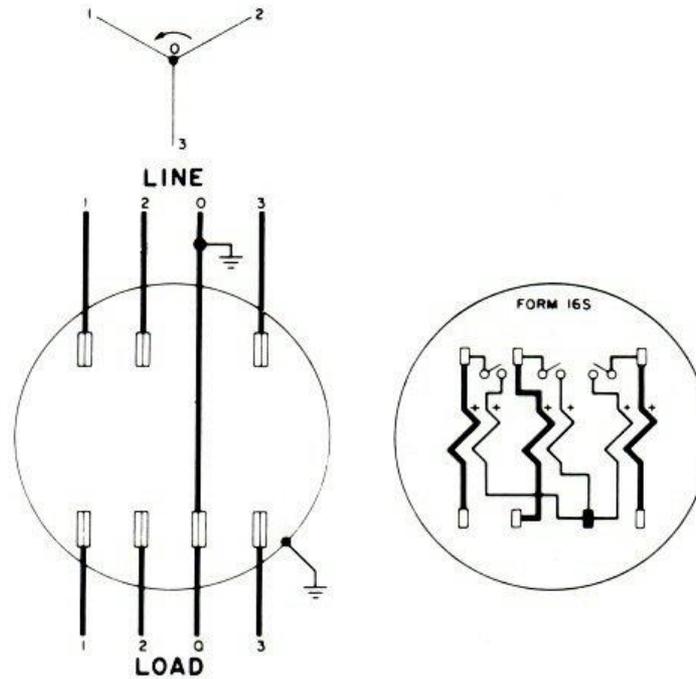

3 ϕ , 4 W, Y CIRCUIT
3 Stator, 3 ϕ , 4 W, Y Meter, Self-Contained



Metering Examples

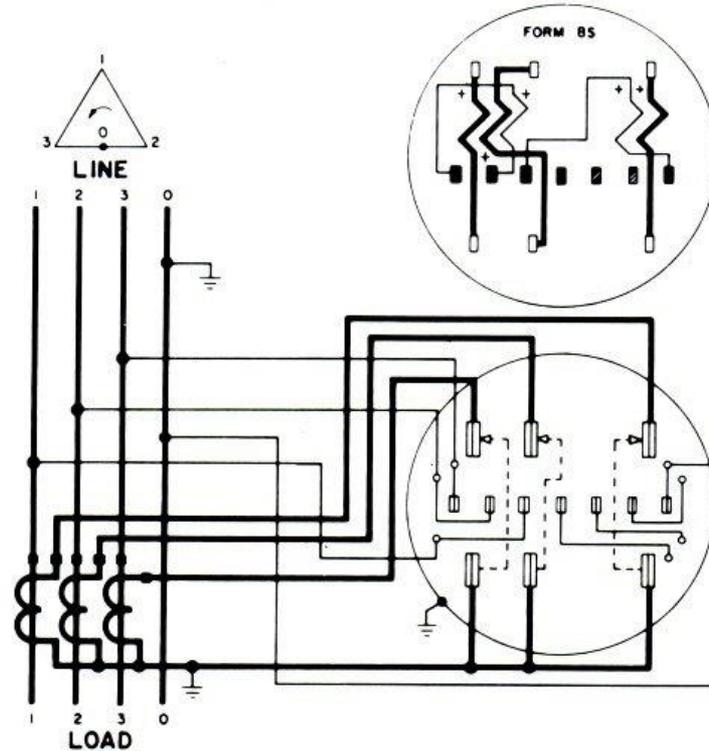

3 ϕ , 4 W, Δ CIRCUIT
2 Stator, 3 ϕ , 4 W, Δ Meter with 3-2 W CT's

 **BCM**
Bay City Metering
P: 212-575-0785

Slide 28

References

- https://en.wikipedia.org/wiki/Blondel%27s_theorem
- <http://www.powermeasurements.org/library/Presentations/NCMS%202013%20-%20Non-Blondel%20Metering.pdf>
- <https://www.baycitymetering.com/>

Questions and Discussion



Rob Reese

rob.reese@tescometering.com

TESCO – The Eastern Specialty Company

Bristol, PA

215-310-8809 (cell)

This presentation can also be found under Meter Conferences and Schools on the TESCO website: www.tescometering.com

ISO 9001:2015 Certified Quality Company
ISO 17025:2017 Accredited Laboratory